

Chapter 3


$$24. (a) P = \left(\frac{I_{CCH} + I_{CCL}}{2} \right) V_{CC} = \left(\frac{1.6 \text{ mA} + 4.4 \text{ mA}}{2} \right) \cdot (5.5) = 16.5 \text{ mW}$$

$$(b) V_{OHmin} = 2.7 \text{ V}$$


$$(c) t_{PLH} = t_{PHL} = 15 \text{ ns}$$

$$(d) V_{OL} = 0.4 \text{ V } (@ I_{OL} = 4.0 \text{ mA}) \\ = 0.5 \text{ V } (@ I_{OL} = 8.0 \text{ mA})$$
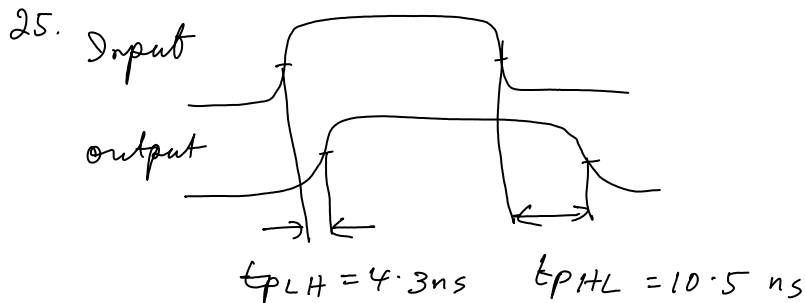
$$(e) t_{PLH} = t_{PHL} = 110 \text{ ns } (V_{CC} = 2 \text{ V } \& T = 125^\circ \text{C}) \\ = 55 \text{ ns } (V_{CC} = 3 \text{ V } \& T = 125^\circ \text{C}) \\ = 22 \text{ ns } (V_{CC} = 4.5 \text{ V } \& T = 125^\circ \text{C})$$



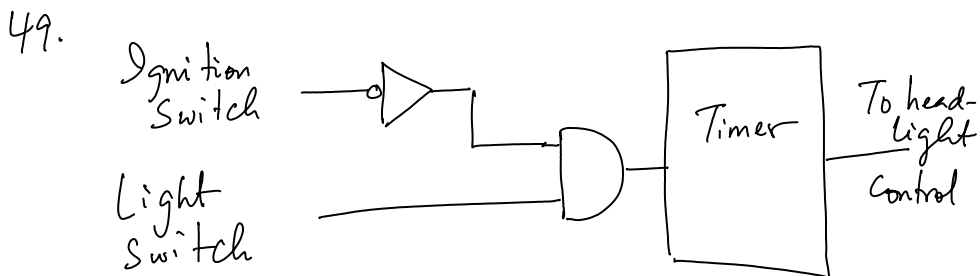
26. Gate A can be operated at a higher frequency because it has a shorter propagation delay than that of gate B.




Timer produces a Low output 15 Secs after the and gate output goes HIGH

output goes HIGH

Chapter 14

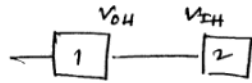

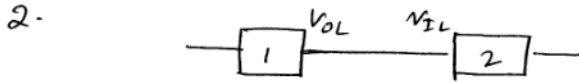1. $NM_H = \text{Noise margin}_H = V_{OH(\min)_1} - V_{IH(\min)_2}$
 $= 2.2 - 2.5 = -0.3 < 0$
No, they are not compatible.



$$NM_L = \text{Noise Margin}_L = V_{IL(\max)_2} - V_{OL(\max)_1}$$
$$= 0.75 - 0.45 = 0.3V > 0$$

Yes, they are compatible

4.

$$NM_H = V_{OH(\min)_1} - V_{IH(\min)_2} = 2.4 - 2.25 = 0.15V$$
$$NM_L = V_{IL(\max)_2} - V_{OL(\max)_1} = 0.65 - 0.4 = 0.25V$$

Maximum amplitudes of noise spikes equal the noise margins of 0.15 & 0.25 for high & low, respectively.

6.

$$P_D(\text{low}) = (5V)(2mA) = 10mW$$
$$P_D(\text{high}) = (5V)(3.5mA) = 17.5mW$$
$$P_D(\text{avg}) = (10 + 17.5)/2 = 13.75mW$$

9. Gate A Average prop delay = $\frac{1ns + 1.2ns}{2} = 1.1ns$
Speed-power product = $(1.1ns)(15mW) = 16.5pJ$


Gate B Average prop delay = $\frac{5+4}{2} = 4.5 \text{ ns}$
 Speed-power product = $(4.5 \text{ ns})(8 \text{ mW}) = 36 \text{ pJ}$

Gate C Average prop delay = $\frac{10 \text{ ns} + 10 \text{ ns}}{2} = 10 \text{ ns}$
 Speed-power product = $(10 \text{ ns})(0.5 \text{ mW}) = 5 \text{ pJ}$

11. G2 is overloaded because it has 12 loads

16. (a) ON: high voltage on base forward-biases the base-emitter junction

(b) OFF: insufficient voltage. Need $0.6 - 0.7 \text{ V}$

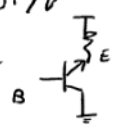(c) OFF: Base voltage lower than emitter 

(d) OFF: Base & emitter at same voltage

20. (a) The driving gate output is high, it is sourcing 3 unit loads.

$I_T = 3(40 \text{ mA}) = 120 \text{ mA}$ (See Table on Page 842)

\uparrow I_{IH} of Load devices

$120 \text{ mA} < | -0.4 \text{ mA} | \text{ OK}$

\uparrow I_{OH} for driver.

(b) The driving gate output is low, it is sinking currents from 2 Loads.

$I_T = 2(-1.6 \text{ mA}) = -3.2 \text{ mA}$

Note $| -3.2 \text{ mA} | < 16 \text{ mA}$

\uparrow $I_{OL \text{ max}}$ for the

(c) G1 output is high, it is sourcing 6 Loads. driver. OK

$$I_T = 6 (40 \mu A) = 240 \mu A < | -0.4 \text{ mA} |$$

G2 output is low, it is sinking OK currents from 2 loads

$$I_T = 2(-1.6 \text{ mA}) = -3.2 \text{ mA} \quad \text{OK}$$

G3 output is high & it is sourcing 2 Loads

$$I_T = 2(40 \mu A) = 80 \mu A \quad \text{OK}$$

22.

(a) $X = \overline{A \cdot B \cdot \bar{C} \cdot \bar{D}}$

(b) $X = \overline{(A \cdot B \cdot C) \cdot (D \cdot E) \cdot (F \cdot G)}$

(c) $X = \overline{(A+B) \cdot (C+D) \cdot (E+F) \cdot (G+H)}$


23. The worst case for determining the minimum value of R_p is when only one gate is sinking all the current (40 mA maximum)

For 10 unit Load: $I_L = 10 \times |-1.6 \text{ mA}| = 16 \text{ mA}$

Current through R_p (for (a), (b) & (c))

$$= 40 \text{ mA} - 16 \text{ mA} = 24 \text{ mA}$$

5V

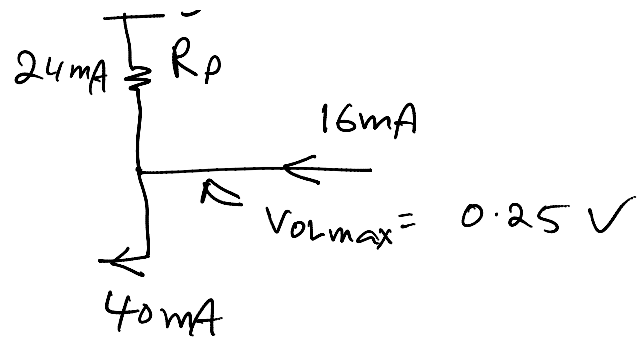

$$\therefore R_p = \frac{5 - 0.25}{24 \text{ mA}} = 198 \Omega \text{ (ohm)}$$