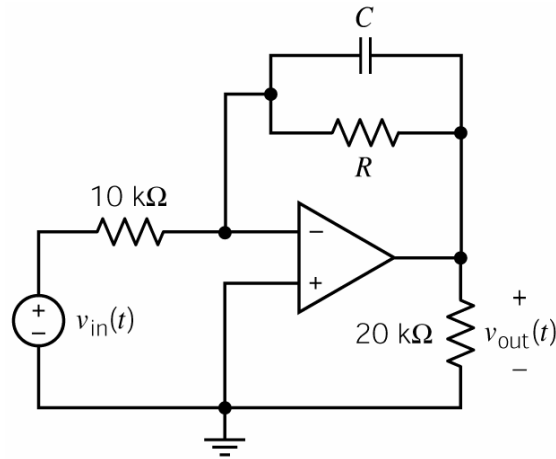


## Circuits and the Fourier Series

### Example 1:



The input to this circuit is the voltage of the voltage source

$$v_{\text{in}}(t) = 2 + 4 \cos(100t) + 5 \cos(400t + 45^\circ) \text{ V}$$

The output is the voltage across the 20-k $\Omega$  resistor

$$v_{\text{out}}(t) = -5 + 7.071 \cos(100t + 135^\circ) + c_4 \cos(400t + \theta_4) \text{ V}$$

Determine the values of the resistance,  $R$ , the capacitance,  $C$ , the coefficient,  $c_4$ , and the phase angle,  $\theta_4$ .

### Solution:

The network function of the circuit is:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = -\frac{R \parallel \frac{1}{j\omega C}}{10^4} = -\frac{R}{1 + j\omega CR} = -\frac{\frac{R}{10^4}}{1 + j\omega CR} = \frac{\frac{R}{10^4}}{\sqrt{1 + (\omega CR)^2}} \angle(180 - \tan^{-1}(\omega CR))$$

The phasors of the input and output are related by

$$|\mathbf{V}_o(\omega)| |\mathbf{H}(\omega)| = |\mathbf{V}_i(\omega)| \quad \text{and} \quad \angle \mathbf{V}_o(\omega) = \angle \mathbf{H}(\omega) + \angle \mathbf{V}_i(\omega)$$

When  $\omega = 0$  (dc)

$$\frac{-5}{2} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = -\frac{\frac{R}{10^4}}{1 + j(0)CR} = -\frac{R}{10^4} \Rightarrow R = 25 \text{ k}\Omega$$

When  $\omega = 100$  rad/s

$$135^\circ = \angle \mathbf{H}(\omega) + 0^\circ = 180^\circ - \tan^{-1}(\omega C R) \Rightarrow \tan(45^\circ) = (100)C(25000)$$

$$\Rightarrow C = 0.4 \mu\text{F}$$

When  $\omega = 400$  rad/s

$$c_4 = (5)|\mathbf{H}(400)| = (5) \left| \frac{\frac{25000}{10^4}}{1 + j(400)(0.4 \times 10^{-6})(25000)} \right| = 3.032$$

$$\theta_4 = 45^\circ + \angle \mathbf{H}(400) = 45^\circ + 180^\circ - \tan^{-1}(400 \times 0.4 \times 10^{-6} \times 25000) = 149^\circ$$

**Example 2:**

The input to a circuit is the voltage

$$v_i(t) = 2 + 4 \cos(25t) + 5 \cos(100t + 45^\circ) \text{ V}$$

The output is the voltage

$$v_o(t) = 5 + 7.071 \cos(25t - 45^\circ) + c_4 \cos(100t + \theta_4) \text{ V}$$

The network function that represents this circuit is

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{H_o}{1 + j \frac{\omega}{p}}$$

Determine the values of the dc gain,  $H_o$ , the pole,  $p$ , the coefficient,  $c_4$ , and the phase angle,  $\theta_4$ .

**Solution:**

The transfer function is

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{H_o}{1 + j \frac{\omega}{p}} = \frac{H_o}{\sqrt{1 + \left(\frac{\omega}{p}\right)^2}} \angle \left( \angle H_o - \tan^{-1} \left( \frac{\omega}{p} \right) \right)$$

The phasors of the input and output are related by

$$|\mathbf{V}_o(\omega)| |\mathbf{H}(\omega)| = |\mathbf{V}_i(\omega)| \text{ and } \angle \mathbf{V}_o(\omega) = \angle \mathbf{H}(\omega) + \angle \mathbf{V}_i(\omega)$$

When  $\omega = 0$  (dc)

$$5 = \frac{H_o}{1 + j\frac{\omega}{p}}(2) = H_o(2) \Rightarrow H_o = 2.5 \text{ V/V}$$

Consequently,  $\angle \mathbf{H}(\omega) = \angle H_o - \tan^{-1}\left(\frac{\omega}{p}\right) = 0 - \tan^{-1}\left(\frac{\omega}{p}\right) = -\tan^{-1}\left(\frac{\omega}{p}\right)$

When  $\omega = 25 \text{ rad/s}$


$$-45^\circ = \angle \mathbf{H}(\omega) + 0 = -\tan^{-1}\left(\frac{\omega}{p}\right) \Rightarrow \tan(45^\circ) = \frac{25}{p} \Rightarrow p = 25 \text{ rad/s}$$

When  $\omega = 100 \text{ rad/s}$

$$c_4 = (5) |\mathbf{H}(100)| = (5) \left| \frac{2.5}{1 + j\frac{100}{25}} \right| = 3.03$$

$$\theta_4 = 45^\circ + \angle \mathbf{H}(100) = 45^\circ - \tan^{-1}\left(\frac{100}{25}\right) = -31^\circ$$

**Example:**

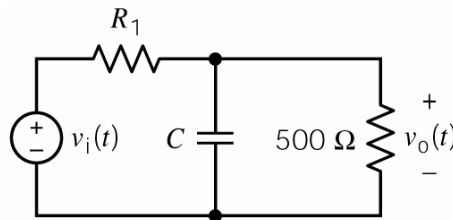

The input to this circuit is the voltage of the independent voltage source

$$v_i(t) = 6 + 4 \cos(1000t) + 5 \cos(3000t + 45^\circ) \text{ V}$$

The output is the voltage across a 500- $\Omega$  resistor

$$v_o(t) = 3.75 + 2.34 \cos(1000t - 20.5^\circ) + c_3 \cos(3000t + \theta_3) \text{ V}$$

Determine the values of the resistance,  $R_1$ , the capacitance,  $C$ , the coefficient,  $c_3$ , and the phase angle,  $\theta_3$ .

**Solution:**

The network function of this circuit

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{R_2 \parallel \frac{1}{j\omega C}}{R_1 + R_2 \parallel \frac{1}{j\omega C}} = \frac{R_2}{R_1 + R_2 + j\omega C R_1 R_2}$$

where  $R_2 = 500 \Omega$ .

The phasors of the input and output are related by

$$|\mathbf{V}_o(\omega)| |\mathbf{H}(\omega)| = |\mathbf{V}_i(\omega)| \quad \text{and} \quad \angle \mathbf{V}_o(\omega) = \angle \mathbf{H}(\omega) + \angle \mathbf{V}_i(\omega)$$

When  $\omega = 0$  (dc)

$$\frac{R_2}{R_1 + R_2} = \frac{3.75}{6} \Rightarrow R_1 = \left( \frac{2.25}{3.75} \right) R_2 = \left( \frac{2.25}{3.75} \right) (500) = 300 \Omega$$

When  $\omega = 1000$  rad/s

$$\begin{aligned} -20.5^\circ = \angle \mathbf{H}(\omega) &= -\tan^{-1} \left( \omega C \frac{R_1 R_2}{R_1 + R_2} \right) \Rightarrow \tan(20.5^\circ) = (1000) C \left( \frac{(300)(500)}{800} \right) \\ &\Rightarrow C = 2 \mu\text{F} \end{aligned}$$

When  $\omega = 3000$  rad/s

$$c_3 \angle \theta_3 = \left( \frac{500}{800 + j(3000)(2 \times 10^{-6})(500)(300)} \right) (5 \angle 45^\circ) = 2.076 \angle -3.4^\circ$$