
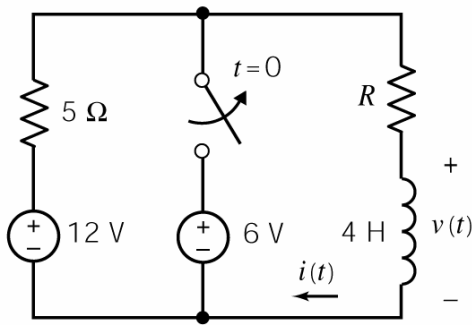


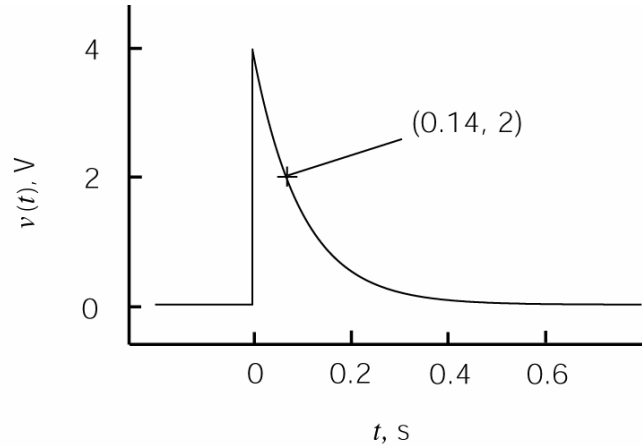- Example 1:** Figure 8-N1a shows a plot of the voltage across the inductor in Figure 8-N1b.
- Determine the equation that represents the inductor voltage as a function of time.
 - Determine the value of the resistance R .
 - Determine the equation that represents the inductor current as a function of time.



(a)



(b)

Figure 8-N1

Solution:

Part a)

The inductor voltage is represented by an equation of the form $v(t) = \begin{cases} D & \text{for } t < 0 \\ E + F e^{-at} & \text{for } t \geq 0 \end{cases}$

where D , E , F and a are unknown constants. The constants D , E and F are described by

$$D = v(t) \text{ when } t < 0, \quad E = \lim_{t \rightarrow \infty} v(t), \quad E + F = \lim_{t \rightarrow 0^+} v(t)$$

From the plot, we see that

$$D = 0, \quad E = 0, \quad \text{and} \quad E + F = 4 \text{ V}$$

Consequently,

$$v(t) = \begin{cases} 0 & \text{for } t < 0 \\ 4 e^{-at} & \text{for } t \geq 0 \end{cases}$$

To determine the value of a , we pick a time when the circuit is not at steady state. One such point is labeled on the plot in Figure 8-N1. We see $v(0.14) = 2 \text{ V}$, that is, the value of the voltage is 2 volts at time 0.14 seconds. Substituting these into the equation for $v(t)$ gives

$$2 = 4e^{-a(0.14)} \Rightarrow a = \frac{\ln(0.5)}{-0.14} = 5$$

Consequently

$$v(t) = \begin{cases} 0 & \text{for } t < 0 \\ 4e^{-5t} & \text{for } t \geq 0 \end{cases}$$

Part b)

Figure 8-N2a shows the circuit immediately after the switch opens. In Figure 8-N2b, the part of the circuit connected to the inductor has been replaced by its Thevenin equivalent circuit. The time constant of the circuit is given by

$$\tau = \frac{L}{R_t} = \frac{4}{R+5}$$

Also, the time constant is related to the exponent in $v(t)$ by $-5t = -\frac{t}{\tau}$. Consequently

$$5 = \frac{1}{\tau} = \frac{R+5}{4} \Rightarrow R = 15 \Omega$$

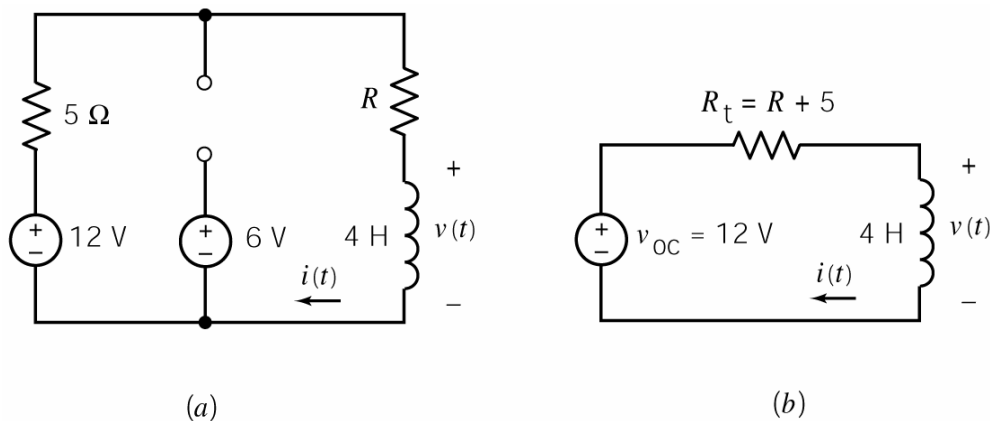


Figure 8-N2

Part c)

The inductor current is related to the inductor voltage by

$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0)$$

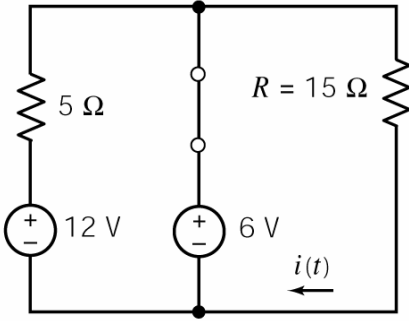


Figure 8-N3

Figure 8-N3 show the circuit before the switch opens. The closed switch is represented by a short circuit. The circuit is at steady state and the voltage sources have constant voltages so the inductor acts like a short circuit. The inductor current is given by

$$i(t) = \frac{6}{15} = 0.4 \text{ A}$$

In particular, $i(0^-) = 0.4 \text{ A}$. The current in an inductor is continuous, so $i(0^+) = i(0^-)$. Consequently,

$$i(0) = 0.4 \text{ A}$$

Returning to the equation for the inductor current, we have


$$i(t) = \frac{1}{4} \int_0^t 4e^{-5\tau} d\tau + 0.4 = \frac{1}{-5} (e^{-5t} - 1) + 0.4 = 0.6 - 0.2e^{-5t}$$

In summary,


$$i(t) = \begin{cases} 0.4 & \text{for } t < 0 \\ 0.6 - 0.2e^{-5t} & \text{for } t \geq 0 \end{cases}$$

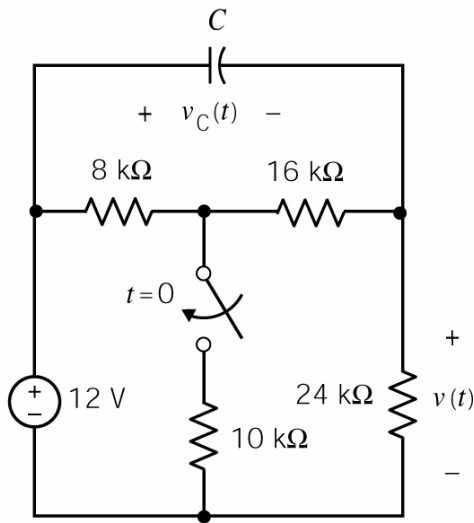Example 2: Figure 8-N4a shows a plot of $v(t)$, the voltage across the $24\text{ k}\Omega$ resistor in Figure 8-N4b.

- Determine the equation that represents $v(t)$ as a function of time.
- Determine the value of the capacitance C .



(a)

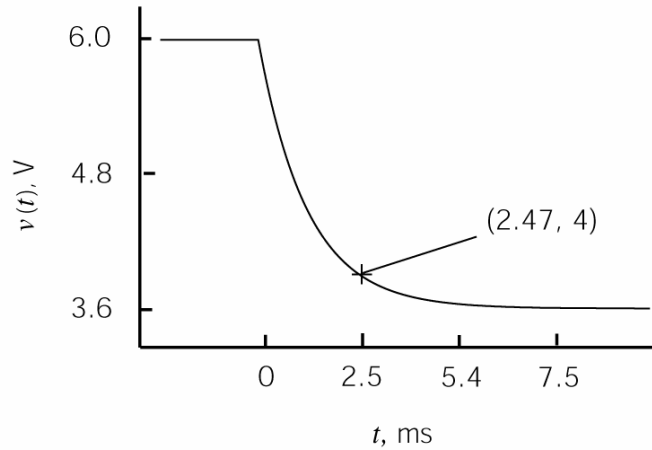

(b)

Figure 8-N4

Part a)

The voltage is represented by an equation of the form $v(t) = \begin{cases} D & \text{for } t < 0 \\ E + F e^{-at} & \text{for } t \geq 0 \end{cases}$

where D , E , F and a are unknown constants. The constants D , E and F are described by

$$D = v(t) \text{ when } t < 0, \quad E = \lim_{t \rightarrow \infty} v(t), \quad E + F = \lim_{t \rightarrow 0^+} v(t)$$

From the plot, we see that

$$D = 6, \quad E = 3.6, \quad \text{and} \quad E + F = 6 \text{ V}$$

Consequently,

$$v(t) = \begin{cases} 6 & \text{for } t < 0 \\ 3.6 + 2.4 e^{-at} & \text{for } t \geq 0 \end{cases}$$

To determine the value of a , we pick a time when the circuit is not at steady state. One such point is labeled on the plot in Figure 8-N4. We see $v(0.00247) = 4 \text{ V}$, that is, the value of the

voltage is 2 volts at time 0.00247 seconds or 2.47 ms. Substituting these into the equation for $v(t)$ gives

$$4 = 3.6 + 2.4 e^{-a(0.00247)} \Rightarrow a = \frac{\ln(0.1667)}{-0.00247} = 725$$

Consequently

$$v(t) = \begin{cases} 6 & \text{for } t < 0 \\ 3.6 + 2.4 e^{-725t} & \text{for } t \geq 0 \end{cases}$$

Part b)

Figure 8-N5a shows the circuit immediately after the switch closes. In Figure 8-N5b, the part of the circuit connected to the capacitor has been replaced by its Thevenin equivalent circuit. The time constant of the circuit is given by

$$\tau = R_t C = (11 \times 10^3) C$$

Also, the time constant is related to the exponent in $v(t)$ by $-725t = -\frac{t}{\tau}$. Consequently

$$\frac{1}{725} = (11 \times 10^3) C \Rightarrow C = \frac{1}{725(11 \times 10^3)} = 125 \times 10^{-9} = 125 \text{ nF}$$


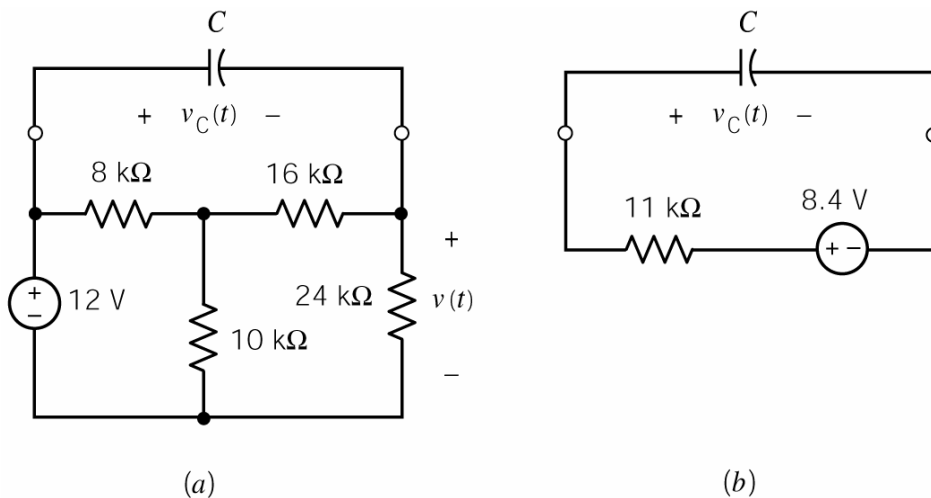



Figure 8-N5

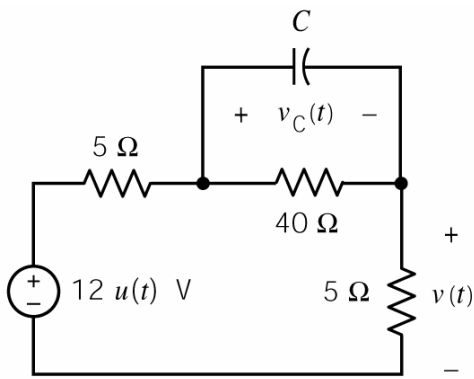Example 3: Figure 8-N6a shows a plot of $v(t)$, the voltage across one of the $5\ \Omega$ resistors in Figure 8-N6b.

- Determine the equation that represents $v(t)$ as a function of time.
- Determine the value of the capacitance C .



(a)

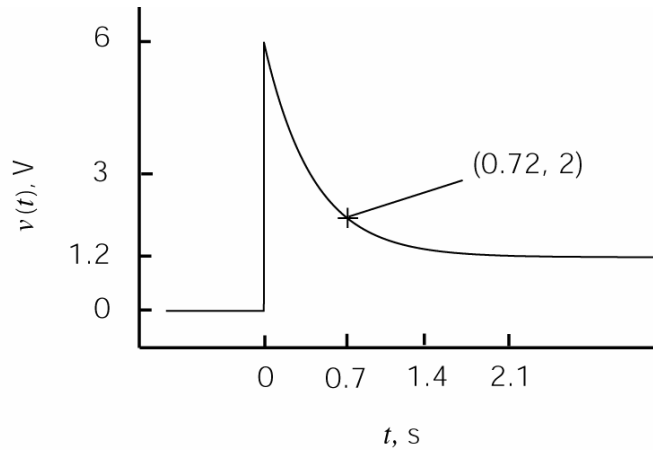

(b)

Figure 8-N6

Part a)

The voltage is represented by an equation of the form $v(t) = \begin{cases} D & \text{for } t < 0 \\ E + F e^{-at} & \text{for } t \geq 0 \end{cases}$

where D , E , F and a are unknown constants. The constants D , E and F are described by

$$D = v(t) \text{ when } t < 0, \quad E = \lim_{t \rightarrow \infty} v(t), \quad E + F = \lim_{t \rightarrow 0^+} v(t)$$

From the plot, we see that

$$D = 0, \quad E = 1.2, \quad \text{and} \quad E + F = 6 \text{ V}$$

Consequently,

$$v(t) = \begin{cases} 0 & \text{for } t < 0 \\ 1.2 + 4.8 e^{-at} & \text{for } t \geq 0 \end{cases}$$

To determine the value of a , we pick a time when the circuit is not at steady state. One such point is labeled on the plot in Figure 8-N6. We see $v(0.72) = 2 \text{ V}$, that is, the value of the voltage is 2 volts at time 0.72 seconds. Substituting these into the equation for $v(t)$ gives

$$2 = 1.2 + 4.8e^{-a(0.72)} \Rightarrow a = \frac{\ln(0.1667)}{-0.72} = 2.5$$

Consequently

$$v(t) = \begin{cases} 0 & \text{for } t < 0 \\ 1.2 + 4.8e^{-2.5t} & \text{for } t \geq 0 \end{cases}$$

Part b)

Figure 8-N7a shows the circuit immediately after time $t = 0$. In Figure 8-N7b, the part of the circuit connected to the capacitor has been replaced by its Thevenin equivalent circuit.

The time constant of the circuit is given by

$$\tau = R_t C = 8C$$

Also, the time constant is related to the exponent in $v(t)$ by $-725t = -\frac{t}{\tau}$. Consequently

$$\frac{1}{2.5} = 8C \Rightarrow C = \frac{1}{2.5(8)} = \frac{1}{20} = 0.05 \text{ F}$$

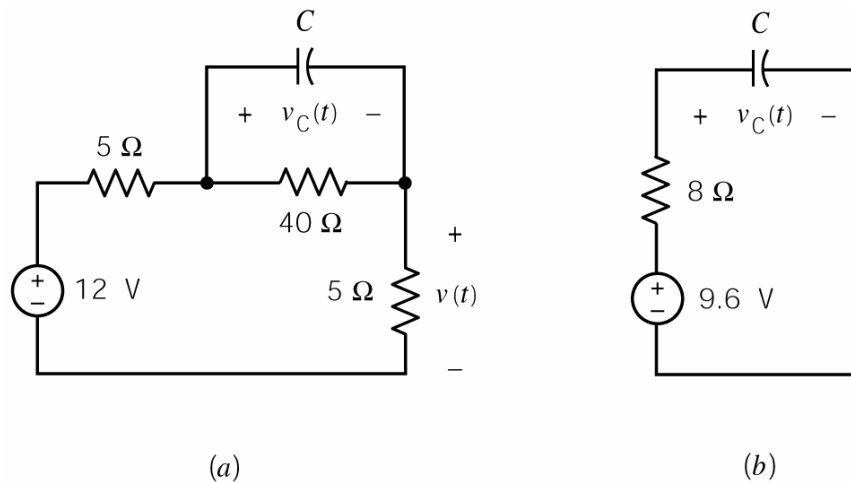


Figure 8-N7