

1. Given that

$$v_i(t) = 24 \cos(3t + 75^\circ) \text{ V}$$

answer the following questions:

- Suppose  $R = 9 \Omega$  and  $L = 5 \text{ H}$ . What are the average, complex and reactive powers delivered by the source to the load?
- Suppose  $R = 15 \Omega$  and  $L = 3 \text{ H}$ . What are the average, complex and reactive powers delivered by the source to the load?
- Suppose the source delivers  $8.47 + j 14.12 \text{ VA}$  to the load. What are the values of the resistance,  $R$ , and the inductance,  $L$ ?
- Suppose the source delivers  $14.12 + j 8.47 \text{ VA}$  to the load. What are the values of the resistance,  $R$ , and the inductance,  $L$ ?
- Suppose the source delivers  $14.12 \text{ W}$  to the load at a power factor of  $0.857$  lagging. What are the values of the resistance,  $R$ , and the inductance,  $L$ ?

2. Suppose the amplitude of the source voltage is doubled so that  $v_i(t) = 48 \cos(3t + 75^\circ) \text{ V}$ .


How will the following change:

- The impedance of the load.
- The complex power delivered to the load.
- The load current.

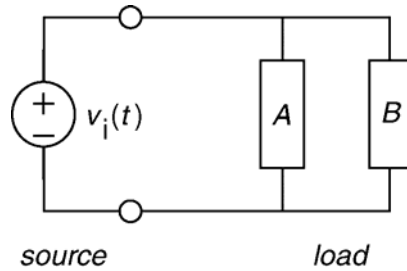3. Suppose, instead, the phase angle of the source voltage is doubled so that

$v_i(t) = 24 \cos(3t + 150^\circ) \text{ V}$ . How will the following change:

- The impedance of the load.
- The complex power delivered to the load.
- The load current.



4. Given that


$$v_i(t) = 24 \cos(3t + 75^\circ) \text{ V}$$

Determine the impedance of the load and the complex power delivered by the source to the load under each of the following conditions:

- The source delivers  $14.12 + j 8.47$  VA to load A and  $8.47 + j 14.12$  VA to load B.
- The source delivers  $8.47 + j 14.12$  VA to load A and the impedance of load B is  $15 + j9 \Omega$ .
- The source delivers 14.12 W to load A at a power factor of 0.857 lagging and the impedance of load B is  $9 + j15 \Omega$ .
- The impedance of load A is  $15 + j9 \Omega$  and the impedance of load B is  $9 + j15 \Omega$ .

**Solution:**

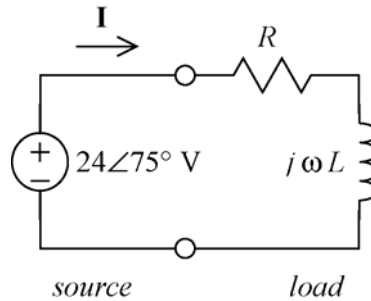1. Represent the circuit in the frequency domain as



$$(a) \quad \mathbf{I} = \frac{24\angle 75^\circ}{9 + j15} = \frac{24\angle 75^\circ}{17.5\angle 59^\circ} = 1.37\angle 16^\circ \text{ A}$$

$$\mathbf{S} = \frac{1}{2}(24\angle 75^\circ)(1.37\angle 16^\circ)^* = \frac{24(1.37)}{2}\angle (75 - 16)^\circ = 16.44\angle 59^\circ = 8.47 + j14.1 \text{ VA}$$

so  $P = 8.47 \text{ W}$  and  $Q = 14.1 \text{ VAR}$

$$(b) \quad \mathbf{I} = \frac{24\angle 75^\circ}{15 + j9} = \frac{24\angle 75^\circ}{17.5\angle 31^\circ} = 1.37\angle 44^\circ \text{ A}$$

$$\mathbf{S} = \frac{1}{2}(24\angle 75^\circ)(1.37\angle 44^\circ)^* = 16.44\angle 31^\circ = 14.1 + j8.47 \text{ VA}$$

$$(c) \quad \mathbf{I} = \left( \frac{2(8.47 + j14.12)}{24\angle 75^\circ} \right)^* = \left( \frac{2(16.44\angle 59^\circ)}{24\angle 75^\circ} \right)^* = (1.37\angle -16^\circ)^* = 1.37\angle 16^\circ \text{ A}$$

$$R + j3L = \frac{24\angle 75^\circ}{1.37\angle 16^\circ} = 17.5\angle 59^\circ = 9 + j15 \Omega$$

$$R = 9 \Omega \text{ and } L = \frac{15}{3} = 5 \text{ H}$$

$$(d) \quad \mathbf{I} = \left( \frac{2(14.12 + j8.47)}{24\angle 75^\circ} \right)^* = (1.37\angle -44^\circ)^* = 1.37\angle 44^\circ \text{ A}$$

$$R + j3L = \frac{24\angle 75^\circ}{1.37\angle 44^\circ} = 17.5\angle 31^\circ = 15 + j9 \Omega$$

$$R = 15 \Omega \text{ and } L = \frac{9}{3} = 3 \text{ H}$$

(e)  $pf = 0.857$  lagging  $\Rightarrow \begin{cases} 0.857 = \cos(\theta) \\ \text{and} \\ \theta > 0 \end{cases}$  so  $\theta = 31^\circ$ .

Next

$$14.12 = P = |\mathbf{S}| \cos \theta = |\mathbf{S}|(0.857)$$

so

$$|\mathbf{S}| = \frac{14.12}{0.857} = 16.48 \text{ VA}$$

Then

$$\mathbf{S} = 16.48 \angle 31^\circ = 14.12 + j8.49$$

and

$$\mathbf{I} = \left( \frac{2\mathbf{S}}{\mathbf{V}} \right)^* = \left[ \frac{2(16.48 \angle 31^\circ)}{24 \angle 75^\circ} \right]^* = 1.37 \angle 44^\circ$$

$$R + j3L = \frac{24 \angle 75^\circ}{1.37 \angle 44^\circ} = 17.5 \angle 31^\circ = 15 + j9 \ \Omega$$

so

$$R = 15 \ \Omega \quad L = 3 \text{ H}$$


2. Doubling the amplitude of  $v_i(t)$ :

- (c) doubles the amplitude of the load current.
- (a) does not change the impedance.
- (b) multiplies the complex power by  $2^2 = 4$ .

3. Doubling the angles of  $v_i(t)$  increases the angle of  $v_i(t)$  by  $75^\circ$

- (c) increases the angle of the load current by  $75^\circ$ .
- (a) does not change the impedance.
- (b) does not change the complex power.

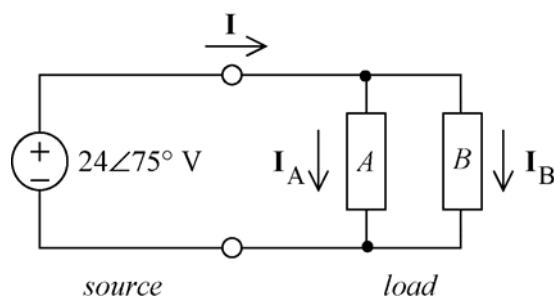4. Represent the circuit in the frequency domain as



(a)

$$\mathbf{I}_A = \left( \frac{2(14.12 + j8.47)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 44^\circ \text{ A}$$

$$\mathbf{I}_B = \left( \frac{2(8.47 + j14.12)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 16^\circ \text{ A}$$

$$\begin{aligned} \mathbf{I} &= \mathbf{I}_A + \mathbf{I}_B = (1.37 \angle 44^\circ) + (1.37 \angle 16^\circ) = (0.986 + j0.954) + (1.319 + j0.377) \\ &= 2.305 + j1.331 = 2.662 \angle 30^\circ \text{ A} \end{aligned}$$

$$\mathbf{Z} = \frac{24 \angle 75^\circ}{2.662 \angle 30^\circ} = 9.016 \angle 45^\circ$$

$$\mathbf{S} = \frac{1}{2} (24 \angle 75^\circ) (2.662 \angle 30^\circ)^* = 31.9 \angle 45^\circ = 22.59 + j22.59 \text{ VA}$$

(b)

$$\mathbf{I}_A = \left( \frac{2(8.47 + j14.12)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 16^\circ \text{ A}$$

$$\mathbf{I}_B = \frac{24 \angle 75^\circ}{15 + j9} = 1.37 \angle 44^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662 \angle 30^\circ \text{ A}$$

$$\mathbf{Z} = \frac{24 \angle 75^\circ}{2.662 \angle 30^\circ} = 9.016 \angle 45^\circ \Omega$$

$$\mathbf{S} = 22.59 + j22.59 \text{ VA}$$

(c)

$$\mathbf{P} = 14.12 \text{ W} = \frac{24 |\mathbf{I}_A|}{2} \cos(75 - \theta_A)$$

$$\left. \begin{array}{l} 0.857 = \cos(75 - \theta_A) \\ 75 - \theta_A > 0 \end{array} \right\} \Rightarrow \theta_A = 75^\circ - 31^\circ = 44^\circ$$

Then

$$|\mathbf{I}_A| = \frac{2(14.12)}{24 \cos(31^\circ)} = 1.37$$

so

$$\mathbf{I}_A = 1.37 \angle 44^\circ \text{ A}$$

Also

$$\mathbf{I}_B = \frac{24 \angle 75^\circ}{9 + j15} = 1.37 \angle 16^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662 \angle 30^\circ \text{ A}$$

(d)

$$\mathbf{I}_A = \frac{24 \angle 75^\circ}{15 + j9} = 1.37 \angle 44^\circ$$

$$\mathbf{I}_B = \frac{24 \angle 75^\circ}{9 + j15} = 1.37 \angle 16^\circ$$

$$\mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662 \angle 30^\circ \text{ A}$$

$$\mathbf{Z} = \frac{24 \angle 75^\circ}{2.662 \angle 30^\circ} = 9.016 \angle 45^\circ \Omega$$

$$\mathbf{S} = 22.59 + j22.59 \text{ VA}$$