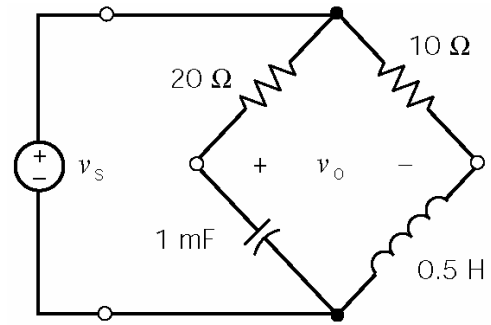
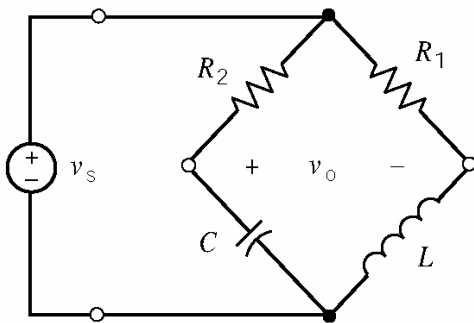


Example:

The input to this circuit is the voltage of the voltage source, v_s . The output of the circuit is the voltage, v_o . Use MATLAB to plot the gain and phase shift of this circuit as a function of frequency for frequencies in the range $1 < \omega < 1000$ rad/s.



Solution:



Using voltage division twice gives

$$\mathbf{V}_o(\omega) = \frac{1}{R_2 + \frac{1}{j\omega C}} \mathbf{V}_s(\omega) - \frac{j\omega L}{R_1 + j\omega L} \mathbf{V}_s(\omega)$$

so

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{1}{1 + j\omega C R_2} - \frac{j\omega L}{R_1 + j\omega L}$$

Modify the MATLAB script given in Section 13.7 of the text:

```
% P13_7_1.m - plot the gain and phase shift of a circuit
%-----
% Create a list of logarithmically spaced frequencies.
%-----

wmin=1;           % starting frequency, rad/s
wmax=1000;       % ending frequency, rad/s

w = logspace(log10(wmin),log10(wmax));

%-----
% Enter values of the parameters that describe the circuit.
%-----

R1 = 10;          % Ohms
R2 = 20;          % Ohms
C = 0.001;       % Farads
L = 0.5;         % Henries

%-----
% Calculate the value of the network function at each frequency.
% Calculate the magnitude and angle of the network function.
%-----
```

```

for k=1:length(w)
    H(k) = 1/(1+j*R2*C*w(k)) - j*L*w(k)/(R1+j*L*w(k));
    gain(k) = abs(H(k));
    phase(k) = angle(H(k))*180/pi;
end

```

```

%-----
%                               Plot the frequency response.
%-----

```

```

subplot(2,1,1), semilogx(w, gain)
xlabel('Frequency, rad/s'), ylabel('Gain, V/V')
title('Frequency Response Plots')
subplot(2,1,2), semilogx(w, phase)
xlabel('Frequency, rad/s'), ylabel('Phase, deg')

```

Here are the plots produced by MATLAB:

