

# EE 221 Practice Problems for the Final Exam

1. The network function of a circuit is

$$\mathbf{H}(\omega) = \frac{-12.5}{1 + j\frac{\omega}{500}}$$

This table records frequency response data for this circuit. Fill in the blanks in the table:

$\omega$ , rad/s	$A$ , V	$\theta$ , °
0	12.5	180
100	12.26	<u>168.7</u>
200	<u>11.61</u>	158.2
500	8.84	135
1000	5.59	116.6

2. The network function of a circuit is

$$\mathbf{H}(\omega) = \frac{-k}{1 + j\frac{\omega}{p}}$$


This table records frequency response data for this circuit. Determine the values of  $p$  and  $k$ :

$$p = \underline{500} \text{ rad/s} \quad \text{and} \quad k = \underline{12.5} \text{ V/V}$$

$\omega$ , rad/s	$A$ , V	$\theta$ , °
0	12.5	180
100	12.26	168.7
200	11.61	158.2
500	8.84	135
1000	5.59	116.6

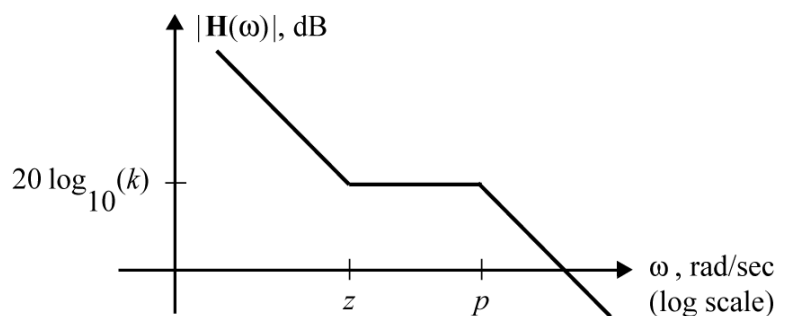3. Here's a network function and corresponding magnitude Bode plot:



$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{50 + \frac{1600}{j\omega}}{640 + j4\omega}$$



Determine the values of the constants  $k$ ,  $z$  and  $p$  used to label the Bode plot:

$$k = \underline{0.078125}, \quad z = \underline{32} \text{ rad/s} \quad \text{and} \quad p = \underline{160} \text{ rad/s.}$$

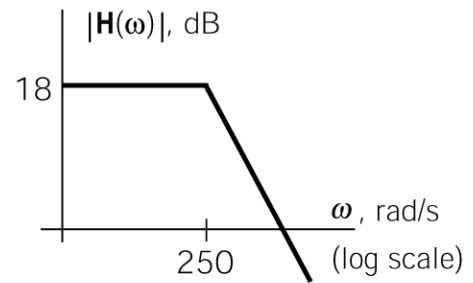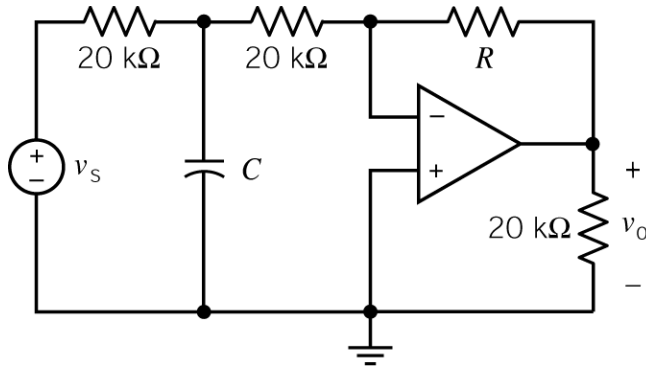
4. Here's a circuit and corresponding Bode plot. The network function of this circuit is  $\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)}$ .



Determine the values of the resistance,  $R$  and capacitance,  $C$  :

$$R = \underline{320} \text{ k}\Omega \quad \text{and} \quad C = \underline{0.4} \text{ }\mu\text{F}$$

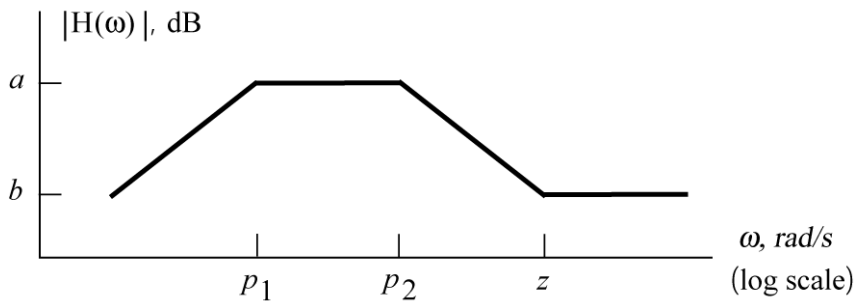5. Here's a magnitude Bode plot and corresponding network function:





$$\mathbf{H}(\omega) = \frac{j\frac{\omega}{4} \left(100 + j\frac{\omega}{4}\right)}{\left(1 + j\frac{\omega}{4}\right) \left(5 + j\frac{\omega}{8}\right)}$$

Determine the values of the constants  $a$ ,  $b$ ,  $p_1$ ,  $p_2$  and  $z$  used to label the Bode plot:

$$a = \underline{26} \text{ dB}, \quad b = \underline{6} \text{ dB}, \quad p_1 = \underline{4} \text{ rad/s}, \quad p_2 = \underline{40} \text{ rad/s} \quad \text{and} \quad z = \underline{400} \text{ rad/s}.$$

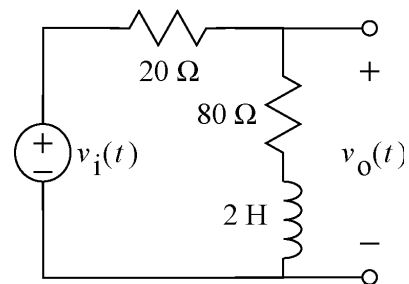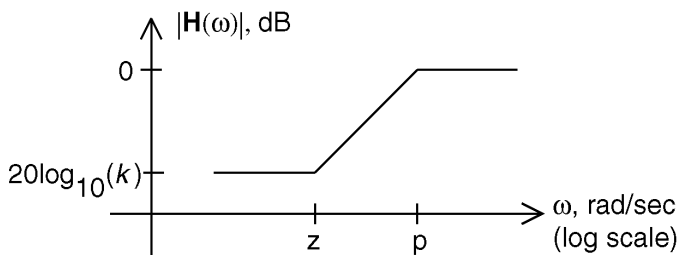6. The input to the circuit is the voltage of the voltage source,  $v_i(t)$ . The output is the voltage  $v_o(t)$ .




$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$  is the network function. The magnitude bode plot that represents this circuit is



The values of the corner frequencies are  $z = \underline{40}$  rad/sec and  $p = \underline{50}$  rad/sec.

The value of the low frequency gain is  $k = \underline{0.8}$  V/V.

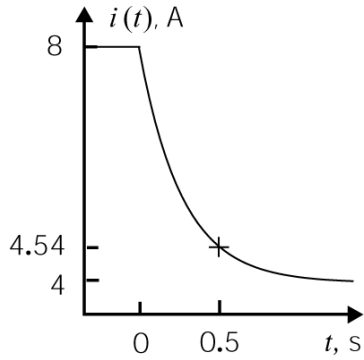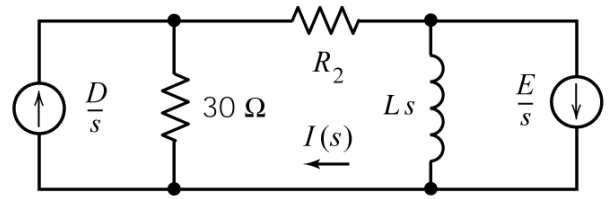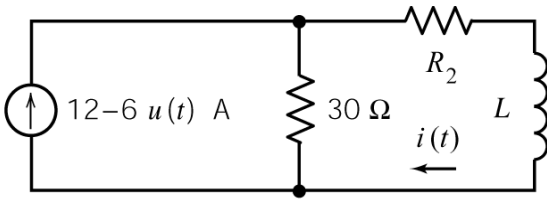7. Here is the same circuit represented in the time domain and also in the complex frequency domain.





Here's a plot of the inductor current. Determine the values of  $D$  and  $E$  used to represent the circuit in the complex frequency domain:

$$D = \underline{6} \text{ V} \quad \text{and} \quad E = \underline{8} \text{ V}$$

Determine the values of the resistance  $R_2$  and the inductance  $L$ :

$$R_2 = \underline{15} \text{ } \Omega \quad \text{and} \quad L = \underline{11.25} \text{ H}$$

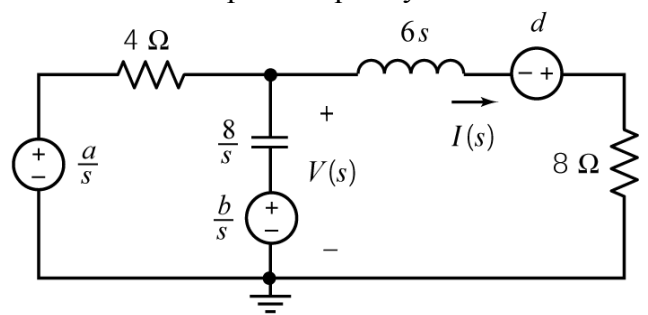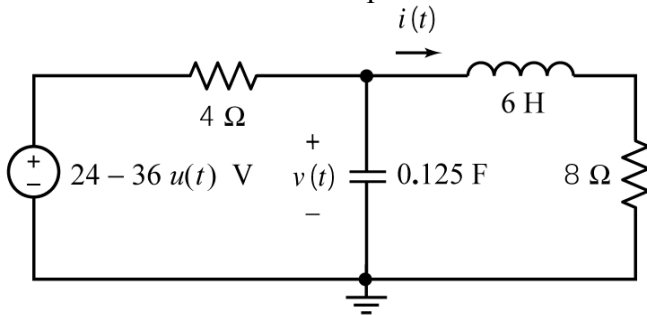8. Here is the same circuit represented in the time domain and also in the complex frequency domain.




Determine the values of  $a$ ,  $b$  and  $d$  used to represent the circuit in the complex frequency domain:

$$a = \underline{-12} \quad b = \underline{16} \quad \text{and} \quad d = \underline{12}$$

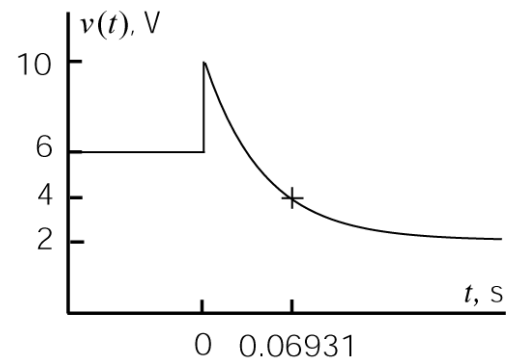9. Given that  $\mathcal{L}[v(t)] = \frac{as+b}{2s^2+40s}$  where  $v(t)$  is the voltage shown to the right, determine the values of  $a$  and  $b$ .

$$a = \underline{20} \text{ V} \quad \text{and} \quad b = \underline{80} \text{ V}$$




10. The Laplace transform of a voltage  $v(t) = [b e^{-at} \sin(ct)] u(t)$  is  $V(s) = \frac{80}{s^2 + 8s + 25}$ . Determine the values of the constant coefficients  $a$ ,  $b$ , and  $c$ :

$$a = \underline{4} \text{ 1/s}, \quad b = \underline{26.67} \text{ V}, \quad \text{and} \quad c = \underline{3} \text{ V}.$$

11. The Laplace transform of a voltage  $v(t) = [b - e^{-at}(c + dt)] u(t)$  is  $V(s) = \frac{12}{s(s^2 + 8s + 16)}$ . Determine the values of the constant coefficients  $a$ ,  $b$ ,  $c$  and  $d$ :

$$a = \underline{4} \text{ 1/s}, \quad b = \underline{0.75} \text{ V}, \quad c = \underline{0.75} \text{ V} \quad \text{and} \quad d = \underline{3} \text{ V}.$$

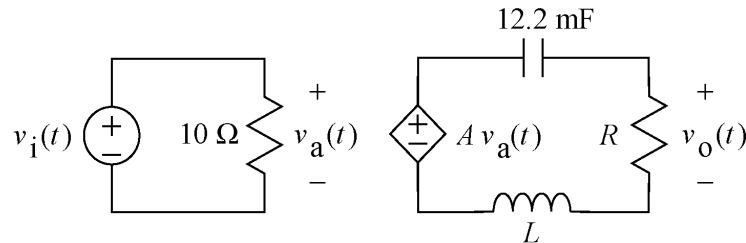12. The input to the circuit is the voltage of the voltage source,  $v_i(t)$ . The output is the voltage  $v_o(t)$ . The step response is  $v_o(t) = 6 e^{-4t} \sin(5t) u(t)$ .




Determine the values of the gain,  $A$ , of the VCVS, the resistance,  $R$ , and the inductance,  $L$ .

$$A = \underline{3.75} \text{ V/V}, \quad R = \underline{16} \text{ } \Omega \quad \text{and} \quad L = \underline{2} \text{ H}.$$

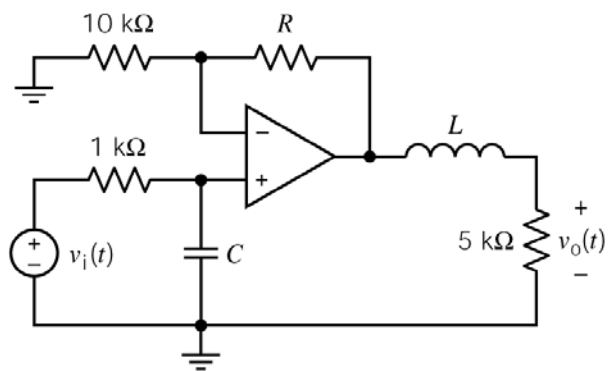13. The input to this circuit is the voltage source voltage,  $v_i(t)$ . The output is the voltage,  $v_o(t)$ . The transfer function of this circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{15 \times 10^6}{(s + 2000)(s + 5000)}$$

Determine the values of  $R$ ,  $L$  and  $C$ :



$$R = \underline{5} \text{ k}\Omega, \quad L = \underline{1} \text{ H} \quad \text{and} \quad C = \underline{0.5} \text{ } \mu\text{F}.$$

or

$$R = \underline{5} \text{ k}\Omega, \quad L = \underline{2.5} \text{ H} \quad \text{and} \quad C = \underline{0.2} \text{ } \mu\text{F}.$$

14. The transfer function of a circuit is  $H(s) = \frac{12}{s^2 + 8s + 16}$ . The step response of this circuit is:  
 $step\ response = [b - e^{-at}(c + dt)]u(t)$ . Determine the values of the constant coefficients  $a$ ,  $b$ ,  $c$  and  $d$ :


$$a = \underline{4} \text{ 1/s}, \quad b = \underline{0.75} \text{ V}, \quad c = \underline{0.75} \text{ V} \quad \text{and} \quad d = \underline{3} \text{ V}.$$

15. The transfer function of a circuit is  $H(s) = \frac{80s}{s^2 + 8s + 25}$ . The step response of this circuit is:  
 $step\ response = [be^{-at} \sin(ct)]u(t)$ . Determine the values of the constant coefficients  $a$ ,  $b$ ,  $c$  and  $d$ :

$$a = \underline{4} \text{ 1/s}, \quad b = \underline{26.67} \text{ V}, \quad \text{and} \quad c = \underline{3} \text{ V}.$$

16. The input to a linear circuit is the voltage,  $v_i$ . The output is the voltage,  $v_o$ . The transfer function of the circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

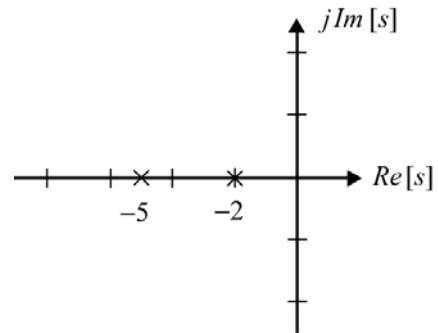

The poles and zeros of  $H(s)$  are shown on this pole-zero diagram. (There are no zeros.) The dc gain of the circuit is


$$\mathbf{H}(0) = 5$$

The step response of the circuit is  $v_o(t) = (a + be^{-5t} - ce^{-2t})u(t)$  V. Determine the values of the constants  $a$ ,  $b$  and  $c$ .

$$a = \underline{5} \text{ V}, \quad b = \underline{10/3} \text{ V} \quad \text{and} \quad c = \underline{25/3} \text{ V}.$$

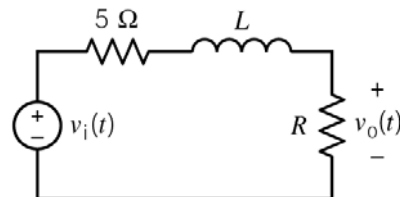17. The input to a circuit is the voltage source voltage,  $v_i$ . The step response of the circuit is

$$v_o(t) = \frac{3}{4}(1 - e^{-100t})u(t) \text{ V}$$



Determine the value of the inductance,  $L$ , and of the resistance,  $R$

$$R = \underline{15} \text{ } \Omega \quad \text{and} \quad L = \underline{0.2} \text{ H}.$$

18. The input to a circuit is the voltage source voltage,  $v_i$ . The step response of the circuit is

$$v_o(t) = 5(1 - (1 + 2t)e^{-2t})u(t) \text{ V}$$

When the input is

$$v_i(t) = 5 \cos(2t + 45^\circ) \text{ V}$$

the steady-state response is

$$v_i(t) = A \cos(2t + \theta) \text{ V}$$

Determine the values of  $A$  and  $\theta$ .

$$A = \underline{12.5} \text{ V} \quad \text{and} \quad \theta = \underline{-45}^\circ.$$


19. The input to a circuit is the voltage  $v_i(t)$ . The output is the voltage  $v_o(t)$ .

When the input is:

$$v_i(t) = 2 + 4 \cos(100t) + 5 \cos(200t + 45^\circ) \text{ V}$$

the corresponding output is:
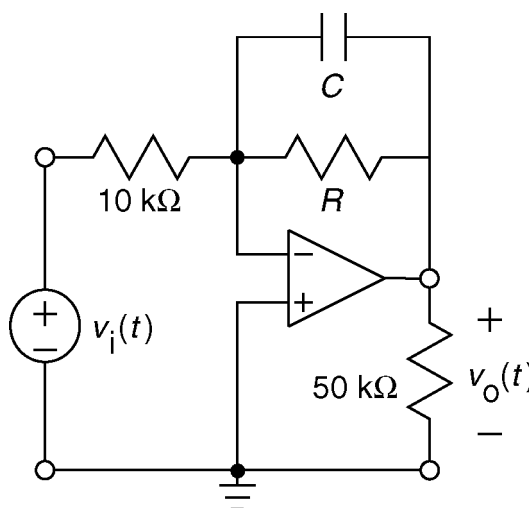
$$v_o(t) = -5 + 7.071 \cos(100t + 135^\circ) + c_2 \cos(200t + \theta_2) \text{ V}$$



Determine the value of  $R$ ,  $C$ ,  $c_2$ , and  $\theta_2$ :

$$R = \underline{25} \text{ k}\Omega, \quad C = \underline{0.4} \text{ }\mu\text{F}, \quad c_2 = \underline{5.59} \text{ V} \quad \text{and} \quad \theta_2 = \underline{161.6}^\circ$$

20. The transfer function of a circuit is  $H(s) = \frac{20}{s+8}$ . When the input to this circuit is sinusoidal, the output is also sinusoidal. Let  $\omega_1$  be the frequency at which the output sinusoid is twice as large as the input sinusoid and let  $\omega_2$  be the frequency at which output sinusoid is delayed by one tenth period with respect to the input sinusoid. Determine the values of  $\omega_1$  and  $\omega_2$ .

$$\omega_1 = \underline{6} \text{ rad/s} \quad \text{and} \quad \omega_2 = \underline{5.8123} \text{ rad/s}$$