

EE 221 Practice Problems for the Final Exam

1. The network function of a circuit is

$$\mathbf{H}(\omega) = \frac{-12.5}{1 + j\frac{\omega}{500}}$$

This table records frequency response data for this circuit. Fill in the blanks in the table:

ω , rad/s	A , V	θ , °
0	12.5	180
100	12.26	_____
200	_____	158.2
500	8.84	135
1000	5.59	116.6

2. The network function of a circuit is

$$\mathbf{H}(\omega) = \frac{-k}{1 + j\frac{\omega}{p}}$$


This table records frequency response data for this circuit. Determine the values of p and k :

$p =$ _____ rad/s and $k =$ _____ V/V

ω , rad/s	A , V	θ , °
0	12.5	180
100	12.26	168.7
200	11.61	158.2
500	8.84	135
1000	5.59	116.6

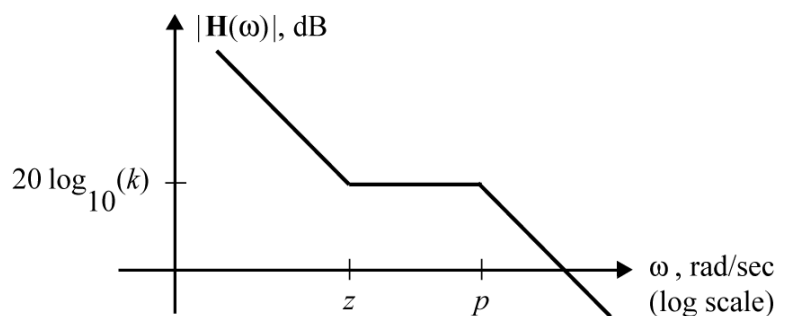3. Here's a network function and corresponding magnitude Bode plot:



$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{50 + \frac{1600}{j\omega}}{640 + j4\omega}$$



Determine the values of the constants k , z and p used to label the Bode plot:

$k =$ _____, $z =$ _____ rad/s and $p =$ _____ rad/s.

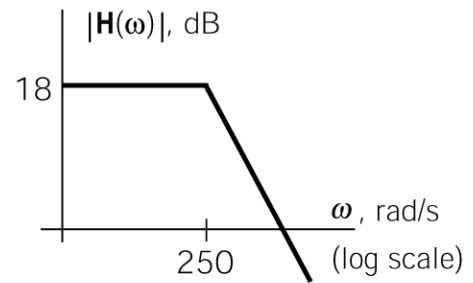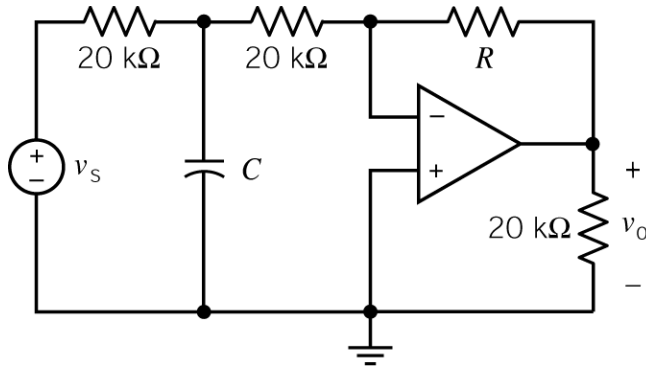
4. Here's a circuit and corresponding Bode plot. The network function of this circuit is $\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)}$.



Determine the values of the resistance, R and capacitance, C :

$$R = \underline{\hspace{2cm}} \text{ k}\Omega \quad \text{and} \quad C = \underline{\hspace{2cm}} \mu\text{F}$$

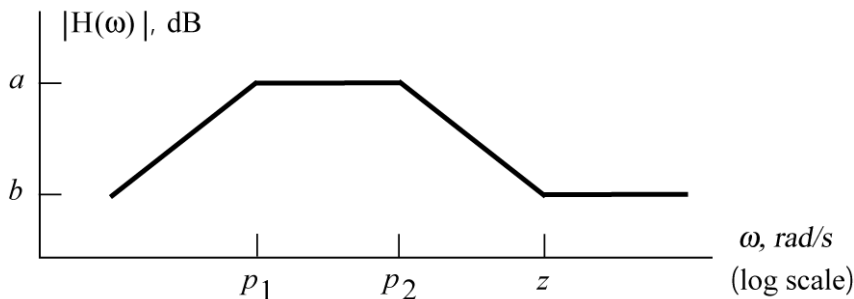5. Here's a magnitude Bode plot and corresponding network function:





$$\mathbf{H}(\omega) = \frac{j\frac{\omega}{4} \left(100 + j\frac{\omega}{4}\right)}{\left(1 + j\frac{\omega}{4}\right) \left(5 + j\frac{\omega}{8}\right)}$$

Determine the values of the constants a , b , p_1 , p_2 and z used to label the Bode plot:

$$a = \underline{\hspace{2cm}} \text{ dB}, \quad b = \underline{\hspace{2cm}} \text{ dB}, \quad p_1 = \underline{\hspace{2cm}} \text{ rad/s}, \quad p_2 = \underline{\hspace{2cm}} \text{ rad/s} \quad \text{and} \quad z = \underline{\hspace{2cm}} \text{ rad/s}.$$

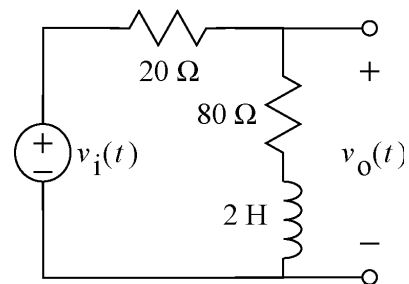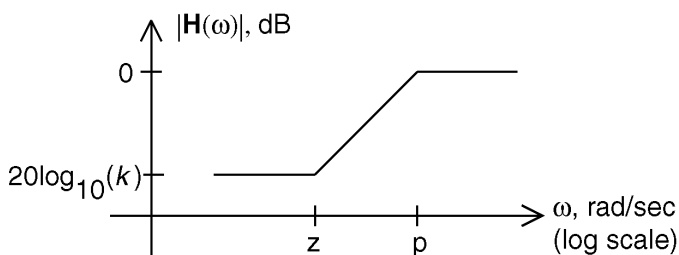6. The input to the circuit is the voltage of the voltage source, $v_i(t)$. The output is the voltage $v_o(t)$.




$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is the network function. The magnitude bode plot that represents this circuit is



The values of the corner frequencies are $z = \underline{\hspace{2cm}}$ rad/sec and $p = \underline{\hspace{2cm}}$ rad/sec.

The value of the low frequency gain is $k = \underline{\hspace{2cm}}$ V/V.

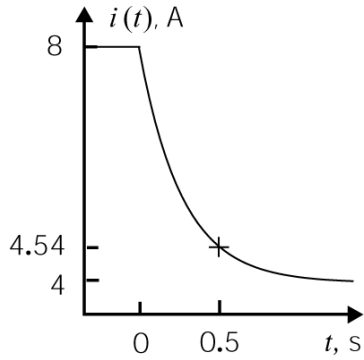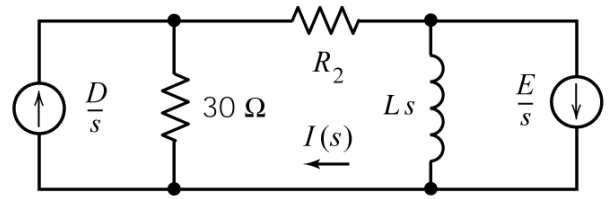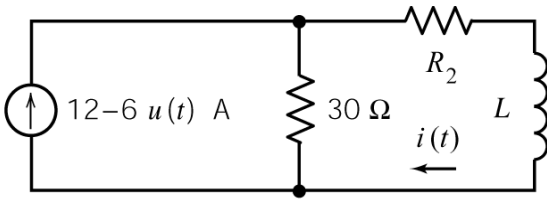7. Here is the same circuit represented in the time domain and also in the complex frequency domain.





Here's a plot of the inductor current. Determine the values of D and E used to represent the circuit in the complex frequency domain:

$$D = \text{_____ V} \quad \text{and} \quad E = \text{_____ V}$$

Determine the values of the resistance R_2 and the inductance L :

$$R_2 = \text{_____ } \Omega \quad \text{and} \quad L = \text{_____ H}$$

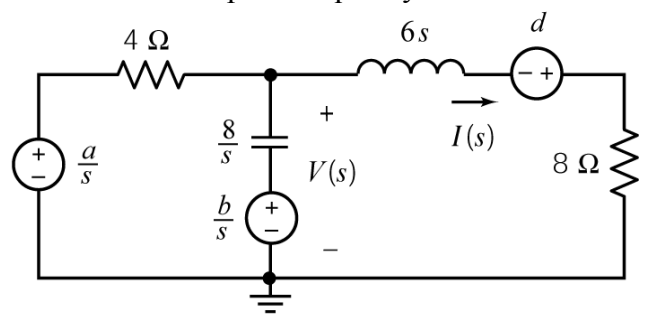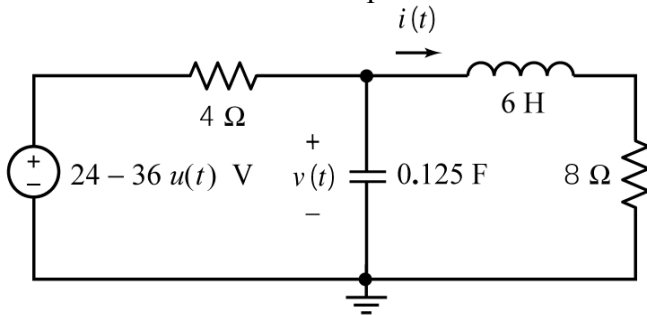8. Here is the same circuit represented in the time domain and also in the complex frequency domain.




Determine the values of a , b and d used to represent the circuit in the complex frequency domain:

$$a = \text{_____} \quad b = \text{_____} \quad \text{and} \quad d = \text{_____}$$

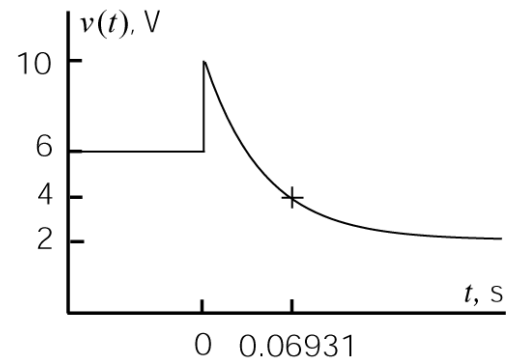9. Given that $\mathcal{L}[v(t)] = \frac{as+b}{2s^2+40s}$ where $v(t)$ is the voltage shown to the right, determine the values of a and b .

$$a = \text{_____ V} \quad \text{and} \quad b = \text{_____ V}$$




10. The Laplace transform of a voltage $v(t) = [b e^{-at} \sin(ct)]u(t)$ is $V(s) = \frac{80}{s^2 + 8s + 25}$. Determine the values of the constant coefficients a , b , and c :

$$a = \underline{\hspace{2cm}} \text{ 1/s, } b = \underline{\hspace{2cm}} \text{ V, } \text{ and } c = \underline{\hspace{2cm}} \text{ V.}$$

11. The Laplace transform of a voltage $v(t) = [b - e^{-at}(c + dt)]u(t)$ is $V(s) = \frac{12}{s(s^2 + 8s + 16)}$. Determine the values of the constant coefficients a , b , c and d :

$$a = \underline{\hspace{2cm}} \text{ 1/s, } b = \underline{\hspace{2cm}} \text{ V, } c = \underline{\hspace{2cm}} \text{ V } \text{ and } d = \underline{\hspace{2cm}} \text{ V.}$$

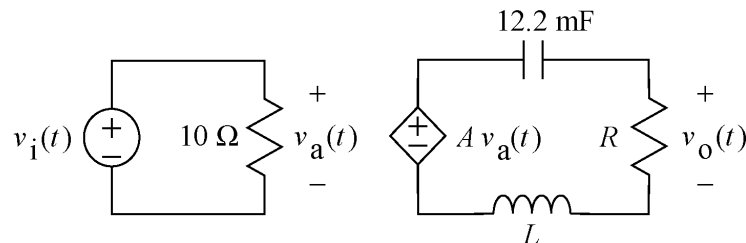12. The input to the circuit is the voltage of the voltage source, $v_i(t)$. The output is the voltage $v_o(t)$. The step response is $v_o(t) = 6e^{-4t} \sin(5t)u(t)$.




Determine the values of the gain, A , of the VCVS, the resistance, R , and the inductance, L .

$$A = \underline{\hspace{2cm}} \text{ V/V, } R = \underline{\hspace{2cm}} \text{ } \Omega \text{ and } L = \underline{\hspace{2cm}} \text{ H.}$$

13. The input to this circuit is the voltage source voltage, $v_i(t)$. The output is the voltage, $v_o(t)$. The transfer function of this circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{15 \times 10^6}{(s + 2000)(s + 5000)}$$

Determine the values of R , L and C :

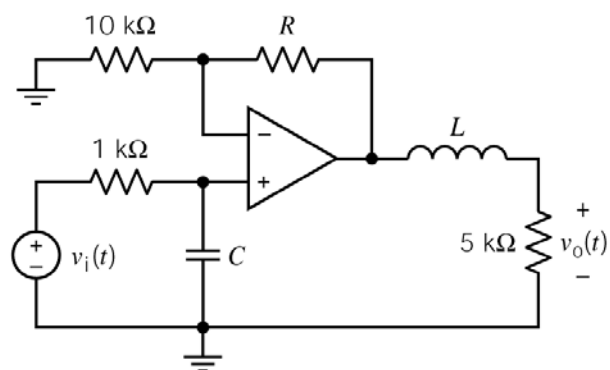

$$R = \underline{\hspace{2cm}} \text{ k}\Omega, L = \underline{\hspace{2cm}} \text{ H and } C = \underline{\hspace{2cm}} \text{ } \mu\text{F.}$$

or

$$R = \underline{\hspace{2cm}} \text{ k}\Omega, L = \underline{\hspace{2cm}} \text{ H and } C = \underline{\hspace{2cm}} \text{ } \mu\text{F.}$$

14. The transfer function of a circuit is $H(s) = \frac{12}{s^2 + 8s + 16}$. The step response of this circuit is:
 $step\ response = [b - e^{-at}(c + dt)]u(t)$. Determine the values of the constant coefficients a , b , c and d :


$$a = \underline{\hspace{2cm}} 1/s, \quad b = \underline{\hspace{2cm}} V, \quad c = \underline{\hspace{2cm}} V \quad \text{and} \quad d = \underline{\hspace{2cm}} V.$$

15. The transfer function of a circuit is $H(s) = \frac{80s}{s^2 + 8s + 25}$. The step response of this circuit is:
 $step\ response = [be^{-at} \sin(ct)]u(t)$. Determine the values of the constant coefficients a , b , c and d :

$$a = \underline{\hspace{2cm}} 1/s, \quad b = \underline{\hspace{2cm}} V, \quad \text{and} \quad c = \underline{\hspace{2cm}} V.$$

16. The input to a linear circuit is the voltage, v_i . The output is the voltage, v_o . The transfer function of the circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

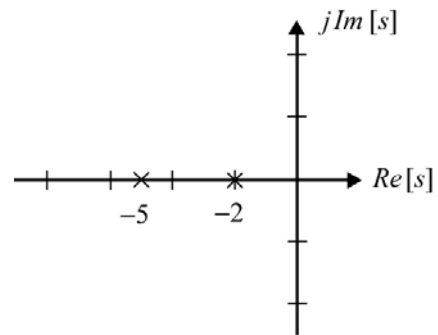

The poles and zeros of $H(s)$ are shown on this pole-zero diagram. (There are no zeros.) The dc gain of the circuit is


$$\mathbf{H(0) = 5}$$

The step response of the circuit is $v_o(t) = (a + be^{-5t} - ce^{-2t})u(t)$ V. Determine the values of the constants a , b and c .

$$a = \underline{\hspace{2cm}} V, \quad b = \underline{\hspace{2cm}} V \quad \text{and} \quad c = \underline{\hspace{2cm}} V.$$

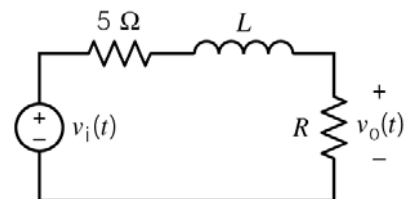17. The input to a circuit is the voltage source voltage, v_i . The step response of the circuit is

$$v_o(t) = \frac{3}{4}(1 - e^{-100t})u(t) \text{ V}$$



Determine the value of the inductance, L , and of the resistance, R

$$R = \underline{\hspace{2cm}} \Omega \quad \text{and} \quad L = \underline{\hspace{2cm}} \text{H}.$$

18. The input to a circuit is the voltage source voltage, v_i . The step response of the circuit is

$$v_o(t) = 5(1 - (1 + 2t)e^{-2t})u(t) \text{ V}$$

When the input is

$$v_i(t) = 5 \cos(2t + 45^\circ) \text{ V}$$

the steady-state response is

$$v_i(t) = A \cos(2t + \theta) \text{ V}$$

Determine the values of A and θ .

$$A = \text{_____ V} \quad \text{and} \quad \theta = \text{_____}^\circ.$$


19. The input to a circuit is the voltage $v_i(t)$. The output is the voltage $v_o(t)$.

When the input is:

$$v_i(t) = 2 + 4 \cos(100t) + 5 \cos(200t + 45^\circ) \text{ V}$$

the corresponding output is:
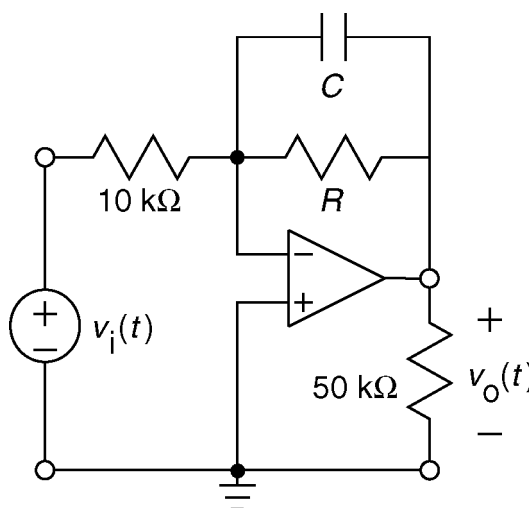
$$v_o(t) = -5 + 7.071 \cos(100t + 135^\circ) + c_2 \cos(200t + \theta_2) \text{ V}$$



Determine the value of R , C , c_2 , and θ_2 :

$$R = \text{_____ k}\Omega, \quad C = \text{_____ }\mu\text{F}, \quad c_2 = \text{_____ V} \quad \text{and} \quad \theta_2 = \text{_____}^\circ$$

20. The transfer function of a circuit is $H(s) = \frac{20}{s+8}$. When the input to this circuit is sinusoidal, the output is also sinusoidal. Let ω_1 be the frequency at which the output sinusoid is twice as large as the input sinusoid and let ω_2 be the frequency at which output sinusoid is delayed by one tenth period with respect to the input sinusoid. Determine the values of ω_1 and ω_2 .

$$\omega_1 = \text{_____ rad/s} \quad \text{and} \quad \omega_2 = \text{_____ rad/s}$$