
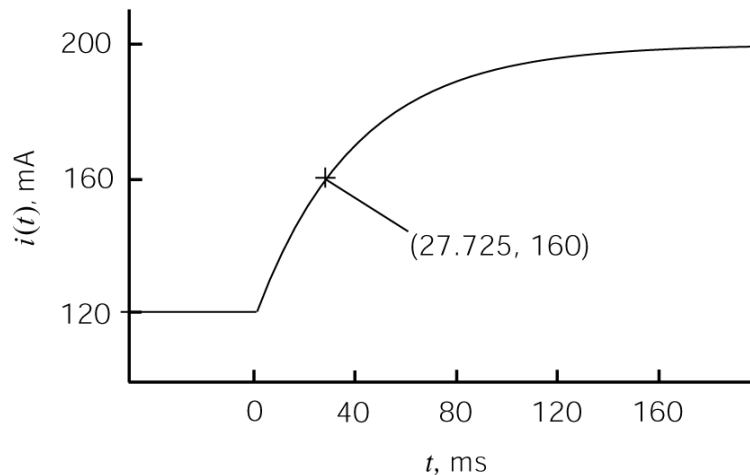


EE221 - Practice for the 1st Midterm Exam

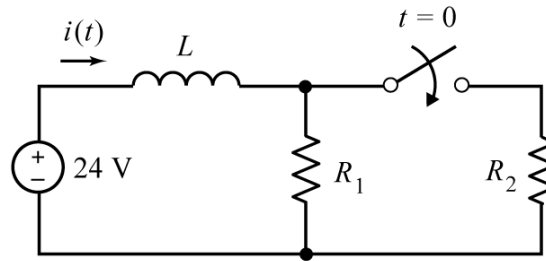1. Consider this circuit and corresponding plot of the inductor current:



Determine the values of L , R_1 and R_2 : $L = \underline{4.8}$ H, $R_1 = \underline{200}$ Ω and $R_2 = \underline{300}$ Ω .

Hint: Use the plot to determine values of D , E , F and a such that the inductor current can be represented as

$$i(t) = \begin{cases} D & \text{for } t \leq 0 \\ E + F e^{-at} & \text{for } t \geq 0 \end{cases}$$

Solution:

From the plot $D = i(t)$ for $t < 0 = 120$ mA = 0.12 A, $E + F = i(0^+) = 120$ mA = 0.12 A and $E = \lim_{t \rightarrow \infty} i(t) = 200$ mA = 0.2 A. The point labeled on the plot indicates that $i(t) = 160$ mA when $t = 27.725$ ms = 0.027725 s. Consequently

$$160 = 200 - 80 e^{-a(0.027725)} \Rightarrow a = \frac{\ln\left(\frac{160-200}{80}\right)}{-0.027725} = 25 \frac{1}{\text{s}}$$

Then

$$i(t) = \begin{cases} 120 \text{ mA} & \text{for } t \leq 0 \\ 200 - 80 e^{-25t} \text{ mA} & \text{for } t \geq 0 \end{cases}$$

When $t < 0$, the circuit is at steady state so the inductor acts like a short circuit.

$$R_1 = \frac{24}{0.12} = 200 \Omega$$



As $t \rightarrow \infty$, the circuit is again at steady state so the inductor acts like a short circuit.

$$R_1 \parallel R_2 = \frac{24}{0.2} = 120 \Omega$$


$$120 = 200 \parallel R_2 \Rightarrow R_2 = 300 \Omega$$

Next, the inductance can be determined using the time constant:

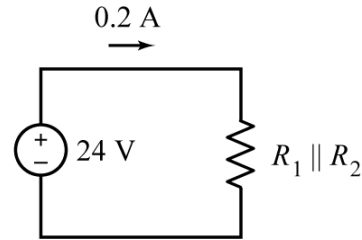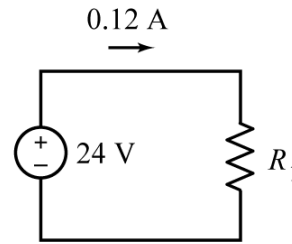
$$25 = a = \frac{1}{\tau} = \frac{R_1 \parallel R_2}{L} = \frac{120}{L} \Rightarrow L = \frac{120}{25} = 4.8 \text{ H}$$



2.

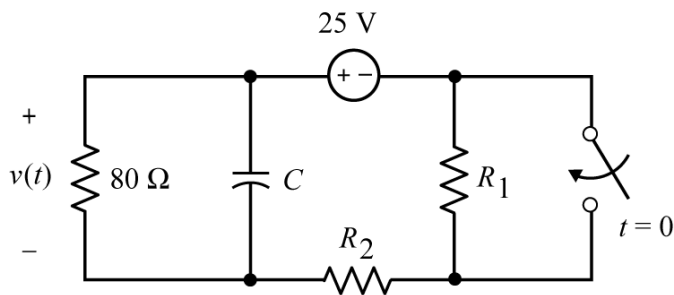

(a)

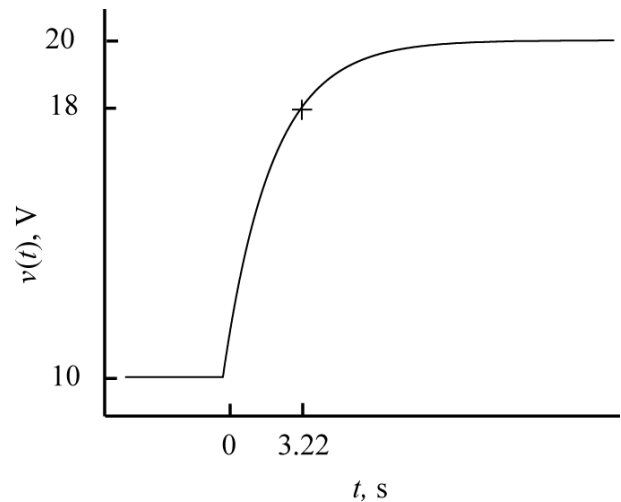

(b)

Design the circuit in (a) to have the response in (b) by specifying the values of C , R_1 and R_2 .

$$C = \underline{\underline{0.125}} \text{ F}, \quad R_1 = \underline{\underline{100}} \Omega \quad \text{and} \quad R_2 = \underline{\underline{20}} \Omega.$$

Solution:

The voltage $v(t)$ is represented by an equation of the form
$$v(t) = \begin{cases} D & \text{for } t < 0 \\ E + F e^{-at} & \text{for } t > 0 \end{cases}$$

where D , E , F and a are unknown constants. The constants D , E and F are described by

$$D = v(t) \text{ when } t < 0, \quad E = \lim_{t \rightarrow \infty} v(t), \quad E + F = \lim_{t \rightarrow 0^+} v(t)$$

From the plot, we see that $D = 10$, $E = 20$, and $E + F = 10 \text{ V}$

Consequently,
$$v(t) = \begin{cases} 10 & \text{for } t < 0 \\ 20 - 10 e^{-at} & \text{for } t > 0 \end{cases}$$

To determine the value of a , we pick a time when the circuit is not at steady state. One such point is labeled on the plot. We see $v(3.22) = 18 \text{ V}$, that is, the value of the voltage is 18 volts at time 3.22 seconds. Substituting these into the equation for $v(t)$ gives

$$18 = 20 - 10e^{-a(3.22)} \Rightarrow a = \frac{\ln(0.2)}{-3.22} = 0.5$$

Consequently

$$v(t) = \begin{cases} 10 & \text{for } t < 0 \\ 20 - 10e^{-0.5t} & \text{for } t > 0 \end{cases}$$




Now let's turn our attention to the circuit. When the circuit is at steady state, the capacitor acts like an open circuit.

After $t = 0$, the switch is closed and the steady state voltage is determined from the plot to be $v(t) = E = 20 \text{ V}$. On the right we see the circuit that results from replacing the capacitor by an open circuit and the switch by a short circuit. Using voltage division gives

$$20 = \frac{80}{80 + R_2}(25) \Rightarrow R_2 = 20 \Omega$$

Before $t = 0$, the switch is open and the steady state voltage is determined from the plot to be $v(t) = E + F = 10 \text{ V}$. On the right we see the circuit that results from replacing the capacitor by an open circuit and the switch by an open circuit. Using voltage division gives
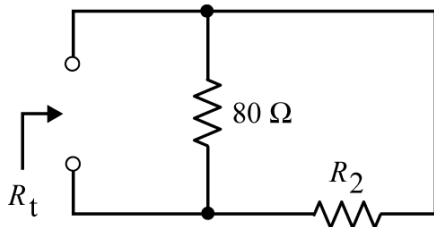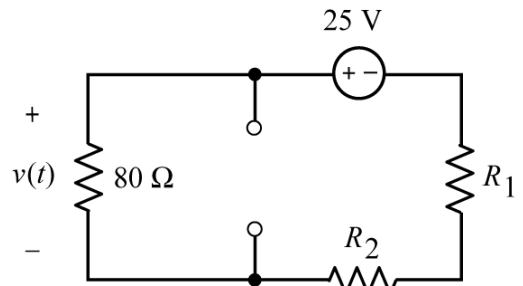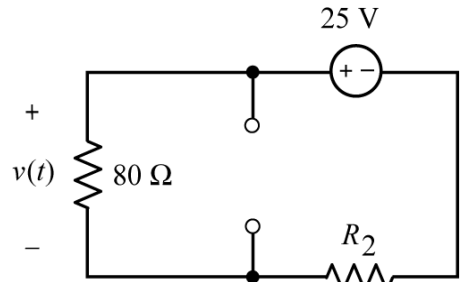
$$10 = \frac{80}{80 + R_1 + R_2}(25) = \frac{80}{100 + R_1}(25) \Rightarrow R_1 = 100 \Omega$$



Recalling that $a = 0.5$ from the plot, consider the time constant


$2 = \frac{1}{a} = \tau = C R_t$. After $t = 0$, the Thevenin resistance of the part of

the circuit connected to the capacitor is

$$R_t = 80 \parallel R_2 = 80 \parallel 20 = 16 \Omega.$$


$$\text{Then } C = \frac{2}{R_t} = \frac{2}{16} = 0.125 \text{ F}.$$

3.

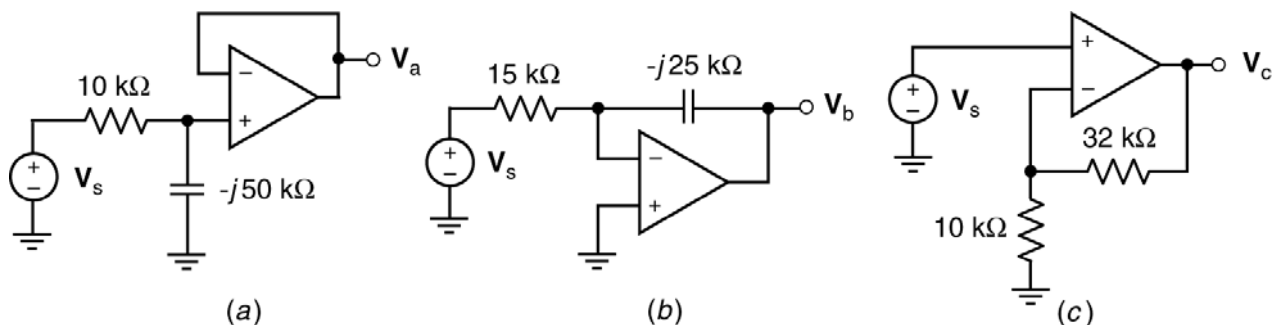

Here are three ac circuits, each represented in the frequency domain. The input to each of these circuits is the phasor voltage $V_s = 2.5 \angle -75^\circ$ V. Let P_a , P_b and P_c denote the average power supplied by the source in circuit (a), (b) and (c) respectively. Determine the values of P_a , P_b and P_c :
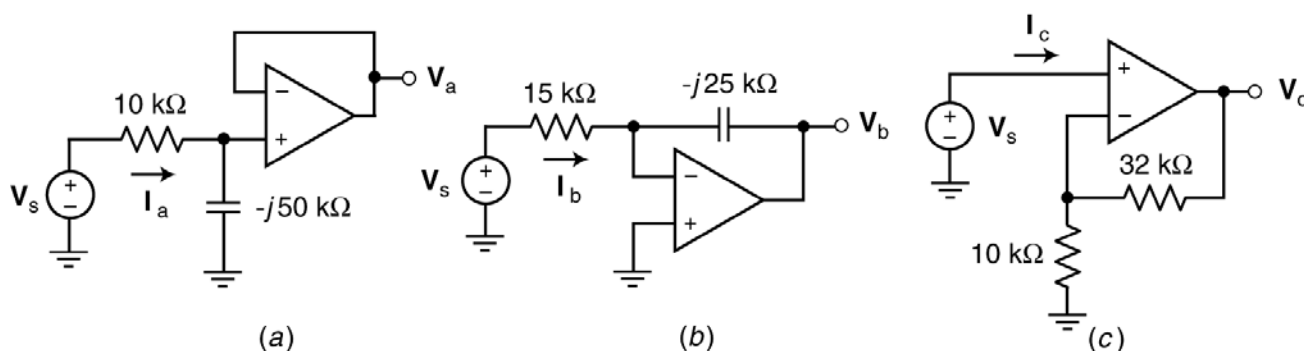
$$P_a = \underline{\underline{0.0120}} \text{ mW}, \quad P_b = \underline{\underline{0.2084}} \text{ mW} \text{ and } P_c = \underline{\underline{0}} \text{ mW}$$



$$I_a = \frac{2.5 \angle -75^\circ}{10 - j50} = \frac{2.5 \angle -75^\circ}{51 \angle -78.7^\circ} = 0.0490 \angle 3.7^\circ \text{ mA} \Rightarrow P_a = \frac{2.5(0.0490)}{2} \cos(-75 - 3.7) = 0.0120 \text{ mW}$$

$$I_b = \frac{2.5 \angle -75^\circ}{15} = 0.1667 \angle -75^\circ \text{ mA} \Rightarrow P_b = \frac{2.5(0.1667)}{2} \cos(-75 - (-75)) = 0.208375 \text{ mW}$$


and

$$I_c = 0 \Rightarrow P_c = 0$$

4. Given that

$$v_i(t) = 24 \cos(3t + 75^\circ) \text{ V}$$

answer the following questions:

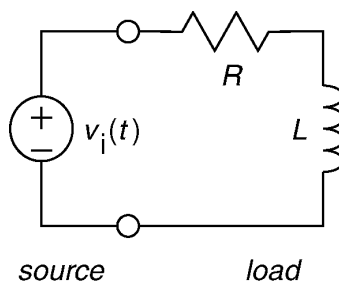

a) Suppose $R = 9 \Omega$ and $L = 5 \text{ H}$. What are the average, complex and reactive powers delivered by the source to the load?

$$P = \underline{\underline{8.47}} \text{ W}, \quad S = \underline{\underline{8.47 + j14.1}} \text{ VA} \text{ and } Q = \underline{\underline{14.1}} \text{ VAR}$$

- b) Suppose the source delivers $8.47 + j 14.12$ VA to the load. What are the values of the resistance, R , and the inductance, L ?


$$R = \underline{9} \ \Omega \text{ and } L = \underline{5} \ \text{H}$$

- c) Suppose the source delivers 14.12 W to the load at a power factor of 0.857 lagging. What are the values of the resistance, R , and the inductance, L ?

$$R = \underline{15} \ \Omega \text{ and } L = \underline{3} \ \text{H}$$

Solution:

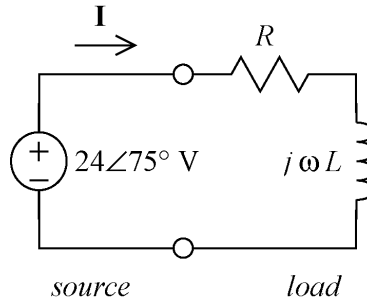Represent the circuit in the frequency domain as



a)
$$\mathbf{I} = \frac{24\angle 75^\circ}{9 + j15} = \frac{24\angle 75^\circ}{17.5\angle 59^\circ} = 1.37\angle 16^\circ \text{ A}$$

$$\mathbf{S} = \frac{1}{2}(24\angle 75^\circ)(1.37\angle 16^\circ)^* = \frac{24(1.37)}{2}\angle (75 - 16)^\circ = 16.44\angle 59^\circ = 8.47 + j14.1 \text{ VA}$$

b)
$$\mathbf{I} = \left(\frac{2(8.47 + j14.12)}{24\angle 75^\circ} \right)^* = \left(\frac{2(16.44\angle 59^\circ)}{24\angle 75^\circ} \right)^* = (1.37\angle -16^\circ)^* = 1.37\angle 16^\circ \text{ A}$$

$$R + j3L = \frac{24\angle 75^\circ}{1.37\angle 16^\circ} = 17.5\angle 59^\circ = 9 + j15 \ \Omega \text{ so } R = 9 \ \Omega \text{ and } L = \frac{15}{3} = 5 \ \text{H}$$

c)
$$pf = 0.857 \text{ lagging} \Rightarrow \begin{cases} 0.857 = \cos(\theta) \\ \text{and } \theta > 0 \end{cases} \text{ so } \theta = 31^\circ.$$

Next
$$14.12 = P = |\mathbf{S}| \cos \theta = |\mathbf{S}|(0.857) \text{ so } |\mathbf{S}| = \frac{14.12}{0.857} = 16.48 \text{ VA}$$


Then
$$\mathbf{S} = 16.48\angle 31^\circ = 14.12 + j8.49 \text{ and } \mathbf{I} = \left(\frac{2\mathbf{S}}{\mathbf{V}} \right)^* = \left[\frac{2(16.48\angle 31^\circ)}{24\angle 75^\circ} \right]^* = 1.37\angle 44^\circ$$

$$R + j3L = \frac{24\angle 75^\circ}{1.37\angle 44^\circ} = 17.5\angle 31^\circ = 15 + j9 \ \Omega \text{ so } R = 15 \ \Omega \text{ and } L = 3 \ \text{H}$$

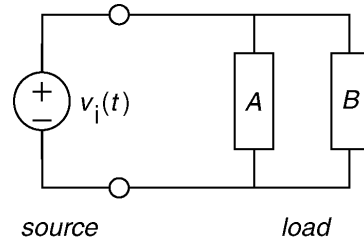5. Given that

$$v_i(t) = 24 \cos(3t + 75^\circ) \text{ V}$$

Determine the impedance of the load and the complex power delivered by the source to the load under each of the following conditions:



a) The source delivers $14.12 + j 8.47$ VA to load A and $8.47 + j 14.12$ VA to load B.

$$\mathbf{Z} = \underline{\quad 9.016 \angle 45^\circ \quad} \Omega, \mathbf{S} = \underline{\quad 22.59 + j22.59 \quad} \text{VA}$$

b) The source delivers $8.47 + j 14.12$ VA to load A and the impedance of load B is $15 + j9 \Omega$.

$$\mathbf{Z} = \underline{\quad 9.016 \angle 45^\circ \quad} \Omega, \mathbf{S} = \underline{\quad 22.59 + j22.59 \quad} \text{VA}$$

c) The source delivers 14.12 W to load A at a power factor of 0.857 lagging and the impedance of load B is $9 + j15 \Omega$.


$$\mathbf{Z} = \underline{\quad 9.016 \angle 45^\circ \quad} \Omega, \mathbf{S} = \underline{\quad 22.59 + j22.59 \quad} \text{VA}$$

d) The impedance of load A is $15 + j9 \Omega$ and the impedance of load B is $9 + j15 \Omega$.

$$\mathbf{Z} = \underline{\quad 9.016 \angle 45^\circ \quad} \Omega, \mathbf{S} = \underline{\quad 22.59 + j22.59 \quad} \text{VA}$$

Solution:

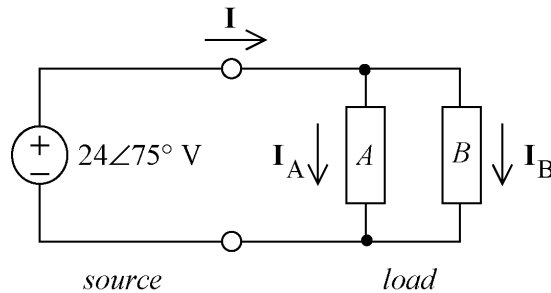Represent the circuit in the frequency domain as



$$(a) \mathbf{I}_A = \left(\frac{2(14.12 + j8.47)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 44^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_B = \left(\frac{2(8.47 + j14.12)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 16^\circ \text{ A}$$

$$\begin{aligned} \mathbf{I} = \mathbf{I}_A + \mathbf{I}_B &= (1.37 \angle 44^\circ) + (1.37 \angle 16^\circ) = (0.986 + j0.954) + (1.319 + j0.377) \\ &= 2.305 + j1.331 = 2.662 \angle 30^\circ \text{ A} \end{aligned}$$

$$\mathbf{Z} = \frac{24 \angle 75^\circ}{2.662 \angle 30^\circ} = 9.016 \angle 45^\circ$$

$$\mathbf{S} = \frac{1}{2} (24 \angle 75^\circ) (2.662 \angle 30^\circ)^* = 31.9 \angle 45^\circ = 22.59 + j22.59 \text{ VA}$$

$$(b) \mathbf{I}_A = \left(\frac{2(8.47 + j14.12)}{24 \angle 75^\circ} \right)^* = 1.37 \angle 16^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_B = \frac{24 \angle 75^\circ}{15 + j9} = 1.37 \angle 44^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662 \angle 30^\circ \text{ A}$$

$$\mathbf{Z} = \frac{24\angle 75^\circ}{2.662\angle 30^\circ} = 9.016\angle 45^\circ \Omega \quad \text{and} \quad \mathbf{S} = 22.59 + j22.59 \text{ VA}$$

(c)
$$\mathbf{P} = 14.12 \text{ W} = \frac{24|\mathbf{I}_A|}{2} \cos(75 - \theta_A)$$

$$\left. \begin{array}{l} 0.857 = \cos(75 - \theta_A) \\ 75 - \theta_A > 0 \end{array} \right\} \Rightarrow \theta_A = 75^\circ - 31^\circ = 44^\circ$$

Then
$$|\mathbf{I}_A| = \frac{2(14.12)}{24 \cos(31^\circ)} = 1.37 \quad \text{so} \quad \mathbf{I}_A = 1.37\angle 44^\circ \text{ A}$$

Also
$$\mathbf{I}_B = \frac{24\angle 75^\circ}{9 + j15} = 137\angle 16^\circ \text{ A} \quad \text{so} \quad \mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662\angle 30^\circ \text{ A}$$

$$\mathbf{Z} = \frac{24\angle 75^\circ}{2.662\angle 30^\circ} = 9.016\angle 45^\circ \Omega \quad \text{and} \quad \mathbf{S} = 22.59 + j22.59 \text{ VA}$$

(d)
$$\mathbf{I}_A = \frac{24\angle 75^\circ}{15 + j9} = 1.37\angle 44^\circ \quad \text{and} \quad \mathbf{I}_B = \frac{24\angle 75^\circ}{9 + j15} = 1.37\angle 16^\circ \quad \text{then} \quad \mathbf{I} = \mathbf{I}_A + \mathbf{I}_B = 2.662\angle 30^\circ \text{ A}$$

$$\mathbf{Z} = \frac{24\angle 75^\circ}{2.662\angle 30^\circ} = 9.016\angle 45^\circ \Omega \quad \text{and} \quad \mathbf{S} = 22.59 + j22.59 \text{ VA}$$

6. In this circuit an ac source is connected to a load by the line. The load voltage is $\mathbf{V}_L = 120\angle 0^\circ$ Vrms and the load receives 50 W at a power factor of 0.8 lagging. The line current is

$$\mathbf{I} = 0.5208\angle -36.87^\circ \text{ Arms}$$

Determine the RMS value of required source voltage, $v_s(t)$, and the average power supplied by the source, P_s .


$$|\mathbf{V}_s| = \underline{\quad 124.2 \quad} \text{ Vrms} \quad \text{and} \quad P_s = \underline{\quad 52.71 \quad} \text{ W}$$

Using KVL

$$\mathbf{V}_s = 10(0.5208\angle -36.87^\circ) + 120\angle 0^\circ = 124.2 - j3.125 = 124.2\angle -1.45^\circ \text{ Vrms}$$

The complex power delivered by the source is
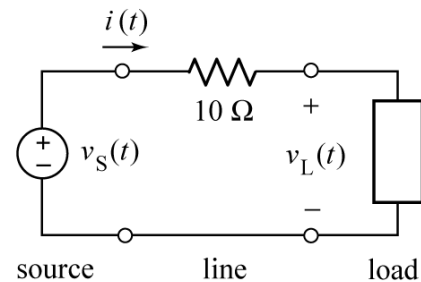
$$\mathbf{S} = (124.2\angle -1.45^\circ)(0.5208\angle -36.87^\circ)^* = 64.68\angle 35.42^\circ = 52.71 + j37.49 \text{ VA}$$



7. In this circuit an ac source is connected to a load by the line. The load voltage is $V_L = 120\angle 0^\circ$ Vrms and the load receives 50 W at a power factor of 0.8 lagging. The line current is

$$\mathbf{I} = B \angle \phi \text{ Arms}$$


Determine the values of B and ϕ .

$$B = \underline{0.5208} \text{ Arms} \text{ and } \phi = \underline{-36.87}^\circ$$

The complex power delivered to the load is

$$S_L = 50 + j \frac{50}{0.8} \sin(\cos^{-1}(0.8)) = 50 + j37.5 = 62.5\angle 36.87^\circ \text{ VA}$$

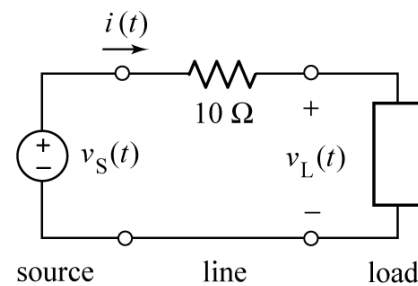The line current is
$$\mathbf{I} = \left(\frac{62.5\angle 36.87^\circ}{120\angle 0^\circ} \right)^* = 0.5208\angle -36.87^\circ \text{ Arms}$$




8. The input to this circuit shown is

$$v_s(t) = 12 \cos(5t) \text{ V}$$

The impedance of the load is $20 + j15 \Omega$.

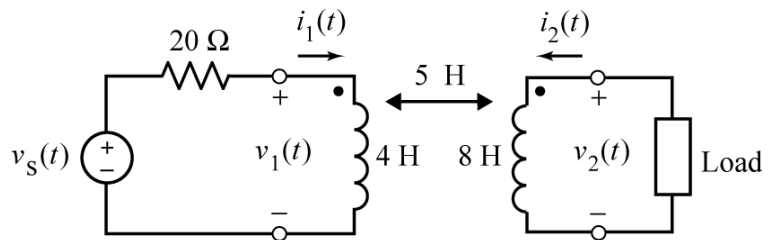Noticing that $i_1(t)$ and $i_2(t)$ are mesh currents, we can represent this circuit by the mesh equations




$$\begin{bmatrix} 20 + ja & jb \\ jc & 20 + jd \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 12\angle 0^\circ \\ 0 \end{bmatrix}$$

where $a, b, c,$ and d are real constants. Determine the values of $a, b, c,$ and d .

$$a = \underline{20} \Omega, \quad b = \underline{25} \Omega, \quad c = \underline{25} \Omega, \quad \text{and} \quad d = \underline{55} \Omega$$

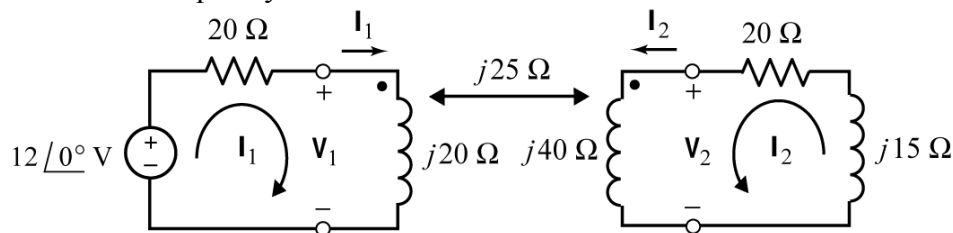Represent the circuit in the frequency domain as



The coil voltages are given by

$$\mathbf{V}_1 = j20\mathbf{I}_1 + j25\mathbf{I}_2 \text{ and } \mathbf{V}_2 = j40\mathbf{I}_2 + j25\mathbf{I}_1$$

Using KVL

$$20\mathbf{I}_1 + \mathbf{V}_1 - 12\angle 45^\circ = 0 \text{ and } 20\mathbf{I}_2 + j15\mathbf{I}_2 + \mathbf{V}_2 = 0$$

Substituting the coil voltages:

$$\begin{aligned} 20\mathbf{I}_1 + j20\mathbf{I}_1 + j25\mathbf{I}_2 &= 12\angle 0^\circ \\ 20\mathbf{I}_2 + j15\mathbf{I}_2 + j40\mathbf{I}_2 + j25\mathbf{I}_1 &= 0 \end{aligned}$$

Solving gives

$$\mathbf{I}_1 = 0.4676\angle -22.8^\circ \text{ A} \text{ and } \mathbf{I}_2 = 0.1998\angle 177.1^\circ \text{ A}$$

9. This circuit consists of a source connected to a load by coupled coils. The input is

$$v_s(t) = 12 \cos(5t) \text{ V}$$

The impedance of the load is $20 + j15 \Omega$.

The mesh currents $i_1(t)$ and $i_2(t)$ are

$$i_1(t) = 0.4676 \cos(5t - 22.8^\circ) \text{ A} \quad \text{and} \quad i_2(t) = 0.1998 \cos(5t + 177.1^\circ) \text{ A}$$

Determine the values of \mathbf{S} , the complex power supplied by the source, \mathbf{S}_c , the complex power received by the coupled inductors and \mathbf{S}_L , the complex power received by the load.

$$\mathbf{S} = \underline{\hspace{2cm}} + j \underline{\hspace{2cm}} \text{ VA}, \quad \mathbf{S}_c = \underline{\hspace{2cm}} + j \underline{\hspace{2cm}} \text{ VA} \quad \text{and} \quad \mathbf{S}_L = \underline{\hspace{2cm}} + j \underline{\hspace{2cm}} \text{ VA}$$

The complex power delivered by the source is

$$\mathbf{S} = \frac{(12 \angle 0^\circ) \mathbf{I}_1^*}{2} = \frac{(12 \angle 0^\circ)(0.4676 \angle -22.8^\circ)^*}{2} = 2.5855 + j1.0893 \text{ VA}$$

The complex power received by the 20Ω resistor is


$$\mathbf{S} = \frac{|\mathbf{I}_1|^2}{2} (20) = \frac{(0.4676)^2}{2} (20) = 2.1865 + j0 \text{ VA}$$

The complex power received by the coupled inductors is

$$\mathbf{S} = \frac{\mathbf{V}_1 \mathbf{I}_1^*}{2} + \frac{\mathbf{V}_2 \mathbf{I}_2^*}{2} = 0 + j0.79 \text{ VA}$$

The complex power received by the load is

$$\mathbf{S} = \frac{|\mathbf{I}_2|^2}{2} (20 + j15) = \frac{(0.1998)^2}{2} (20 + j15) = 0.399 + j0.299 \text{ VA}$$

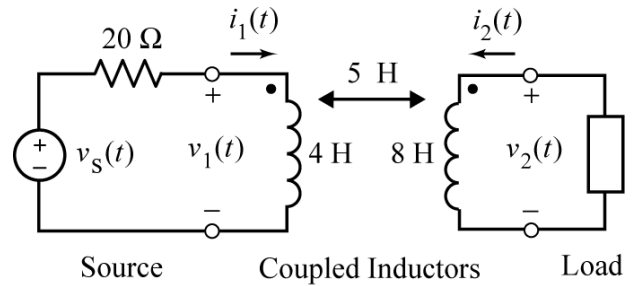


10. Here is a circuit containing coupled coils, represented in the frequency domain. The currents \mathbf{I}_1 and \mathbf{I}_2 are mesh currents. The mesh equations representing this circuit can be expressed as

$$(a + jb) \mathbf{I}_1 + (c + jd) \mathbf{I}_2 = 15 \angle 30^\circ$$

$$(c + jd) \mathbf{I}_1 + (80 + jf) \mathbf{I}_2 = 0$$

where $a + jb$, $c + jd$, and $40 + jf$ represent complex numbers in rectangular form. Determine the following:
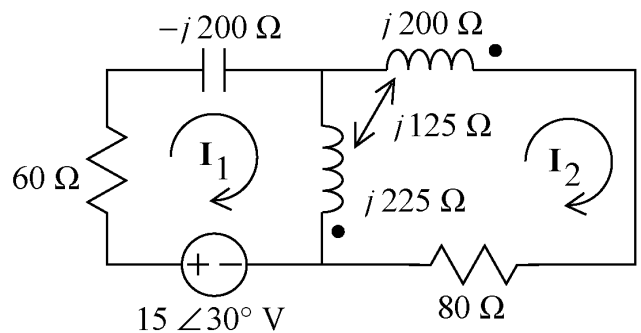
$$a = \underline{60}, \quad b = \underline{25}, \quad c = \underline{0}, \quad d = \underline{-100}, \quad f = \underline{175}$$



Apply KVL to the left mesh to get

$$(-j200)\mathbf{I}_1 + [(j225)(\mathbf{I}_1 - \mathbf{I}_2) + (j125)\mathbf{I}_2] - 15\angle 30^\circ + 60\mathbf{I}_1 = 0$$

$$(60 + j25)\mathbf{I}_1 - (j100)\mathbf{I}_2 = 15\angle 30^\circ$$

Apply KVL to the right mesh to get

$$[(j200)\mathbf{I}_2 + (j125)(\mathbf{I}_1 - \mathbf{I}_2)] + 80\mathbf{I}_2 - [(j225)(\mathbf{I}_1 - \mathbf{I}_2) + (j125)\mathbf{I}_2] = 0$$


$$(-j100)\mathbf{I}_1 + (80 + j175)\mathbf{I}_2 = 0$$

11. The current $i(t)$ and voltage $v(t)$ labeled on the circuit drawing are


$$i(t) = \underline{\underline{0.376}} \cos(3t + 68.4^\circ) \text{ A}$$

and
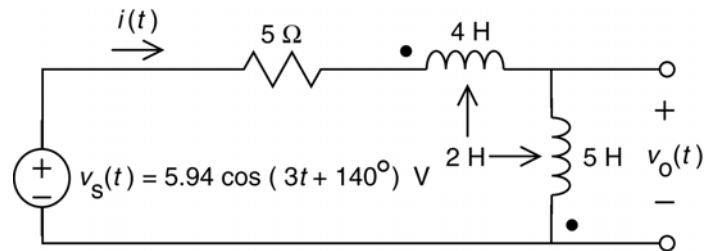
$$v(t) = \underline{\underline{3.38}} \cos(3t + \underline{\underline{158.4}}^\circ) \text{ V}$$



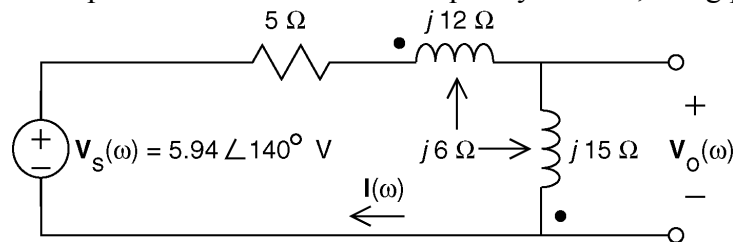Solution: The first step is to represent the circuit in the frequency domain, using phasors and impedances.



This circuit consists of a single mesh. Notice that the mesh current, $\mathbf{I}(\omega)$, enters the dotted end of the left-hand coil and the undotted end of the right-hand coil. Apply KVL to the mesh to get

$$5\mathbf{I}(\omega) + (j12\mathbf{I}(\omega) - j6\mathbf{I}(\omega)) + (-j6\mathbf{I}(\omega) + j15\mathbf{I}(\omega)) - 5.94\angle 140^\circ = 0$$

$$5\mathbf{I}(\omega) + (j12 - j6 - j6 + j15)\mathbf{I}(\omega) - 5.94\angle 140^\circ = 0$$

$$\mathbf{I}(\omega) = \frac{5.94\angle 140^\circ}{5 + j(12 - 6 - 6 + 15)} = \frac{5.94\angle 140^\circ}{5 + j15} = \frac{5.94\angle 140^\circ}{15.8\angle 71.6^\circ} = 0.376\angle 68.4^\circ \text{ A}$$

Notice that the voltage, $\mathbf{V}_o(\omega)$, across the right-hand coil and the mesh current, $\mathbf{I}(\omega)$, adhere to the passive convention. The voltage across the right-hand coil is given by

$$\mathbf{V}_o(\omega) = j15\mathbf{I}(\omega) - j6\mathbf{I}(\omega) = j9\mathbf{I}(\omega) = j9(0.376\angle 68.4^\circ)$$

$$= (9\angle 90^\circ)(0.376\angle 68.4^\circ) = 3.38\angle 158.4^\circ \text{ V}$$


In the time domain, the output voltage is given by $v_o(t) = 3.38 \cos(3t + 158.4^\circ) \text{ V}$

12. The current $i(t)$ and voltage $v(t)$ labeled on the circuit drawing are

$$i(t) = \underline{1.87} \cos(4t - 51.3^\circ) \text{ A}$$

and
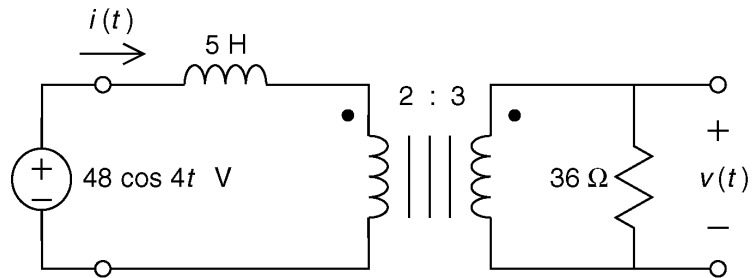
$$v(t) = \underline{45} \cos(4t - \underline{51.3}^\circ) \text{ V}$$




Represent the circuit in the frequency domain. Then

$$\mathbf{I} = \frac{48\angle 0^\circ}{j20 + \left(\frac{2}{3}\right)^2 (36)} = \frac{48\angle 0^\circ}{j20 + 16} = 1.874\angle -51.3^\circ \text{ A}$$

and

$$\mathbf{V} = -\left(\frac{2}{3}\right)(1.874\angle -51.3^\circ)(36) = 44.978\angle -51.3^\circ \text{ V}$$

13.

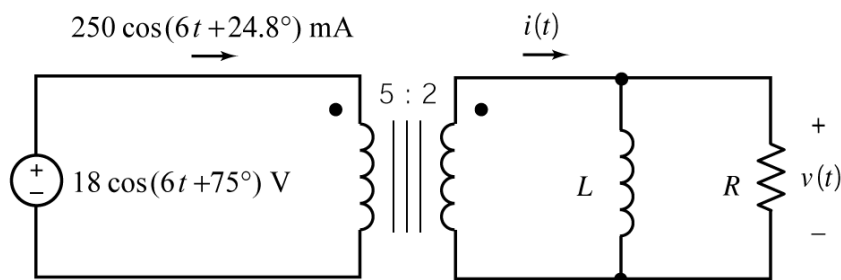

Determine the values of R and L : $R = \underline{18} \Omega$ and $L = \underline{2.5} \text{ H}$

$$\frac{18\angle 75^\circ}{0.250\angle 24.8^\circ} = \left(\frac{5}{2}\right)^2 (R \parallel j6L) \Rightarrow \frac{1}{R} + \frac{1}{j6L} = \frac{1}{\frac{18\angle 75^\circ}{0.250\angle 24.8^\circ} \left(\frac{2}{5}\right)^2} = \left(\frac{5}{2}\right)^2 \left(\frac{0.250\angle 24.8^\circ}{18\angle 75^\circ}\right)$$

$$\frac{1}{R} - \frac{1}{j6L} = \left(\frac{5}{2}\right)^2 \left(\frac{0.250\angle 24.8^\circ}{18\angle 75^\circ}\right) = 0.0868\angle 50.2^\circ = 0.05556 - j0.066687$$


$$R = \frac{1}{0.05556} = 18 \Omega \quad \text{and} \quad 6L = \frac{1}{0.066687} = 15$$

14. This circuit consists of a load connected to a source through an ideal transformer. The input to the circuit is

$$v_s(t) = 12 \cos(20t) \text{ V}$$

Determine the values of the turns ratio, n , and load inductance, L , required for maximum power transfer to the load.
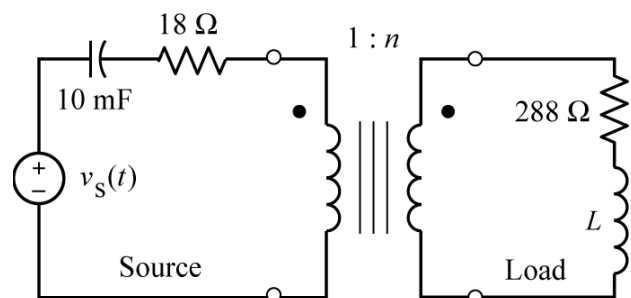
$$n = \underline{4} \quad \text{and} \quad L = \underline{4} \text{ H}$$



$$\text{For maximum power transfer: } \frac{1}{n^2}(288 + j20L) = \left(18 - j\frac{1}{20 \times 0.01}\right)^* = 18 + j5$$

$$\text{Equating real parts gives } n = \sqrt{\frac{288}{18}} = 4. \text{ Equating imaginary parts gives } L = \frac{5(4^2)}{20} = 4 \text{ H}$$

15. This circuit consists of a load connected to a source through an ideal transformer. The input to the circuit is


$$v_s(t) = 12 \cos(20t) \text{ V}$$

The coil voltages and currents are

$$v_1(t) = A \cos(20t + 15.5^\circ) \text{ V},$$

$$v_2(t) = B \cos(20t + 15.5^\circ) \text{ V}$$

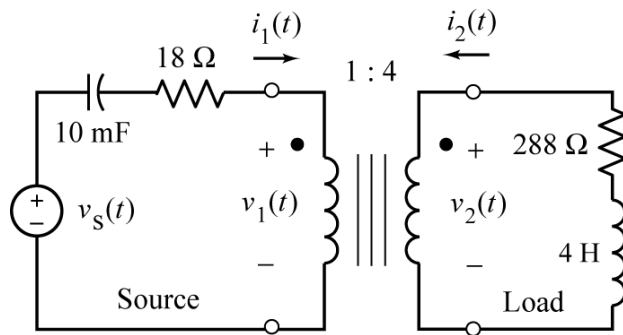
$$i_1(t) = C \cos(20t) \text{ A} \text{ and } i_2(t) = D \cos(20t + 180^\circ) \text{ A}$$



Determine the values of A , B , C and D .


$$A = \underline{\underline{6.227}} \text{ V}, \quad B = \underline{\underline{24.91}} \text{ V}, \quad C = \underline{\underline{0.33}} \text{ A} \text{ and } D = \underline{\underline{0.0833}} \text{ A}$$

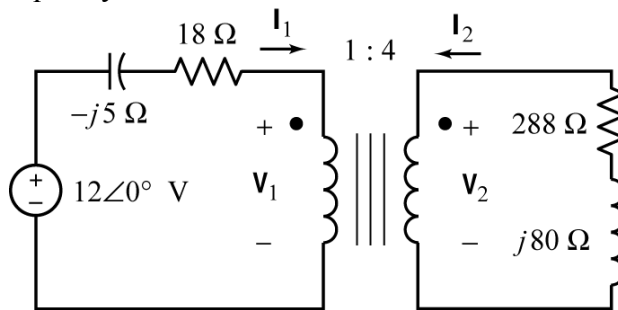Represent the circuit in the frequency domain as



Replace the transformer and load by an equivalent impedance
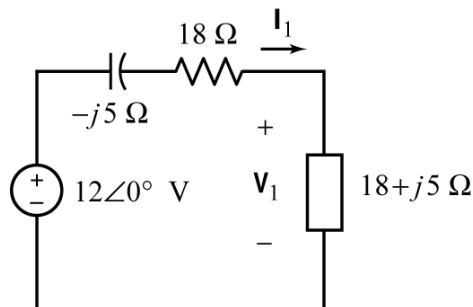
$$Z_{\text{equiv}} = \frac{1}{4^2}(288 + j80) = 18 + j5 \text{ } \Omega$$



$$\mathbf{I}_1 = \frac{12 \angle 0^\circ}{(18 - j5) + (18 + j5)} = \frac{12 \angle 0^\circ}{36} = \frac{1}{3} \angle 0^\circ \text{ A}$$

and
$$\mathbf{V}_1 = (18 + j5)\mathbf{I}_1 = (18 + j5)\left(\frac{1}{3} \angle 0^\circ\right) = 6.227 \angle 15.5^\circ \text{ V}$$

The secondary coil current and voltages

$$\mathbf{I}_2 = -\frac{1}{4}\mathbf{I}_1 = -\frac{1}{4}\left(\frac{1}{3} \angle 0^\circ\right) = -\frac{1}{12} \angle 0^\circ = -0.0833 \angle 0^\circ \text{ A}$$

and
$$\mathbf{V}_2 = \frac{4}{1}\mathbf{V}_1 = 24.91 \angle 15.5^\circ \text{ V}$$


16. This circuit consists of a load connected to a source through an ideal transformer. The input to the circuit is

$$v_s(t) = 12 \cos(20t) \text{ V}$$

The coil voltages and currents are

$$v_1(t) = 6.227 \cos(20t + 15.5^\circ) \text{ V},$$
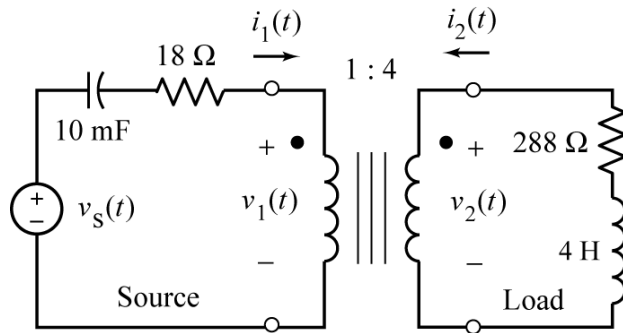
$$v_2(t) = 24.91 \cos(20t + 15.5^\circ) \text{ V}$$



$$i_1(t) = 0.333 \cos(20t) \text{ A} \text{ and } i_2(t) = 0.0833 \cos(20t + 180^\circ) \text{ A}$$

Determine the values of S_p , the complex power received by the primary (left) coil of the transformer and S_L , the complex power received by the load.

$$S_p = \underline{\quad 1 \quad} + j \underline{\quad 0.277 \quad} \text{ VA} \text{ and } S_L = \underline{\quad 1 \quad} + j \underline{\quad 0.277 \quad} \text{ VA}$$

The complex power received by the primary (left) coil of the transformer is

$$\frac{\mathbf{V}_1 \mathbf{I}_1^*}{2} = 1 + j0.277 \text{ VA} = \frac{|\mathbf{I}_1|^2}{2} (18 + j5)$$

The complex power received by the load is

$$-\frac{\mathbf{V}_2 \mathbf{I}_2^*}{2} = 1 + j0.277 \text{ VA} = \frac{|\mathbf{I}_2|^2}{2} (288 + j80)$$

17. The network function of a circuit is $\mathbf{H}(\omega) = -10 \frac{j\omega}{1 + j\frac{\omega}{20}}$. The table below tabulates frequency

response data for this circuit. Fill in the blanks in the table:

ω , rad/s	Gain, V/V	Phase Shift, $^\circ$
10	89.44	<u> -116.6 </u>
40	<u> 178.9 </u>	-153.4

$$\mathbf{H}(10) = -10 \frac{j(10)}{1 + j\frac{10}{20}} = -10 \frac{j(10)}{1 + j0.5} = \frac{100}{\sqrt{1.25}} \angle (-180 + 90 - \tan^{-1}(0.5)) = 89.44 \angle -116.6^\circ$$

$$\mathbf{H}(40) = -10 \frac{j(40)}{1 + j\frac{40}{20}} = -10 \frac{j(40)}{1 + j2} = \frac{400}{\sqrt{5}} \angle (-180 + 90 - \tan^{-1}(2)) = 178.9 \angle -153.4^\circ$$

18. The network function of a circuit is $\mathbf{H}(\omega) = \frac{k}{1 + j\frac{\omega}{p}}$. The table below tabulates frequency response data for this circuit.

ω , rad/s	Gain, V/V	Phase Shift, °
10	17.18	-17.4
40	11.25	-51.3

Determine the values of p and k : $p = \underline{\quad 32 \quad}$ rad/s and $k = \underline{\quad 18 \quad}$ V/V

$$\frac{k}{1 + j\frac{10}{p}} = \frac{k}{\sqrt{1 + \left(\frac{10}{p}\right)^2}} \angle -\tan^{-1}\left(\frac{10}{p}\right) = 17.18 \angle -17.4^\circ$$

so


$$-\tan^{-1}\left(\frac{10}{p}\right) = -17.4^\circ \Rightarrow \frac{10}{p} = \tan(17.4^\circ) = 0.3134 \Rightarrow p = \frac{10}{0.3134} = 31.9 \text{ rad/s}$$

and

$$\frac{k}{\sqrt{1 + \left(\frac{10}{p}\right)^2}} = \frac{k}{\sqrt{1 + (0.3134)^2}} = \frac{k}{1.048} = 17.18 \Rightarrow k = 18$$

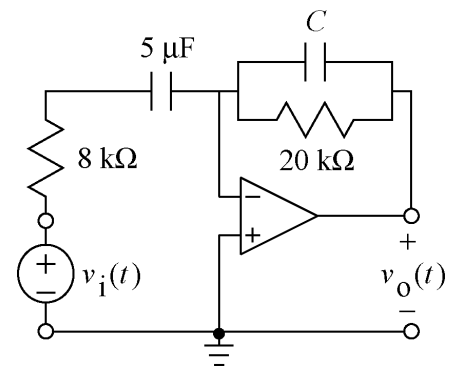
19. The input to the circuit is the voltage of the voltage source, $v_i(t)$. The output is the voltage $v_o(t)$. The network function of this circuit is

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{(-0.1)j\omega}{\left(1 + j\frac{\omega}{p}\right)\left(1 + j\frac{\omega}{125}\right)}$$



Determine the values of the capacitance, C , and the pole, p .
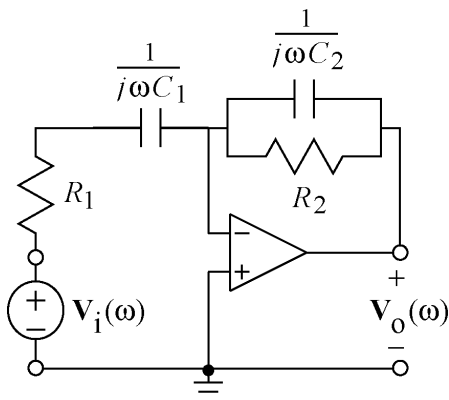
$$C = \underline{\quad 0.4 \quad} \mu\text{F} \text{ and } p = \underline{\quad 25 \quad} \text{rad/s}.$$



$$\begin{aligned} \mathbf{H}(\omega) &= -\frac{R_2 \parallel \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = -\frac{R_2}{\frac{1 + j\omega C_2 R_2}{j\omega C_1 R_1 + 1}} \\ &= \frac{(-C_1 R_2) j\omega}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)} \end{aligned}$$

$$\frac{(-C_1 R_2) j \omega}{(1 + j \omega C_1 R_1)(1 + j \omega C_2 R_2)} = \frac{(-0.1) j \omega}{\left(1 + j \frac{\omega}{p}\right) \left(1 + j \frac{\omega}{125}\right)} \Rightarrow \begin{cases} -C_1 R_2 = -0.1 \\ C_1 R_1 = \frac{1}{p} \text{ or } \frac{1}{125} \\ C_2 R_2 = \frac{1}{125} \text{ or } \frac{1}{p} \end{cases}$$


Since $C_1 = 5 \mu\text{F}$, $R_1 = 8 \text{ k}\Omega$ and $R_2 = 20 \text{ k}\Omega$

$$C_1 R_1 = (5 \times 10^{-6})(8 \times 10^3) = \frac{40}{1000} = \frac{1}{25} \neq \frac{1}{125} \Rightarrow p = 25 \text{ rad/s}$$

$$\frac{1}{125} = C_2 R_2 \Rightarrow C_2 = \frac{1}{125 R_2} = \frac{1}{125(20 \times 10^3)} = 0.4 \times 10^{-6} = 0.4 \mu\text{F}$$

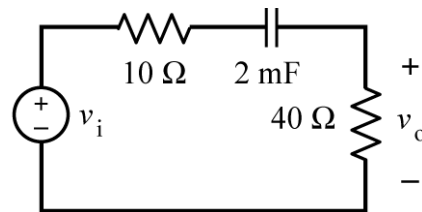20. The network function of this circuit is:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = (k) \frac{j \omega}{1 + j \frac{\omega}{p}}$$



Determine the values of k and p :

$$k = \underline{0.08}, \text{ and } p = \underline{10} \text{ rad/s}.$$


$$\mathbf{V}_o(\omega) = \left(\frac{R_2}{R_1 + R_2 + \frac{1}{j \omega C}} \right) \mathbf{V}_s(\omega) \Rightarrow \mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{R_2}{R_1 + R_2 + \frac{1}{j \omega C}} = \frac{j \omega C R_2}{1 + j \omega C (R_1 + R_2)} = (k) \frac{j \omega}{1 + j \frac{\omega}{p}}$$

Consequently

$$k = C R_2 = (0.002)(40) = 0.08 \text{ s} \quad \text{and} \quad p = \frac{1}{C(R_1 + R_2)} = \frac{1}{(0.002)(10 + 40)} = 10 \text{ rad/s}$$

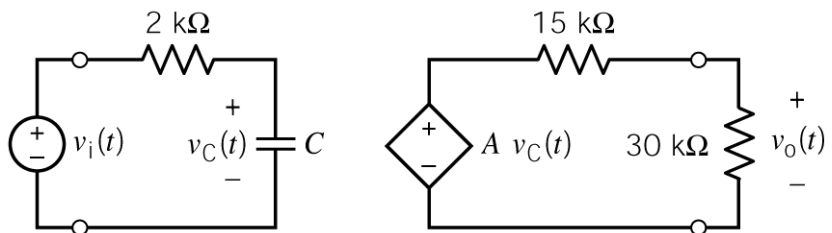21. The input to the circuit is the voltage of the voltage source, $v_i(t)$. The output is the voltage $v_o(t)$. The network function of this circuit is

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{4}{1 + j \frac{\omega}{100}}$$




Determine the values of the capacitance, C , and the VCVS gain, A .

$$C = \underline{5} \mu\text{F} \text{ and } A = \underline{6} \text{ V/V}.$$

In the frequency domain, use voltage division on the left side of the circuit to get:
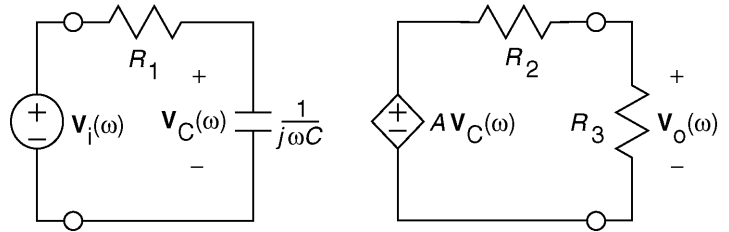
$$V_C(\omega) = \frac{\frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} V_i(\omega) = \frac{1}{1 + j\omega C R_1} V_i(\omega)$$



Next, use voltage division on the right side of the circuit to get:

$$V_o(\omega) = \frac{R_3}{R_2 + R_3} A V_C(\omega) = \frac{2}{3} A V_C(\omega) = \frac{\frac{2}{3} A}{1 + j\omega C R_1} V_i(\omega)$$


Compare the specified network function to the calculated network function:

$$\frac{4}{1 + j\frac{\omega}{100}} = \frac{\frac{2}{3} A}{1 + j\omega C R_1} = \frac{\frac{2}{3} A}{1 + j\omega C 2000} \Rightarrow 4 = \frac{2}{3} A \text{ and } \frac{1}{100} = 2000 C$$

Thus, $C = 5 \mu\text{F}$ and $A = 6 \text{ V/V}$.

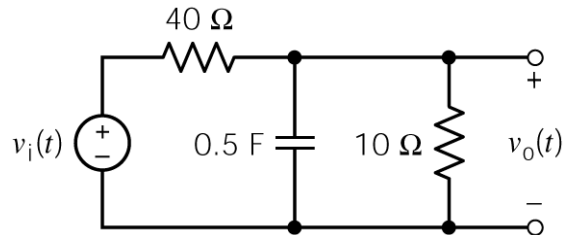22. The network function of this circuit is:

$$\mathbf{H}(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{k}{1 + j\frac{\omega}{p}}$$




Determine the values of k and p :

$$k = \underline{\quad 0.2 \quad}, \text{ and } p = \underline{\quad 0.25 \quad} \text{ rad/s.}$$

Represent the circuit in the frequency domain. It's convenient to calculate:
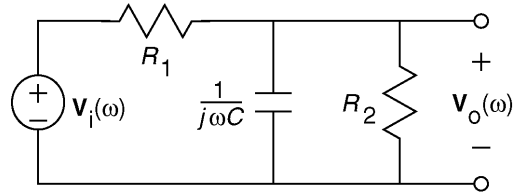
$$R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega C R_2}$$



Then, using voltage division

$$\mathbf{H}(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{\frac{R_2}{1 + j\omega C R_2}}{R_1 + \frac{R_2}{1 + j\omega C R_2}} = \frac{R_2}{R_1 + R_2} \frac{1}{1 + j\omega C R_p}$$

where $R_p = R_1 \parallel R_2$. When $R_1 = 40 \Omega$, $R_2 = 10 \Omega$ and $C = 0.5 \text{ F}$

$$\mathbf{H}(\omega) = \frac{0.2}{1 + j4\omega}$$