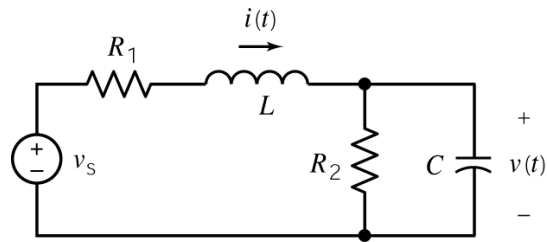


**Example:**

Represent this circuit by a second order differential equation.

**Solution:**

Use KCL to write

$$i(t) = \frac{v(t)}{R_2} + C \frac{d}{dt} v(t)$$

where  $C \frac{d}{dt} v(t)$  is the current directed downward in the capacitor and  $\frac{v(t)}{R_2}$  is the current directed downward in  $R_2$ . Use KVL to write

$$v_s = R_1 i(t) + L \frac{d}{dt} i(t) + v(t)$$

where  $L \frac{d}{dt} i(t)$  is the voltage across the inductor and  $R_1 i(t)$  is the voltage across  $R_1$ .


Substitute to get

$$\begin{aligned} v_s &= \frac{R_1}{R_2} v(t) + R_1 C \frac{d}{dt} v(t) + \frac{L}{R_2} \frac{d}{dt} v(t) + CL \frac{d^2}{dt^2} v(t) + v(t) \\ &= CL \frac{d^2}{dt^2} v(t) + \left( R_1 C + \frac{1}{R_2 C} \right) \frac{d}{dt} v(t) + \frac{R_1 + R_2}{R_2 CL} v(t) \end{aligned}$$

Finally,

$$\frac{v_s}{CL} = \frac{d^2}{dt^2} v(t) + \left( \frac{R_1}{L} + \frac{1}{R_2 C} \right) \frac{d}{dt} v(t) + \frac{R_1 + R_2}{R_2 CL} v(t)$$

**Example:**

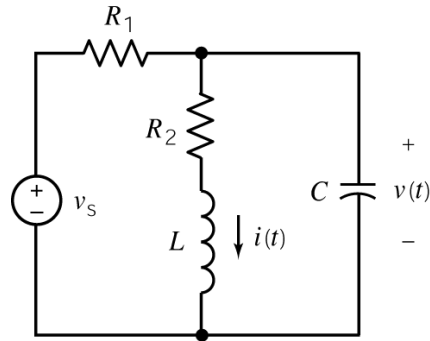

Represent this circuit by a second order differential equation.

**Solution:**

Use KVL to get

$$R_2 i(t) + L \frac{d}{dt} i(t) = v(t)$$

where  $L \frac{d}{dt} i(t)$  is the voltage across the inductor and  $R_2 i(t)$  is the voltage across  $R_2$ . Use KCL and KVL to get

$$v_s = R_1 \left( i(t) + C \frac{d}{dt} v(t) \right) + v(t)$$

where  $C \frac{d}{dt} v(t)$  is the current directed downward in the capacitor and  $i(t) + C \frac{d}{dt} v(t)$  is the current directed to the left in  $R_1$ . Substitute to get


$$\begin{aligned} v_s &= R_1 v(t) + R_1 C R_2 \frac{d}{dt} i(t) + R_1 C \frac{d^2}{dt^2} i(t) + R_2 i(t) + L \frac{d}{dt} i(t) \\ &= R_1 C L \frac{d^2}{dt^2} i(t) + (R_1 R_2 + L) \frac{d}{dt} i(t) + (R_1 + R_2) i(t) \end{aligned}$$

Finally

$$\frac{v_s}{R_1 C L} = \frac{d^2}{dt^2} i(t) + \left( \frac{R_2}{L} + \frac{1}{R_1 C} \right) \frac{d}{dt} i(t) + \frac{R_1 + R_2}{R_1 C L} i(t)$$

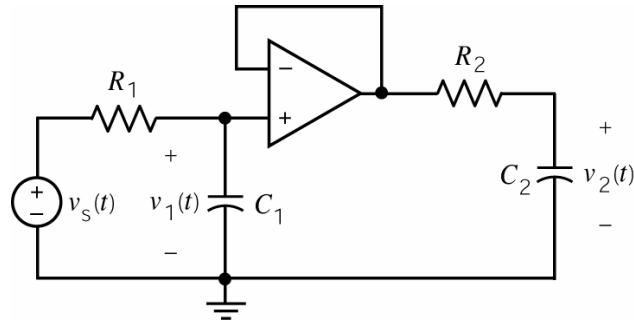**Example:**

The input to the circuit this is the voltage of the voltage source,  $v_s(t)$ . The output is the voltage  $v_2(t)$ .



Derive the second order differential equation that shows how the output of this circuit is related to the input.

**Solution:**

KCL gives

$$\frac{v_s(t) - v_1(t)}{R_1} = C_1 \frac{d}{dt} v_1(t) \quad \Rightarrow \quad v_s(t) = R_1 C_1 \frac{d}{dt} v_1(t) + v_1(t)$$

and

$$\frac{v_1(t) - v_2(t)}{R_2} = C_2 \frac{d}{dt} v_2(t) \quad \Rightarrow \quad v_1(t) = R_2 C_2 \frac{d}{dt} v_2(t) + v_2(t)$$

Substituting gives

$$v_s(t) = R_1 C_1 \frac{d}{dt} \left[ R_2 C_2 \frac{d}{dt} v_2(t) + v_2(t) \right] + R_2 C_2 \frac{d}{dt} v_2(t) + v_2(t)$$

so

$$\frac{1}{R_1 R_2 C_1 C_2} v_s(t) = \frac{d^2}{dt^2} v_2(t) + \left( \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} \right) \frac{d}{dt} v_2(t) + \frac{1}{R_1 R_2 C_1 C_2} v_2(t)$$