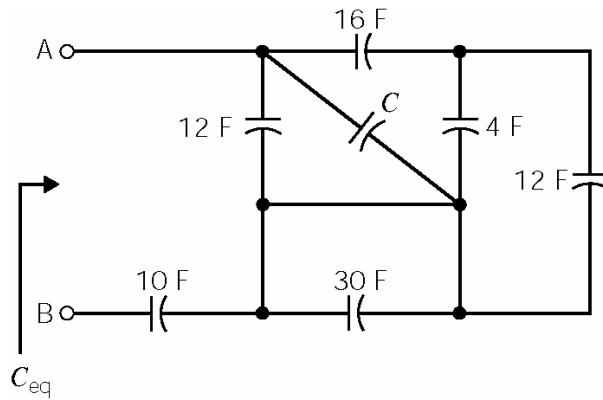


Example:




This circuit is equivalent to a single capacitor having capacitance $C_{eq} = 8 \text{ F}$. Determine the value of the capacitance C

Solution:

The 16 F capacitor is in series with a parallel combination of 4 F and 12 F capacitors. The capacitance of the equivalent capacitor is

$$\frac{16(4+12)}{16+(4+12)} = 8 \text{ F}$$

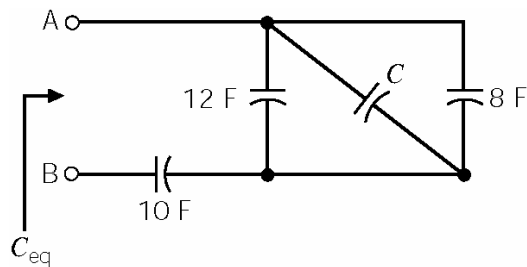The 30 F capacitor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then


$$8 = C_{eq} = \frac{10(12+C+8)}{10+(12+C+8)} \Rightarrow C = 20 \text{ F}$$

Example:


This circuit contains 7 capacitors each having capacitance C . The voltage source voltage is given by

$$v(t) = 4 \cos(3t) \text{ V}$$

Find the current $i(t)$ when $C = 1 \text{ F}$.

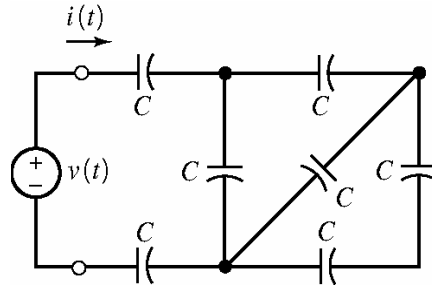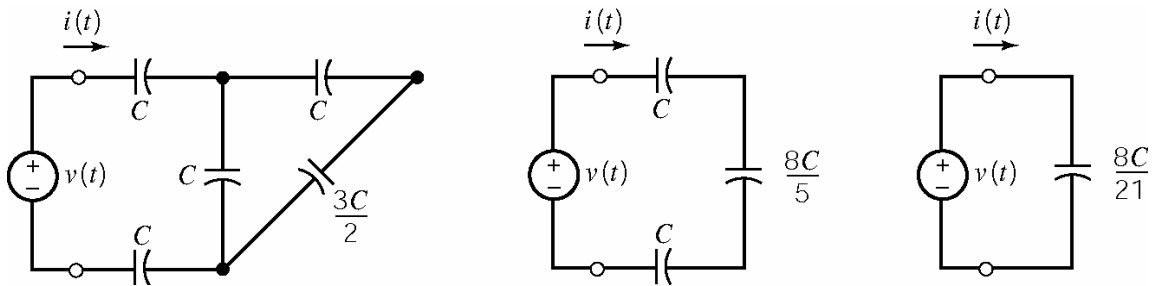**Solution:**

Replacing series and parallel capacitors by equivalent capacitors, the circuit can be reduced as follows:



Then

$$i(t) = \frac{8C}{21} \frac{d}{dt} v(t) = \frac{8C}{21} \frac{d}{dt} 4 \cos(3t) = \frac{8 \times 1}{21} [-12 \sin(3t)] = -\frac{32}{7} \sin(3t) \text{ V}$$