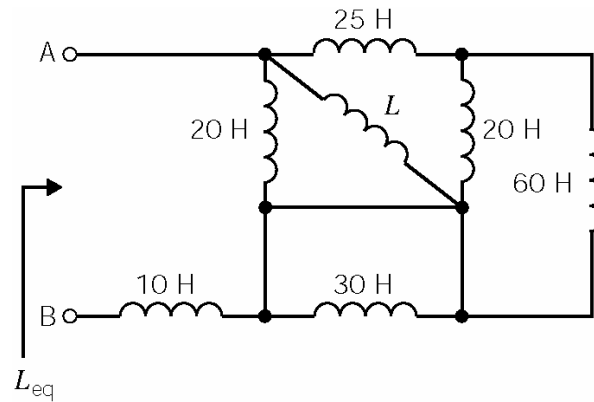


Example:




This circuit is equivalent to a single inductor having inductance $L_{eq} = 18 \text{ H}$. Determine the value of the inductance L .

Solution:

The 25 H inductor is in series with a parallel combination of 20 H and 60 H inductors. The inductance of the equivalent inductor is

$$25 + \frac{60 \times 20}{60 + 20} = 40 \text{ H}$$

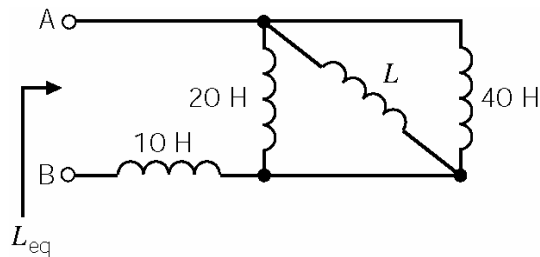
The 30 H inductor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then

$$18 = L_{eq} = 10 + \frac{1}{\frac{1}{20} + \frac{1}{L} + \frac{1}{40}} \Rightarrow \frac{1}{20} + \frac{1}{L} + \frac{1}{40} = \frac{1}{8} \Rightarrow L = 20 \text{ H}$$

Example:

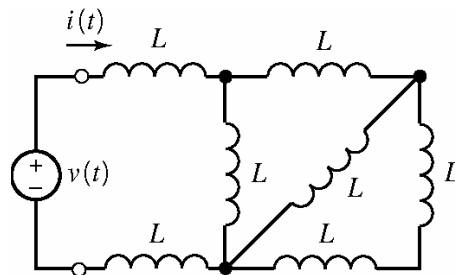

This circuit contains 7 inductors each having inductance L . The voltage source voltage is given by

$$v(t) = 4 \cos(3t) \text{ V}$$

Find the current $i(t)$ when $L = 4 \text{ H}$.

Solution:

The equivalent inductance is:

$$\frac{\left(\frac{L \times 2L}{L + 2L} + L\right) \times L}{\left(\frac{L \times 2L}{L + 2L} + L\right) + L} + 2L = \frac{21}{8}L$$

Then

$$i(t) = \frac{1}{\frac{21}{8}L} \int_{-\infty}^t 4 \cos(3\tau) d\tau = \frac{8}{21 \times 4} \times \frac{4}{3} \sin(3t) = 127 \sin(3t) \text{ mA}$$