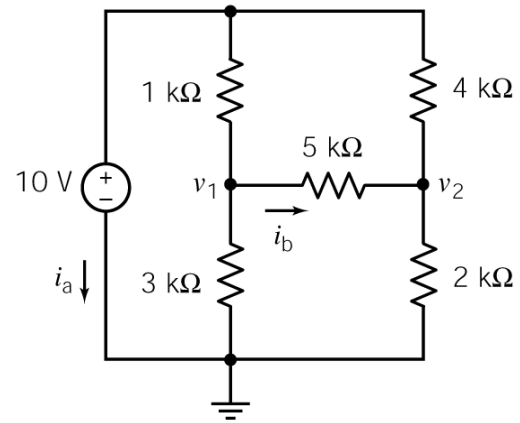


Problem 4.3-7 Determine the values of the node voltages, v_1 and v_2 . Determine the values of the currents i_a and i_b .

Solution Apply KCL at nodes 1 and 2 to get

$$\frac{10-v_1}{1000} = \frac{v_1}{3000} + \frac{v_1-v_2}{5000} \Rightarrow 23v_1 - 3v_2 = 150$$

$$\frac{10-v_2}{4000} + \frac{v_1-v_2}{5000} = \frac{v_2}{2000} \Rightarrow -4v_1 + 19v_2 = 50$$



Solving, e.g. using MATLAB, gives


$$\begin{bmatrix} 23 & -3 \\ -4 & 19 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 150 \\ 50 \end{bmatrix} \Rightarrow v_1 = 7.06 \text{ V and } v_2 = 4.12 \text{ V}$$

Then
$$i_b = \frac{v_1 - v_2}{5000} = \frac{7.06 - 4.12}{5000} = 0.588 \text{ mA}$$

Apply KCL at the top node to get

$$i_a = \frac{v_1 - 10}{1000} + \frac{v_2 - 10}{4000} = \frac{7.06 - 10}{1000} + \frac{4.12 - 10}{4000} = -4.41 \text{ mA}$$

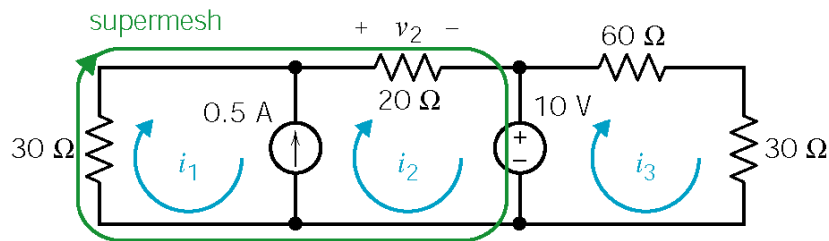Problem 4.6-3 Write and solve mesh equations in order to find v_2 for this circuit



Solution to Problem 4.6-3

Express the current source current as a function of the mesh currents:

$$i_1 - i_2 = -0.5 \Rightarrow i_1 = i_2 - 0.5$$

Apply KVL to the supermesh:

$$30 i_1 + 20 i_2 + 10 = 0 \Rightarrow 30 (i_2 - 0.5) + 20 i_2 = -10$$

$$50 i_2 - 15 = -10 \Rightarrow i_2 = \frac{5}{50} = 0.1 \text{ A}$$

$$i_1 = -0.4 \text{ A and } v_2 = 20 i_2 = \underline{2 \text{ V}}$$