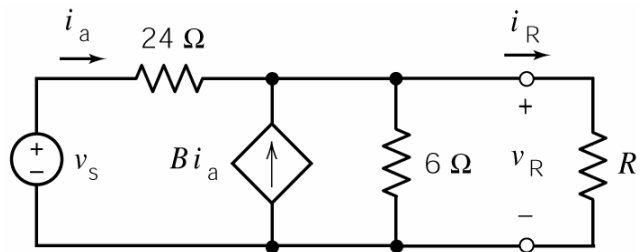


Example 1. Given that $0 \leq R \leq \infty$ in this circuit, consider these two observations:


When $R = 2 \Omega$ then $v_R = 4 \text{ V}$ and $i_R = 2 \text{ A}$.

When $R = 6 \Omega$ then $v_R = 6 \text{ V}$ and $i_R = 1 \text{ A}$.

Determine v_{oc} , i_{sc} and R_t .



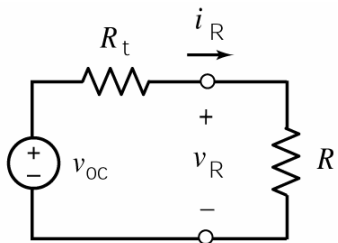Solution: We can replace the part of the circuit to the left of the terminals by its Thevenin equivalent circuit:



Using voltage division $v_R = \frac{R}{R+R_t} v_{oc}$ and using Ohm's law $i_R = \frac{v_{oc}}{R+R_t}$.


Let's substitute the given data into the equation $i_R = \frac{v_{oc}}{R+R_t}$.

When $R = 2 \Omega$ we get $2 = \frac{v_{oc}}{2+R_t} \Rightarrow 4 + 2R_t = v_{oc}$. When $R = 6 \Omega$ we get $1 = \frac{v_{oc}}{6+R_t} \Rightarrow 6 + R_t = v_{oc}$.

So $6 + R_t = 4 + 2R_t \Rightarrow R_t = 2 \Omega$ and $v_{oc} = 4 + 2R_t = 8 \text{ V}$. Also $i_{sc} = \frac{v_{oc}}{R_t} = \frac{8}{2} = 4 \text{ A}$.

Example 2. This circuit has two inputs, v_s and i_s , and one output i_o . The output is related to the inputs by the equation

$$i_o = ai_s + bv_s$$

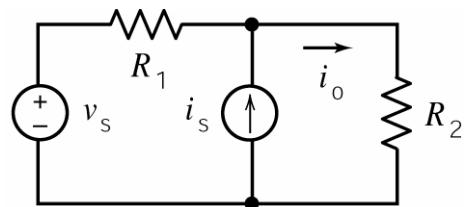

Given the following two facts:

The output is $i_o = 0.45 \text{ A}$ when the inputs are $i_s = 0.25 \text{ A}$ and $v_s = 15 \text{ V}$.

and

The output is $i_o = 0.30 \text{ A}$ when the inputs are $i_s = 0.50 \text{ A}$ and $v_s = 0 \text{ V}$.

Determine the following the values of the constants a and b .

Solution:

From the 1st fact:

$$0.45 = a(0.25) + b(15)$$

From the 2nd fact:

$$0.30 = a(0.50) + b(0) \Rightarrow a = \frac{0.30}{0.50} = 0.60$$

Substituting gives $0.45 = (0.60)(0.25) + b(15) \Rightarrow b = \frac{0.45 - (0.60)(0.25)}{15} = 0.02$