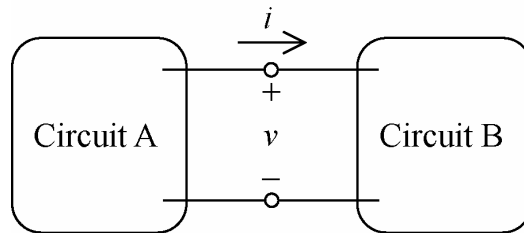


## What is a Thevenin Equivalent Circuit?

Figure 1 shows a circuit that has been separated into two parts, Circuit A and Circuit B. These parts are connected at a single pair of terminals.

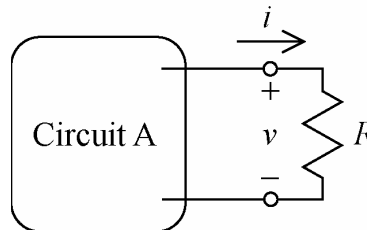


**Figure 1.** Two circuits connected at a pair of terminals.

We'd like to understand the interaction between these two circuits. Circuit A and Circuit B share two things: the current,  $i$ , and the voltage,  $v$ . It seems reasonable to ask

1. Are  $i$  and  $v$  related to each other? If so, how?
2. Does Circuit B affect  $i$  and  $v$ ? How?
3. Suppose we knew  $i$  and  $v$ . What would they tell us about Circuit A?

To start our investigation, let's simplify the problem by considering the case where Circuit B is a single resistor:



**Figure 2.** Circuit B is a resistor.


Let's go to the laboratory and take some data:

$R, \Omega$	1	2	3	4	5	6	8	10	15
$i, A$	0.476	0.455	0.435	0.417	0.400	0.385	0.357	0.333	0.286
$v, V$	0.476	0.909	1.304	1.667	2.000	2.308	2.857	3.333	4.286

$R, \Omega$	20	25	30	40	50	100			
$i, A$	0.250	0.222	0.200	0.167	0.143	0.083			
$v, V$	5.000	5.556	6.000	6.667	7.143	8.333			

(This data was obtained by computer simulation using PSpice [] rather than laboratory measurements. The circuit labeled "Circuit A2" in Figure 10 was used as Circuit A.)

Maybe a picture will help us to see a pattern in this data. Figure 3 shows a graph of  $v$  as a function of  $i$ .

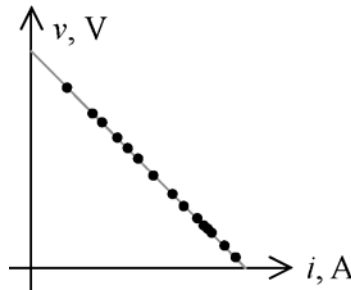

**Figure 3.** A graph of the data.


The data points all lie on a segment of a straight line. That line segment connects two data points that we did not measure, the points on the axes. The point on the  $i$  axis corresponds to  $v = 0$ . To cause  $v = 0$ , we set  $R = 0$  in Figure 2. Similarly, the point on the  $v$  axis corresponds to  $i = 0$  and  $R = \infty$ .

$$i_{sc} = \text{the current when } R = 0 \quad (\text{a short circuit})$$


and

$$v_{oc} = \text{the voltage when } R = \infty \quad (\text{an open circuit})$$

We go back into the lab and measure  $i_{sc}$  and  $v_{oc}$ . Figure 4 illustrates the procedure for making those measurements. For this particular choice of Circuit A, we find  $v_{oc} = 10$  V and  $i_{sc} = 0.5$  A. Figure 5 shows the graph of  $v$  versus  $i$ , updated to show the new data.

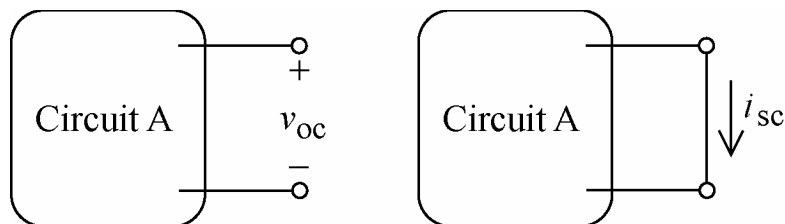

**Figure 4.** The laboratory procedure for measuring  $i_{sc}$  and  $v_{oc}$ .

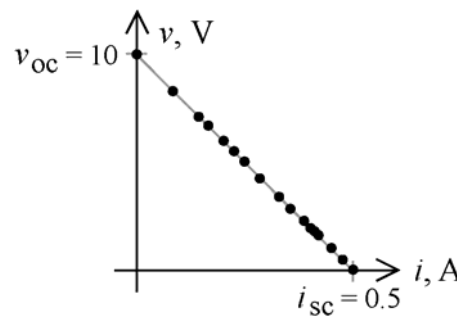

**Figure 5.** The graph of the data after measuring  $i_{sc}$  and  $v_{oc}$ .

The equation of the straight line in Figure 5 is

$$v = mi + b$$

where

$$b = v_{oc} \quad \text{and} \quad m = -\frac{v_{oc}}{i_{sc}}$$

That is

$$v = \left( -\frac{v_{oc}}{i_{sc}} \right) i + v_{oc} = (-20)i + 10$$

Of course we can calculate the slope and intercept, hence  $i_{sc}$  and  $v_{oc}$ , from the coordinates of any two points on the line. For example,  $v = 2$  V when  $i = 0.4$  A and  $v = 5$  V when  $i = 0.25$  A, so

$$m = \frac{2-5}{0.4-0.25} = \frac{-3}{0.15} = -20$$

Thus

$$v = -20i + b$$

Next, using  $v = 2$  V when  $i = 0.4$  A


$$2 = (-20)0.4 + b \Rightarrow b = 10$$

As before,

$$v = -20i + 10$$

To summarize:

1. The plot of  $v$  versus  $i$  in Figure 1 is a straight line. Of course, the plot of  $v$  versus  $i$  in Ohm's law is also a straight line. Figure 6 shows these two straight lines when  $R = 6 \Omega$ .

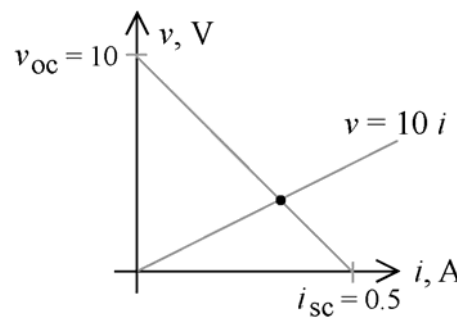


**Figure 6.** Another plot.

2. The intercepts of that straight line are  $i_{sc}$  and  $v_{oc}$ , the short circuit current and the open circuit voltage.
3. We can calculate  $i_{sc}$  and  $v_{oc}$  in either of two ways

- a. Replace Circuit B with a resistor. Measure  $v$  and  $i$ . Change the resistance of the resistor. Measure  $v$  and  $i$  again. Do some arithmetic.
- b. Measure  $i_{sc}$  and  $v_{oc}$  as shown in Figure 4.

Replacing Circuit B by a single resistor worked quite well. Let's see try something different. Consider replacing Circuit A in Figure 1 with a simple circuit as shown in Figure 7.

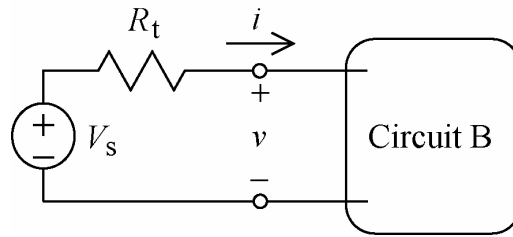


**Figure 7.**

Kirchhoff's voltage law gives

$$R_t i + v - V_s = 0 \Rightarrow v = -R_t i + V_s$$


This is the equation of the straight line shown in Figure 8.

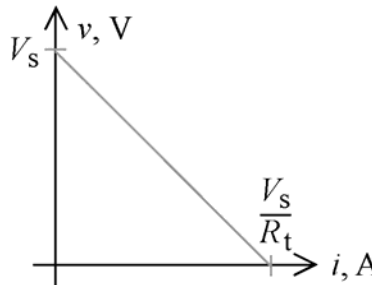

**Figure 8.** KVL for the circuit in Figure 7.


The plot in Figure 7 looks like the plot shown in Figure 3 with  $v_{oc} = V_s$  and  $i_{sc} = \frac{V_s}{R_t}$ . Figure 9

shows ...

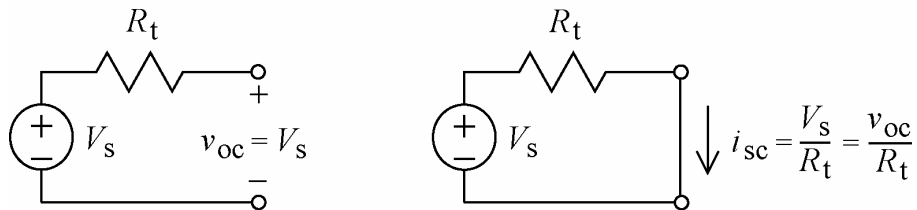

**Figure 9.**

The only characteristics of Circuit A that are important to Circuit B are  $i_{sc}$  and  $v_{oc}$ . For example, Circuits A1 and A2 shown in Figure 10 both have  $i_{sc} = 0.6$  A and  $v_{oc} = 12$  V so Circuit B would not be able to distinguish between these circuits.

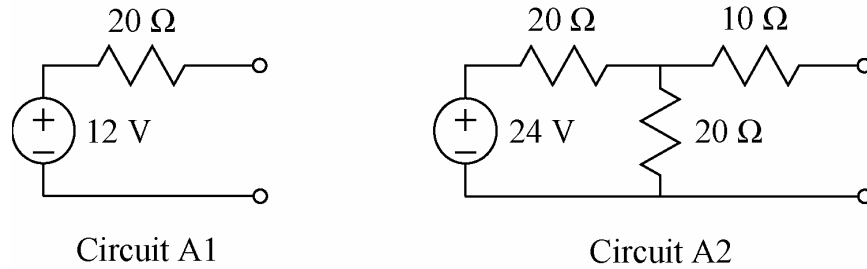

**Figure 10.** Two circuit with the same values of  $i_{sc}$  and  $v_{oc}$ .