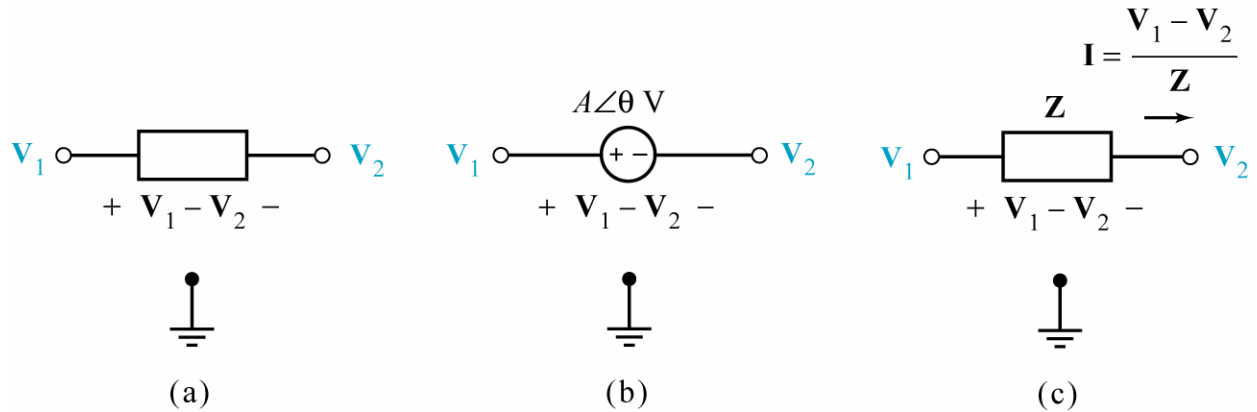
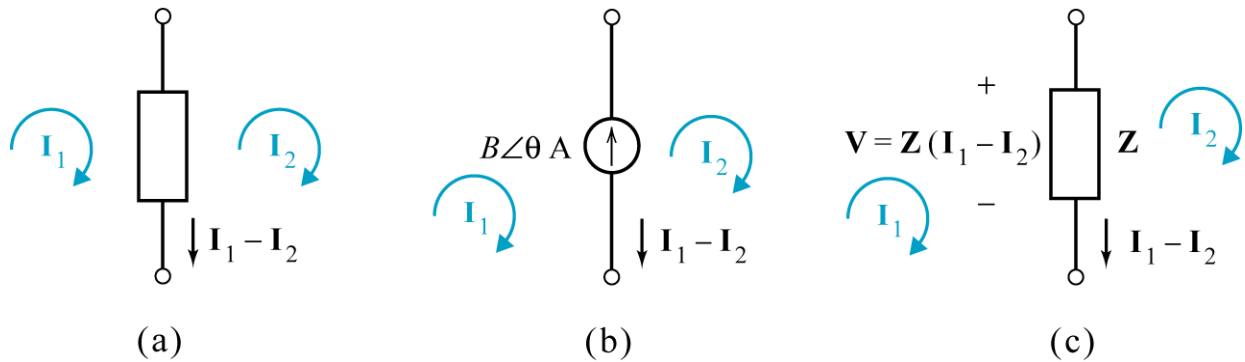


“Express everything ...” in the Frequency Domain



We can express the (a) element voltage, (b) source voltage or (c) current and/or voltage of an impedance in terms of node voltages.



We can express the (a) element current, (b) source current or (c) current and/or voltage of an impedance in terms of mesh currents.