

1. Kirchhoff's Laws

Introduction

The circuits in this problem set are comprised of unspecified circuit elements. (We don't know if a particular circuit element is a resistor or a voltage source or something else.) The current and voltage of each circuit element is labeled, sometimes as a value and sometimes as a variable. Some of these problems ask that we determine the value of a particular voltage or current. Other problems ask for the values of the power supplied or received by a particular circuit element. Kirchhoff's laws are used to determine values of currents or voltages. The passive convention is used to decide if the product of a particular element current and voltage is the power supplied or received by the circuit element.

The passive convention is discussed in Section 1.5 of *Introduction to Electric Circuits* (7e) by R. C. Dorf and J. A. Svoboda and summarized in Table 1.5-1. Kirchhoff's laws are discussed in Section 3.2 of *Introduction to Electric Circuits*.

Worked Examples

Example 1:

Consider the circuit shown in Figure 1. Determine the power supplied by element D and the power received by element F .

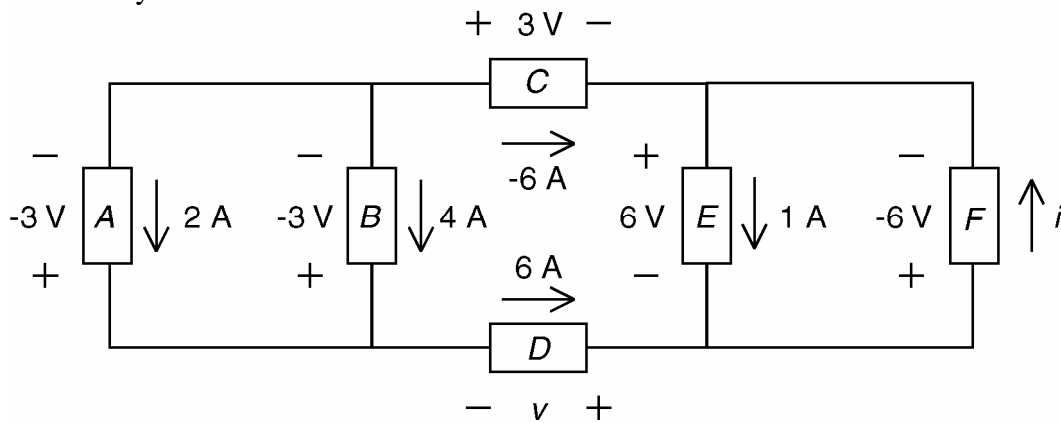


Figure 1. The circuit considered in Example 1

Solution: Figure 1 provides a value for the current in element D but not for the voltage, v , across element D . The voltage and current of element D given in Figure 1 do not adhere to the passive convention so the product of this voltage and current is the power *supplied* by element D . Similarly, Figure 1 provides a value for the voltage across element F but not for the current, i , in element F . The voltage and current of element F given in Figure 1 do adhere to the passive convention so the product of this voltage and current is the power *received* by element F .

We need to determine the voltage, v , across element D and the current, i , in element F . We will use Kirchhoff's laws to determine values of v and i . First, we identify and label the nodes of the circuit as shown in Figure 2.

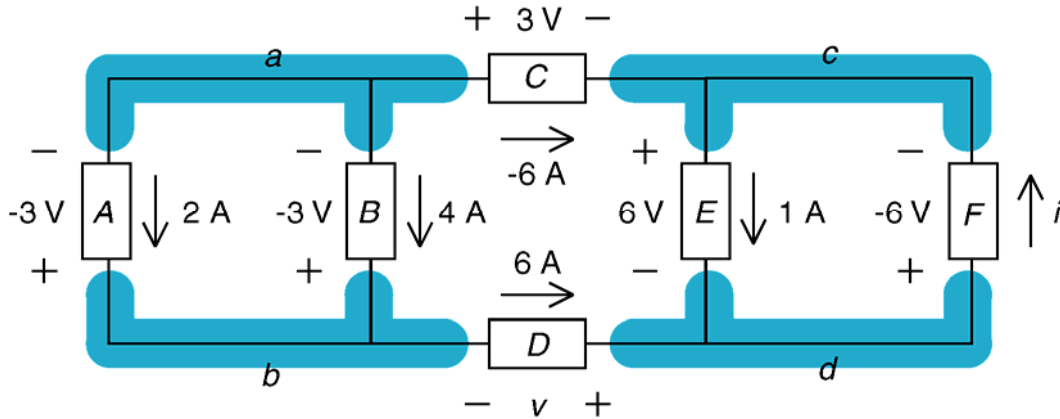


Figure 2. Labeling the nodes of the circuit from Figure 1.

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements C , E , D and B to get

$$3 + 6 + v + (-3) = 0 \quad \Rightarrow \quad v = -6 \text{ V}$$

The value of the current in element D in Figure 2 is 6 A. The voltage and current of element D given in Figure 2 do not adhere to the passive convention so

$$p_D = v (6) = (-6) (6) = -36 \text{ W}$$

is the power *supplied* by element D . (Equivalently, we could say that element D *receives* 36 W.)

Next, apply Kirchhoff's current law (KCL) at node c to get

$$-6 + i = 1 \quad \Rightarrow \quad i = 7 \text{ A}$$

The value of the voltage across element F in Figure 2 is -6 V. The voltage and current of element F given in Figure 2 adhere to the passive convention so

$$p_F = (-6) i = (-6) (7) = -42 \text{ W}$$

is the power *received* by element F . (Equivalently, we could say that element F *supplies* 42 W.)

Example 2:

Consider the circuit shown in Figure 3. Determine the power supplied by element B and the power supplied by element C .

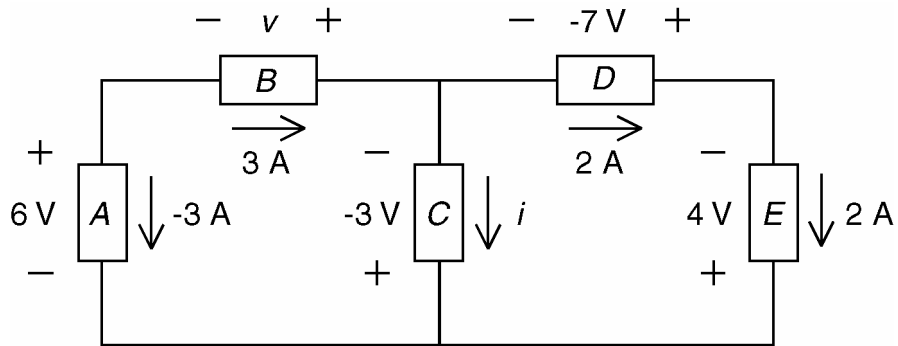


Figure 3. The circuit considered in Example 2

Solution: Figure 3 provides a value for the current in element B but not for the voltage, v , across element B . The voltage and current of element B given in Figure 1 do not adhere to the passive convention so the product of this voltage and current is the power *supplied* by element B . Similarly, Figure 3 provides a value for the voltage across element C but not for the current, i , in element C . The voltage and current of element C given in Figure 1 do not adhere to the passive convention so the product of this voltage and current is the power *supplied* by element C .

We need to determine the voltage, v , across element B and the current, i , in element C . We will use Kirchhoff's laws to determine values of v and i . First, we identify and label the nodes of the circuit as shown in Figure 4.

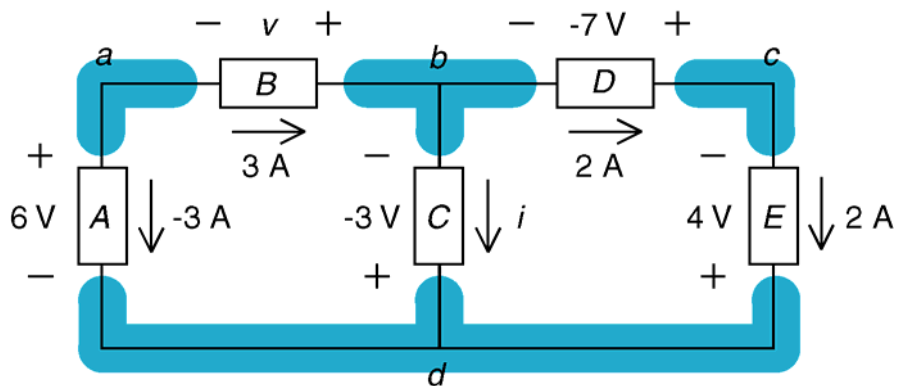


Figure 4. Labeling the nodes of the circuit from Figure 3.

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements B , C and A to get

$$-v - (-3) - 6 = 0 \quad \Rightarrow \quad v = -3 \text{ V}$$

The value of the current in element B in Figure 4 is 3 A. The voltage and current of element B given in Figure 4 do not adhere to the passive convention so

$$p_B = v(3) = (-3)(3) = -9 \text{ W}$$

is the power *supplied* by element B . (Equivalently, we could say that element B *receives* 9 W.)

Next, apply Kirchoff's current law (KCL) at node b to get

$$2 + i = 3 \quad \Rightarrow \quad i = 1 \text{ A}$$

The value of the voltage across element C in Figure 4 is -3 V. The voltage and current of element C given in Figure 4 do not adhere to the passive convention so

$$p_C = (-3)i = (-3)(1) = -3 \text{ W}$$

is the power *supplied* by element C . (Equivalently, we could say that element C *receives* 3 W.)

Example 3:

Consider the circuit shown in Figure 5. Determine the power supplied by element C and the power received by element D .

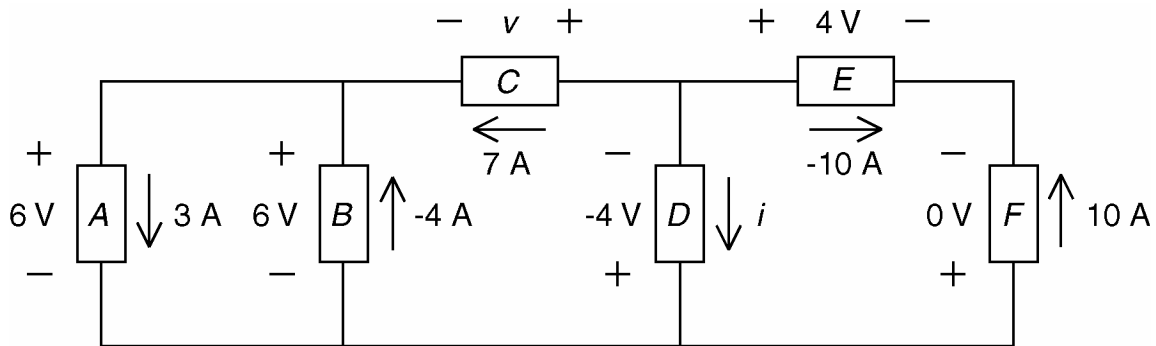


Figure 5. The circuit considered in Example 3

Solution: Figure 5 provides a value for the current in element C but not for the voltage, v , across element C . The voltage and current of element C given in Figure 5 adhere to the passive convention so the product of this voltage and current is the power *received* by element C . Similarly, Figure 5 provides a value for the voltage across element D but not for the current, i , in element D . The voltage and current of element D given in Figure 5 do not adhere to the passive convention so the product of this voltage and current is the power *supplied* by element D .

We need to determine the voltage, v , across element C and the current, i , in element D . We will use Kirchhoff's laws to determine values of v and i . First, we identify and label the nodes of the circuit as shown in Figure 6.

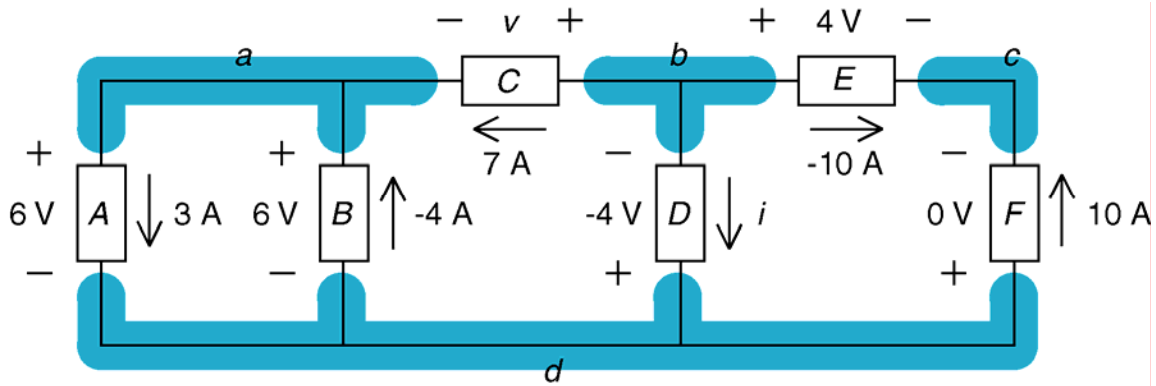


Figure 6. Labeling the nodes of the circuit from Figure 5.

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements C , D and B to get

$$-v - (-4) - 6 = 0 \quad \Rightarrow \quad v = -2 \text{ V}$$

The value of the current in element C in Figure 6 is 7 A. The voltage and current of element C given in Figure 6 adhere to the passive convention so

$$p_D = v (7) = (-2) (7) = -14 \text{ W}$$

is the power *received* by element C . Therefore element C *supplies* 14 W.

Next, apply Kirchhoff's current law (KCL) at node b to get

$$7 + (-10) + i = 0 \quad \Rightarrow \quad i = 3 \text{ A}$$

The value of the voltage across element D in Figure 6 is -4 V. The voltage and current of element D given in Figure 6 do not adhere to the passive convention so the power *supplied* by element F is given by

$$p_F = (-4) i = (-4) (3) = -12 \text{ W}$$

Therefore, element D *receives* 12 W.

Example 4:

Consider the circuit shown in Figure 7. Determine the power supplied by element B and the power received by element F .

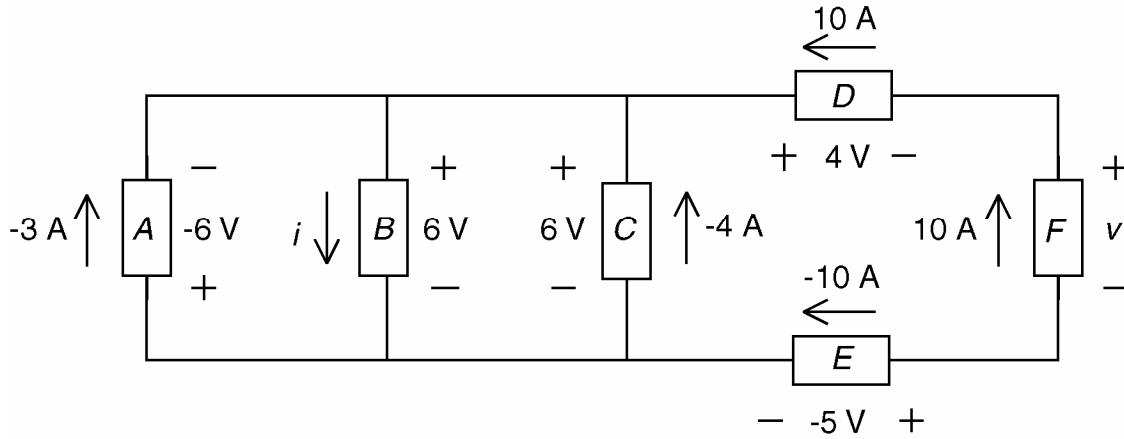


Figure 7. The circuit considered in Example 4

Solution: Figure 7 provides a value for the voltage across element B but not for the current, i , in element B . The voltage and current of element B given in Figure 7 adhere to the passive convention so the product of this voltage and current is the power *received* by element B . Similarly, Figure 7 provides a value for the current in element F but not for the voltage, v , across element F . The voltage and current of element F given in Figure 7 do not adhere to the passive convention so the product of this voltage and current is the power *supplied* by element F .

We need to determine the current, i , in element B and the voltage, v , across element F . We will use Kirchhoff's laws to determine values of i and v . First, we identify and label the nodes of the circuit as shown in Figure 8.

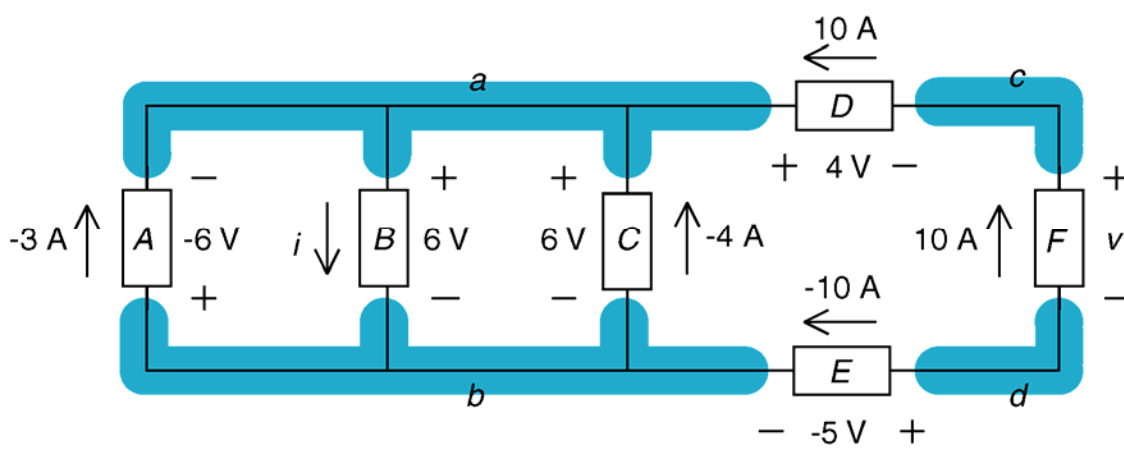


Figure 8. Labeling the nodes of the circuit from Figure 7.

Apply Kirchhoff's current law (KCL) at node a to get

$$i = -3 + (-4) + 10 \quad \Rightarrow \quad i = 3 \text{ A}$$

The value of the voltage across element B in Figure 8 is 6 V. The voltage and current of element B given in Figure 8 adhere to the passive convention so

$$p_B = (6) i = (6) (3) = 18 \text{ W}$$

is the power *received* by element B . Therefore element B *supplies* -18 W.

Next, apply Kirchhoff's voltage law (KVL) to the loop consisting of elements D , F , E and C to get

$$4 + v + (-5) - (6) = 0 \quad \Rightarrow \quad v = 7 \text{ V}$$

The value of the current in element F in Figure 8 is 10 A. The voltage and current of element F given in Figure 8 do not adhere to the passive convention so

$$p_D = v (10) = (7) (10) = 70 \text{ W}$$

is the power *supplied* by element F . Therefore element F *receives* -70 W.

Example 5:

Consider the circuit shown in Figure 9. Determine the values of the currents in and voltages across the various circuit elements.

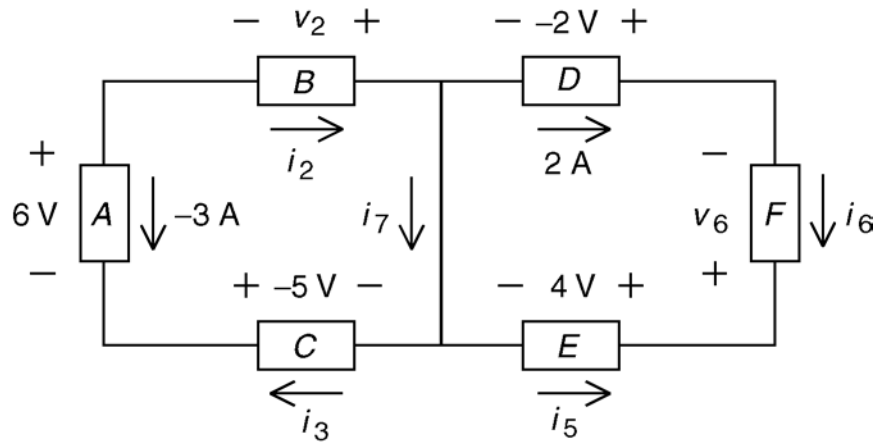


Figure 9. The circuit considered in Example 5

Solution: First, we identify and label the nodes of the circuit as shown in Figure 10.

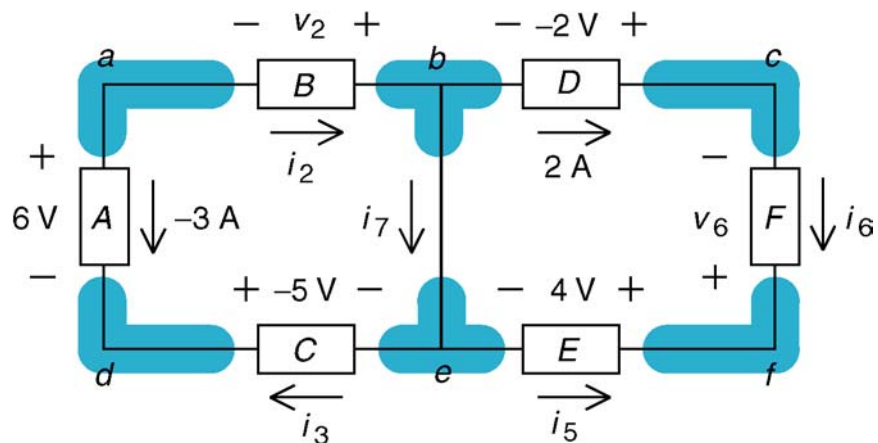


Figure 10. Labeling the nodes of the circuit from Figure 9.

Apply Kirchhoff's current law (KCL) at node *a* to get

$$i_2 + (-3) = 0 \Rightarrow i_2 = 3 \text{ A}$$

Apply KCL at node *d* to get

$$i_3 + (-3) = 0 \Rightarrow i_3 = 3 \text{ A}$$

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements A , B and C to get

$$-(v_2) - (-5) - 6 = 0 \Rightarrow v_2 = 1 \text{ V}$$

Apply KCL at node c to get

$$i_6 = 2 \text{ A}$$

Apply KCL at node f to get

$$i_5 + i_6 = 0 \Rightarrow i_5 = -i_6 = -2 \text{ A}$$

Apply KVL to the loop consisting of elements D , E and F to get

$$-(-2) - (v_6) + 4 = 0 \Rightarrow v_6 = 6 \text{ V}$$

Finally, apply KCL at node b to get

$$i_2 = i_7 + 2 \Rightarrow i_7 = 2 - i_2 = 2 - 3 = -1 \text{ A}$$

Example 6:

Consider the circuit shown in Figure 12. Determine the values of the currents in and voltages across the various circuit elements.

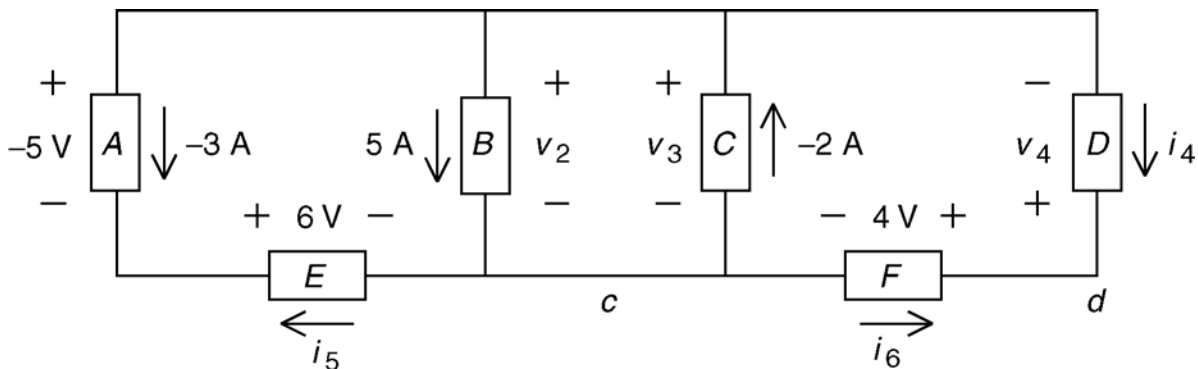


Figure 12. The circuit considered in Example 6

Solution: First, we identify and label the nodes of the circuit as shown in Figure 13.

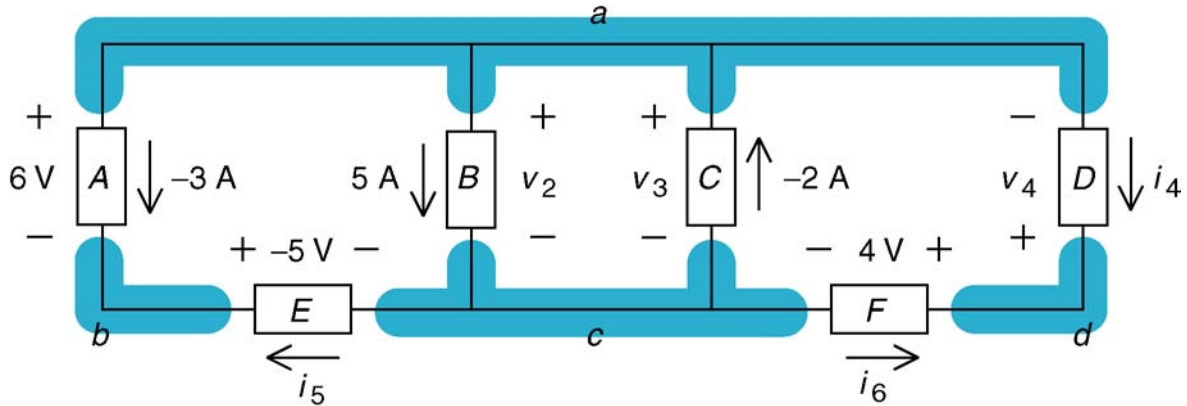


Figure 13. Labeling the nodes of the circuit from Figure 12.

Apply Kirchhoff's current law (KCL) at node b to get

$$i_5 + (-3) = 0 \Rightarrow i_5 = 3 \text{ A}$$

Apply KCL at node a to get

$$-2 = -3 + 5 + i_4 \Rightarrow i_4 = -4 \text{ A}$$

Apply KCL at node d to get

$$i_4 + i_6 = 0 \Rightarrow i_6 = -i_4 = -(-4) = 4 \text{ A}$$

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements A , B and E to get

$$v_2 - (-5) - 6 = 0 \Rightarrow v_2 = 1 \text{ V}$$

Apply KVL to the loop consisting of elements B and C to get

$$v_3 - v_2 = 0 \Rightarrow v_3 = v_2 = 1 \text{ V}$$

Finally, apply KVL to the loop consisting of elements C , D and F to get

$$-v_4 + 4 - v_3 = 0 \Rightarrow v_4 = 4 - v_3 = 4 - 1 = 3 \text{ V}$$

Example 7:

Consider the circuit shown in Figure 14. Determine the values of the currents in and voltages across the various circuit elements.

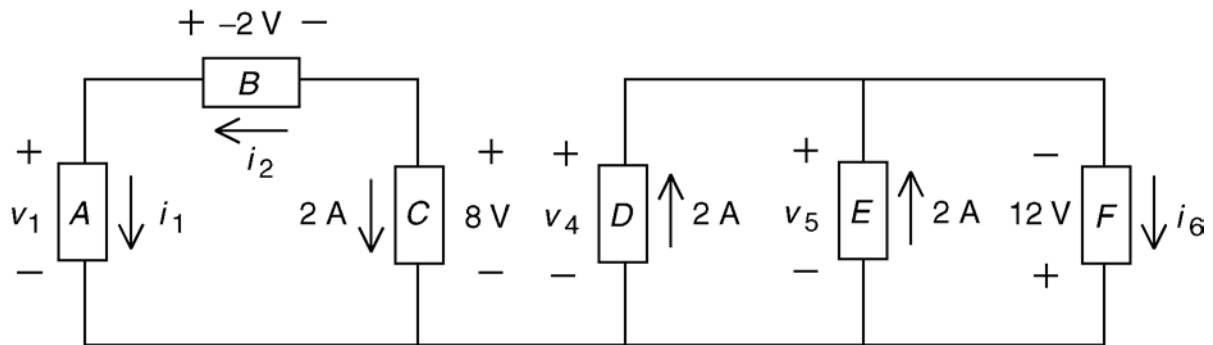


Figure 14. The circuit considered in Example 7

Solution: First, we identify and label the nodes of the circuit as shown in Figure 15.

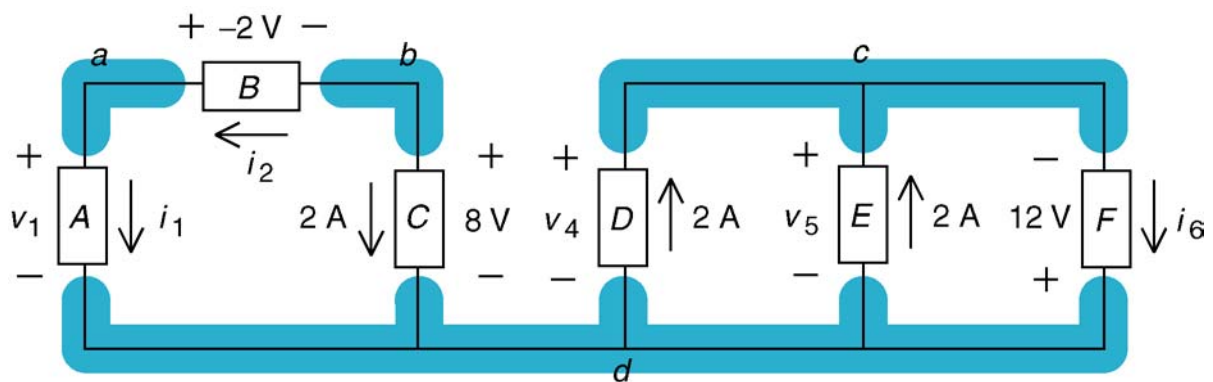


Figure 15. Labeling the nodes of the circuit from Figure 14.

Apply Kirchhoff's current law (KCL) at node *b* to get

$$i_2 + 2 = 0 \Rightarrow i_2 = -2 \text{ A}$$

Apply KCL at node *a* to get

$$i_1 = i_2 = -2 \text{ A}$$

Apply Kirchhoff's voltage law (KVL) to the loop consisting of elements A , B and C to get

$$-2 + 8 - v_1 = 0 \Rightarrow v_1 = 6 \text{ V}$$

Apply KCL at node c to get

$$i_6 = 2 + 2 = 4 \text{ A}$$

Apply KVL to the loop consisting of elements E and F to get

$$-12 - v_5 = 0 \Rightarrow v_5 = -12 \text{ V}$$

Finally, apply KVL to the loop consisting of elements D and E to get

$$v_5 - v_4 = 0 \Rightarrow v_4 = v_5 = -12 \text{ V}$$

Example 8:

Verify that power is conserved in the circuit shown in Figure 14.

Solution: The values of the currents in and voltages across the various circuit elements were determined in Example 7. Let's summarize what we know in the following table.

Element	Current, A	Voltage, V	Adhere to passive convention?	Power received, W
A	-2	6	Yes	-12
B	-2	-2	No	-4
C	2	8	Yes	16
D	2	-12	No	24
E	2	-12	No	24
F	4	12	No	-48

The sum of the power received by all of the elements in the circuit is zero so power is conserved.