

## Ohm's and Kirchoff's Laws


1. For  $t > 0$ , the inductor current and voltage are given by

$$i_6(t) = 0.8 - 0.6e^{-8t} \text{ A}$$

and

$$v_6(t) = 12e^{-8t} \text{ V}$$

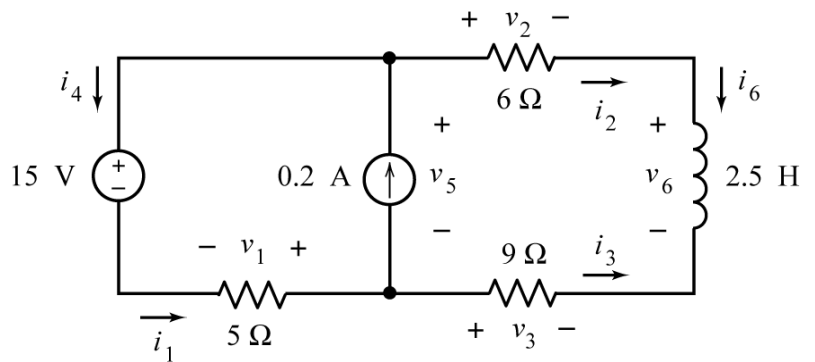Determine the voltage source current  $i_4(t)$ , the current source voltage,  $v_5(t)$  and the resistor voltage  $v_1(t)$ .




2. The voltages across the 10 Ω resistors are given to be

$$v_4(t) = 6.656 \cos(5t + 19.4^\circ) \text{ V}$$

and
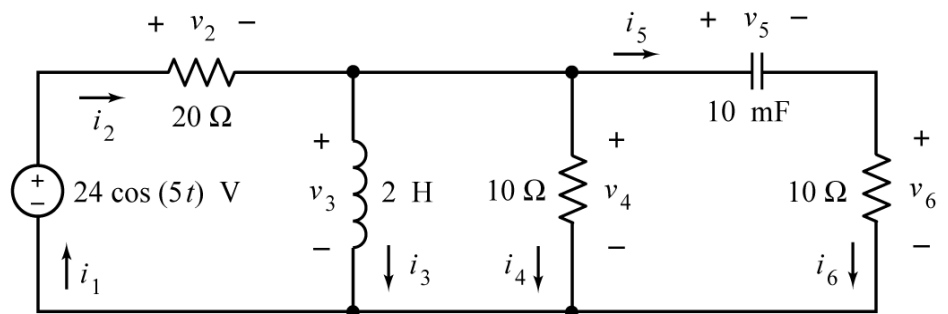
$$v_6(t) = 2.977 \cos(5t + 82.9^\circ) \text{ V}$$




Determine the voltages  $v_2(t)$  and  $v_5(t)$  and the current  $i_3(t)$ .

3. The voltages across the 40 Ω and 15 Ω resistors are given to be

$$v_3(t) = 10 \text{ V}$$

and

$$v_6(t) = 7.5 \text{ V}$$

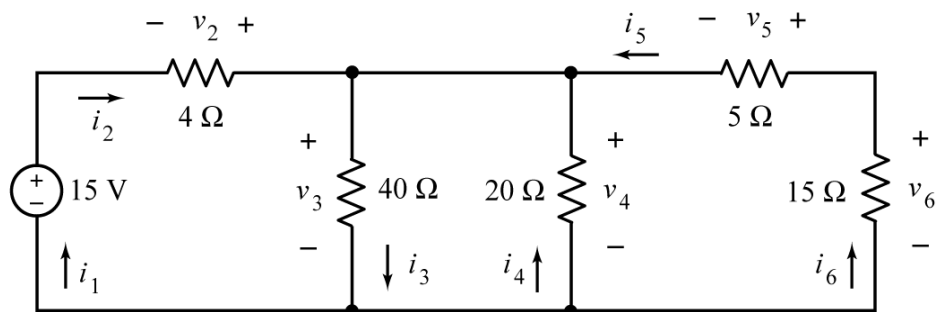


Determine the voltages  $v_2(t)$  and  $v_5(t)$  and the current  $i_4(t)$ .

## Complex Numbers

$$a + jb = r e^{j\theta} = r \angle \theta$$

where  $j = \sqrt{-1}$ ,  $a = r \cos \theta$ ,  $b = r \sin \theta$ ,  $r = \sqrt{a^2 + b^2}$

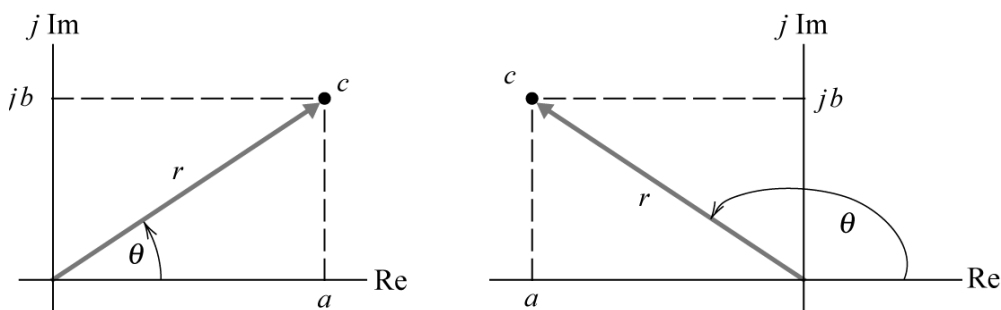and 
$$\theta = \begin{cases} \tan^{-1}\left(\frac{b}{a}\right) & a > 0 \\ 180^\circ - \tan^{-1}\left(\frac{b}{-a}\right) & a < 0 \end{cases}$$



$$c = a + jb = r e^{j\theta}$$

$$1 = 1 \angle 0^\circ, \quad j = 1 \angle 90^\circ, \quad -1 = j^2 = 1 \angle 180^\circ = 1 \angle -180^\circ, \quad -j = 1 \angle -90^\circ$$

## Complex Arithmetic

$$(a + jb)(c + jd) = (A e^{j\theta})(B e^{j\phi}) = AB \angle (\theta + \phi)$$

$$\frac{a + jb}{c + jd} = \frac{A e^{j\theta}}{B e^{j\phi}} = \frac{A}{B} \angle (\theta - \phi)$$

$$A e^{j\theta} + B e^{j\phi} = (a + jb) + (c + jd) = (a + c) + j(b + d)$$

$$(a + jb)(c + jd) = (ac - bd) + j(ad + bc)$$

$$(a + jb)^* = a - jb, \quad (A e^{j\theta})^* = A e^{-j\theta}, \quad (A \angle \theta)^* = A \angle -\theta$$

$$(a + jb) + (a + jb)^* = 2a, \quad (a + jb) - (a + jb)^* = j2b, \quad (A e^{j\theta})(A e^{j\theta})^* = A^2$$