

Ohm's and Kirchoff's Laws

1. Consider this circuit.

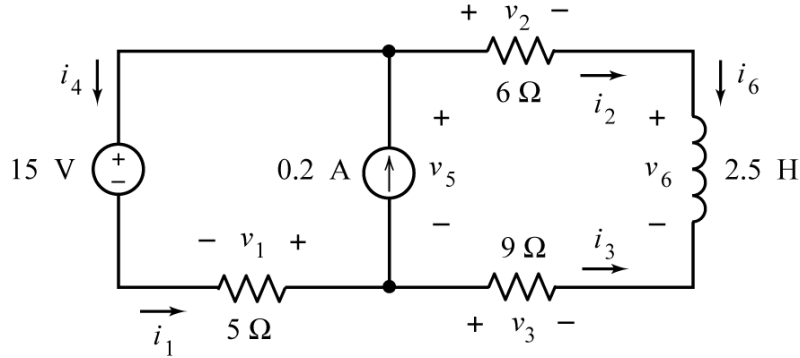


Figure 1

For $t > 0$, the inductor current and voltage are given by

$$i_6(t) = 0.8 - 0.6e^{-8t} \text{ A} \quad \text{and} \quad v_6(t) = 12e^{-8t} \text{ V} \quad (1)$$

Determine the voltage source current $i_4(t)$, the current source voltage, $v_5(t)$ and the resistor voltage $v_1(t)$.

Solution

From **KCL**

$$i_2(t) = i_6(t) = 0.8 - 0.6e^{-8t} \text{ A} \quad \text{and} \quad i_3(t) + i_6(t) = 0 \Rightarrow i_3(t) = -0.8 + 0.6e^{-8t} \text{ A}$$

From **Ohm's law**

$$v_2(t) = 6i_2(t) = 6(0.8 - 0.6e^{-8t}) = 4.8 - 3.6e^{-8t} \text{ V} \quad (2)$$

and

$$v_3(t) = 9i_3(t) = 9(-0.8 + 0.6e^{-8t}) = -7.2 + 5.4e^{-8t} \text{ V} \quad (3)$$

(Notice that the current and voltage of the 6Ω resistor, $i_2(t)$ and $v_2(t)$, adhere to the passive convention. Similarly, $i_3(t)$ and $v_3(t)$, adhere to the passive convention.)

From **KVL**

$$v_2(t) + v_6(t) - v_3(t) - v_5(t) = 0 \Rightarrow v_5(t) = v_2(t) + v_6(t) - v_3(t) \quad (4)$$

so

$$v_5(t) = (4.8 - 3.6e^{-8t}) + 12e^{-8t} - (-7.2 + 5.4e^{-8t}) = 12 + 3e^{-8t} \text{ V} \quad (5)$$

From **KCL**

$$0.2 = i_2(t) + i_4(t) \Rightarrow i_4(t) = 0.2 - i_2(t) = 0.2 - (0.8 - 0.6e^{-8t}) = -0.6 + 0.6e^{-8t} \text{ A}$$

and

$$i_1(t) = i_4(t) = -0.6 + 0.6e^{-8t} \text{ A}$$

From **Ohm's law**

$$v_1(t) = -5i_1(t) = -5(-0.6 + 0.6e^{-8t}) = 3 - 3e^{-8t} \text{ V}$$

(Notice that the current and voltage of the 5Ω resistor, $i_1(t)$ and $v_1(t)$, **do not** adhere to the passive convention. Consequently $v_1(t) = -5i_1(t)$ rather than $v_1(t) = 5i_1(t)$.)

As a check, apply KVL to the left mesh to get

$$v_5(t) + v_1(t) - 15 = 0 \Rightarrow v_1(t) = -v_5(t) + 15 = -(12 + 3e^{-8t}) + 15 = 3 - 3e^{-8t} \text{ V}$$

as before.

```

MATLAB
File Edit Debug Desktop Window Help
Shortcuts How to Add What's New
>> t=0.2;
>> v6 = 12*exp(-8*t)
v6 =
    2.4228
>> v2 = 4.8 - 3.6*exp(-8*t)
v2 =
    4.0732
>> v3 = -7.2 + 5.4*exp(-8*t)
v3 =
   -6.1098
>> v5 = v2 + v6 - v3
v5 =
   12.6057
>> v5 = 12 + 3*exp(-8*t)
v5 =
   12.6057
>>
  
```

Figure 2 Using MATLAB to check a KVL equation.

The computer program MATLAB (Hanselman and Littlefield, 2005) provides additional ways to check our results. For example, Equation 4 is valid at all times $t > 0$. In Figure 2, Equation 4 is checked at time $t = 0.2$ seconds using MATLAB. Voltages v_6 , v_2 , and v_3 are

evaluated at time $t = 0.2$ seconds using equations 1, 2 and 3. Next, The voltage v_5 is calculated twice, using equations 4 and 5. The two values of v_5 are identical, indicating that our results are correct.

The computer program MATLAB also helps us to visualize the voltages and currents in our circuit. For example, Figure 3 shows a plot of the voltage v_5 as a function of time. We see that v_5 makes an exponential transition from 15 V at time zero to an eventual value of 12 V. These are the same values that are obtained from equation 5 by taking the limit of v_5 as time goes to zero and to infinity.


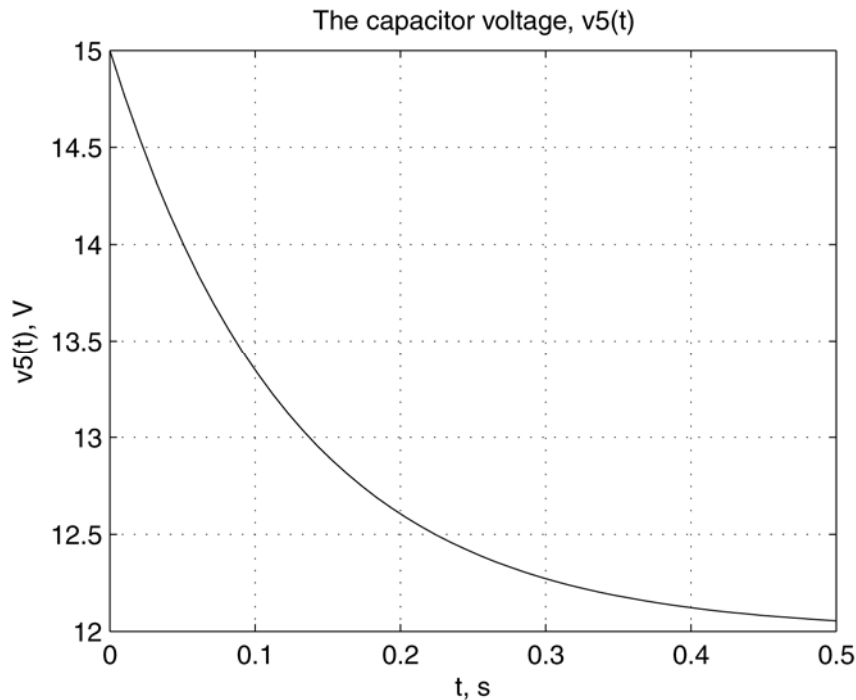


Figure 3 MATLAB plot of the voltage v_5 as a function of time.

2. Consider this circuit.

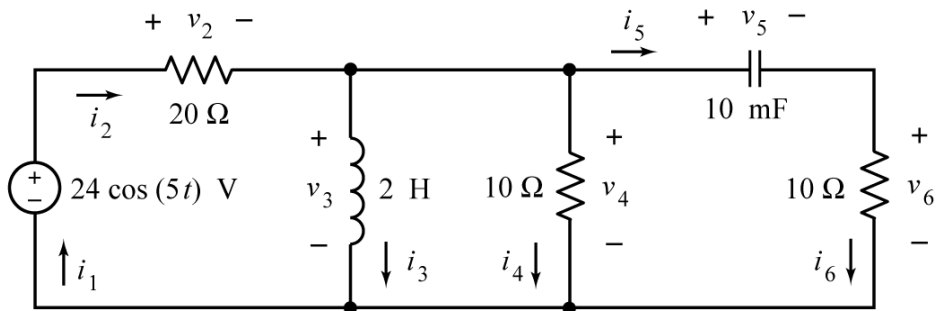

The voltages across the 10Ω resistors are given to be

$$v_4(t) = 6.656 \cos(5t + 19.4^\circ) \text{ V} \quad \text{and} \quad v_6(t) = 2.977 \cos(5t + 82.9^\circ) \text{ V}$$

Determine the voltages $v_2(t)$ and $v_5(t)$ and the current $i_3(t)$.

SolutionFrom **KVL**

$$\begin{aligned}
v_2(t) + v_4(t) - 24 \cos(5t) = 0 &\Rightarrow v_2(t) = -6.656 \cos(5t + 19.4^\circ) + 24 \cos(5t) \\
&= -(6.278 \cos(5t) + 2.211 \sin(5t)) + 24 \cos(5t) \\
&= 17.722 \cos(5t) - 2.211 \sin(5t) \\
&= 17.859 \cos(5t - 7.2^\circ) \text{ V}
\end{aligned}$$

Alternately, we can solve this problem using complex arithmetic instead of trigonometry. We use phasors to associate a complex number with each cosine:

$$A \cos(\omega t + \theta) \leftrightarrow A \angle \theta$$

Representing the cosines as complex numbers gives

$$-6.656 \cos(5t + 19.4^\circ) + 24 \cos(5t) \leftrightarrow -6.656 \angle 19.4^\circ + 24 \angle 0^\circ$$

Adding the complex numbers gives

$$-6.656 \angle 19.4^\circ + 24 \angle 0^\circ = -(6.278 + j2.211) + (24 + j0) = 17.722 - j2.211 = 17.859 \angle -7.2^\circ$$

Next, $v_2(t)$ is the sinusoidal voltage corresponding to $17.859 \angle -7.2^\circ$, that is

$$v_2(t) = 17.859 \cos(5t - 7.2^\circ) \text{ V}$$

From **KVL**

$$\begin{aligned}
v_5(t) + v_6(t) - v_4(t) = 0 &\Rightarrow v_5(t) = -2.977 \cos(5t + 82.9^\circ) + 6.656 \cos(5t + 19.4^\circ) \\
&= -(0.3680 \cos(5t) + 2.954 \sin(5t)) + (6.278 \cos(5t) + 2.211 \sin(5t)) \\
&= 5.910 \cos(5t) - 0.743 \sin(5t) \\
&= 5.957 \cos(5t - 7.2^\circ) \text{ V}
\end{aligned}$$

Using **Ohm's law** we can determine the resistor currents:

$$i_4(t) = \frac{v_4(t)}{10} = \frac{6.656 \cos(5t + 19.4^\circ)}{10} = 0.6656 \cos(5t + 19.4^\circ) \text{ A}$$

$$i_6(t) = \frac{v_6(t)}{10} = \frac{2.977 \cos(5t + 82.9^\circ)}{10} = 0.2977 \cos(5t + 82.9^\circ) \text{ A}$$

$$i_2(t) = \frac{v_2(t)}{20} = \frac{17.859 \cos(5t - 7.2^\circ)}{20} = 0.8930 \cos(5t - 7.2^\circ) \text{ A}$$

(Notice that the current and voltage of each resistor adhere to the passive convention.)

From **KCL**

$$i_2(t) = i_3(t) + i_4(t) + i_6(t) \Rightarrow i_3(t) = i_2(t) - (i_4(t) + i_6(t))$$

so

$$i_3(t) = 0.8930 \cos(5t + 172.8^\circ) - (0.6656 \cos(5t + 19.4^\circ) + 0.2977 \cos(5t + 82.9^\circ))$$

Adding the complex numbers gives

$$\begin{aligned} & 0.8930 \angle 7.2^\circ - (0.6656 \angle 19.4^\circ + 0.2977 \angle 82.9^\circ) \\ &= 0.8861 + j0.1105 - (0.6278 + j0.2211 + 0.0368 + j0.2954) \\ &= 0.2215 - j0.6270 = 0.6650 \angle -70.5^\circ \end{aligned}$$

Finally, $i_3(t)$ is the sinusoidal voltage corresponding to $0.6650 \angle -70.5^\circ$, that is

$$i_3(t) = 0.6650 \cos(5t - 70.5^\circ) \text{ V}$$


In summary, the required voltages and current are

$$v_2(t) = 17.859 \cos(5t - 7.2^\circ) \text{ V}, \quad v_5(t) = 5.957 \cos(5t - 7.2^\circ) \text{ V}$$

and

$$i_3(t) = 0.6650 \cos(5t - 70.5^\circ) \text{ V}$$

3. Consider this circuit.

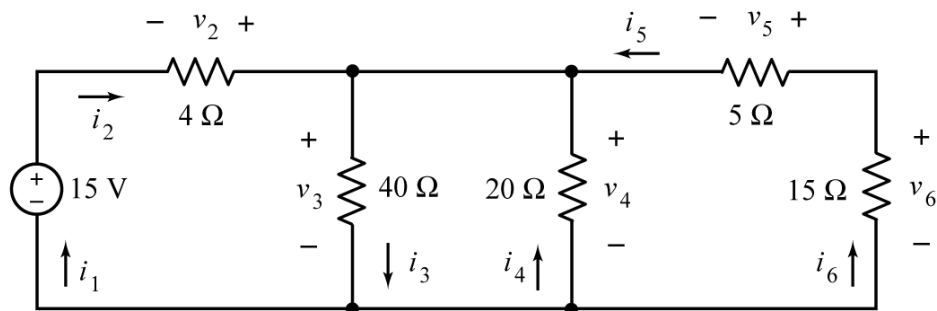

The voltages across the 40Ω and 15Ω resistors are given to be

$$v_3(t) = 10 \text{ V} \quad \text{and} \quad v_6(t) = 7.5 \text{ V}$$

Determine the voltages $v_2(t)$ and $v_5(t)$ and the current $i_4(t)$.

Solution:

From **KVL**

$$-v_5(t) + v_6(t) - v_3(t) = 0 \Rightarrow v_5(t) = v_6(t) - v_3(t) = 7.5 - 10 = -2.5 \text{ V}$$

and

$$-v_2(t) + v_3(t) - 15 = 0 \Rightarrow v_2(t) = v_3(t) - 15 = 10 - 15 = -5 \text{ V}$$

From **Ohm's law**

$$i_3(t) = \frac{v_3(t)}{40} = \frac{10}{40} = 0.25 \text{ A} \quad \text{and} \quad i_5(t) = \frac{v_5(t)}{5} = \frac{-2.5}{5} = -0.5 \text{ A}$$

(Notice that the current and voltage of the 40 Ω and 5 Ω resistors adhere to the passive convention.) Also,

$$i_2(t) = -\frac{v_2(t)}{4} = -\frac{-5}{4} = 1.25 \text{ A}$$

(Notice that the current and voltage of the 4 Ω resistor **does not** adhere to the passive convention.)

Finally, from **KCL**

$$i_2(t) + i_4(t) + i_5(t) = i_3(t) \Rightarrow i_4(t) = i_3(t) - (i_2(t) + i_5(t)) = 0.25 - (1.25 + (-0.5)) = -0.5 \text{ A}$$