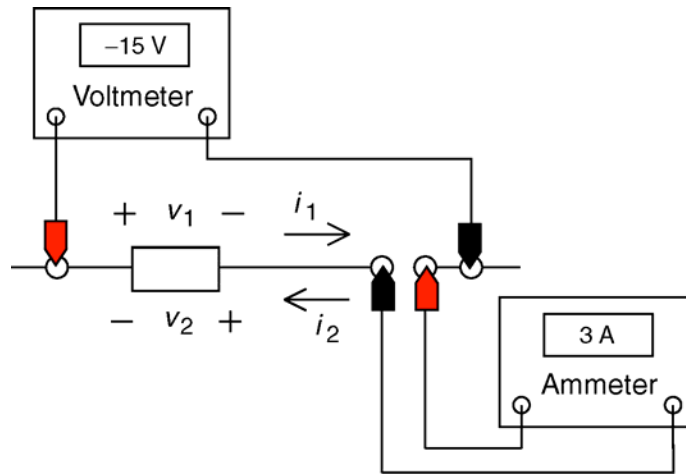


Passive Convention Exercises

Exercise 1:



The values of the element voltages and currents are

$$v_1 = \text{_____ V}, v_2 = \text{_____ V}, i_1 = \text{_____ A} \text{ and } i_2 = \text{_____ A}.$$

The value of power received by the circuit element is _____ W.

Is it possible that the circuit element is a resistor? What would be the value of resistance?

Solution 1:

The values of the element voltages and currents are

$$v_1 = \underline{-15} \text{ V}, v_2 = \underline{15} \text{ V}, i_1 = \underline{-3} \text{ A} \text{ and } i_2 = \underline{3} \text{ A}.$$

The value of power received by the circuit element is 45 W.


Is it possible that the circuit element is a resistor? What would be the value of resistance?

It's possible to build an electronic circuit that acts like a negative resistance, but we expect the resistance of a resistor to be positive, or at least non-negative. Here, noticing that v_1 and i_1 adhere to the passive convention, the resistance would be

$$R = \frac{v_1}{i_1} = \frac{-15}{-3} = 5 \Omega$$

Consequently, the element can be a resistor.

Exercise 2:

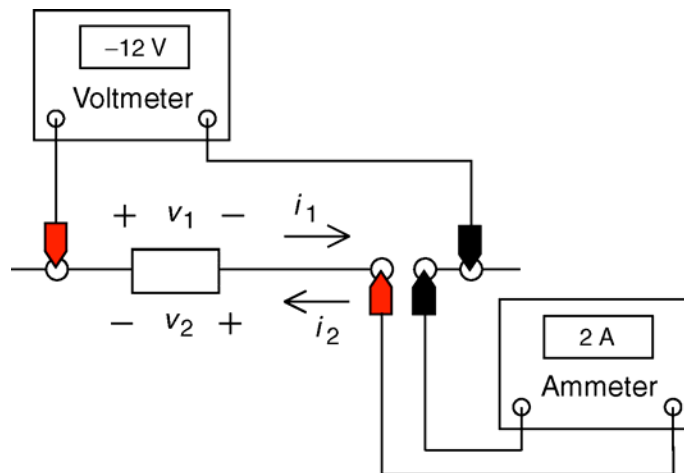

The values of the element voltages and currents are

$$v_1 = \underline{\hspace{2cm}} \text{ V}, v_2 = \underline{\hspace{2cm}} \text{ V}, i_1 = \underline{\hspace{2cm}} \text{ A} \text{ and } i_2 = \underline{\hspace{2cm}} \text{ A}.$$

The value of power received by the circuit element is W.

Is it possible that the circuit element is a resistor? What would be the value of resistance?

Solution 2:

The values of the element voltages and currents are


$$v_1 = \underline{-12} \text{ V}, v_2 = \underline{12} \text{ V}, i_1 = \underline{2} \text{ A} \text{ and } i_2 = \underline{-2} \text{ A}.$$

The value of power supplied by the circuit element is 24 W.

Noticing that v_1 and i_1 adhere to the passive convention, the resistance of the resistor would be

$$R = \frac{v_1}{i_1} = \frac{-12}{2} = -6 \Omega$$

Consequently, the element cannot be a resistor.

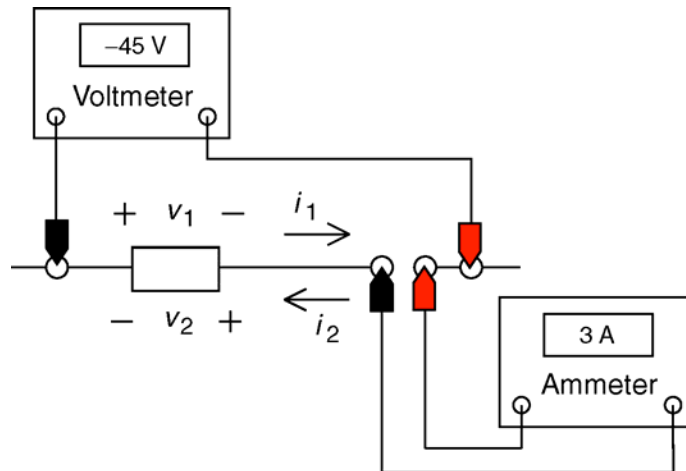Exercise 3:

The values of the element voltages and currents are

$$v_1 = \underline{\hspace{2cm}} \text{ V}, v_2 = \underline{\hspace{2cm}} \text{ V}, i_1 = \underline{\hspace{2cm}} \text{ A} \text{ and } i_2 = \underline{\hspace{2cm}} \text{ A}.$$

The value of power received by the circuit element is W.

The value of power supplied by the circuit element is W.

Solution 3:


The values of the element voltages and currents are

$$v_1 = \underline{\quad 45 \quad} \text{ V}, v_2 = \underline{\quad -45 \quad} \text{ V}, i_1 = \underline{\quad -3 \quad} \text{ A} \text{ and } i_2 = \underline{\quad 3 \quad} \text{ A}.$$

The value of power received by the circuit element is $\underline{\quad -135 \quad}$ W.

The value of power supplied by the circuit element is $\underline{\quad 135 \quad}$ W.

Exercise 4:

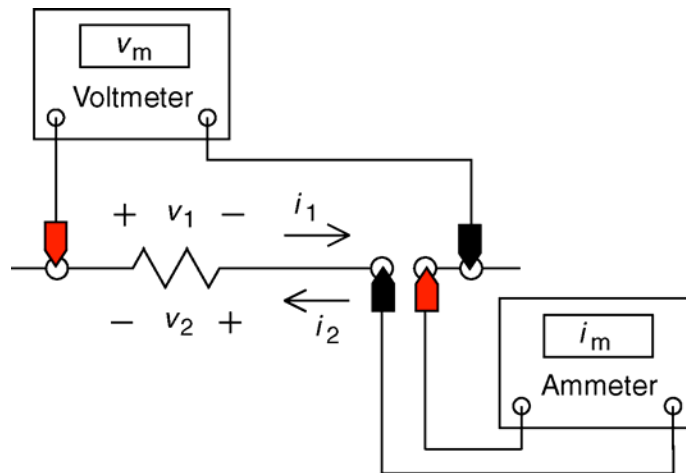

Suppose $v_m = 12$ V and $i_m = -2$ A. The value of power dissipated by the resistor is $\underline{\hspace{2cm}}$ W.

Suppose the resistance of the resistor is 15Ω and $i_m = -2$ A. The value of voltage measured by the voltmeter is $v_m = \underline{\hspace{2cm}}$ V.

Suppose $v_m = 60$ V and $i_m = 5$ A. The value of resistance of the resistor is $\underline{\hspace{2cm}}$ Ω .

Solution 4:

Suppose $v_m = 12$ V and $i_m = -2$ A. The value of power dissipated by the resistor is 24 W.

Suppose the resistance of the resistor is 15Ω and $i_m = -2$ A. The value of voltage measured by the voltmeter is $v_m =$ 30 V.

Suppose $v_m = 60$ V and $i_m = 5$ A. The value of resistance of the resistor is -12 Ω . (It's probably not a good idea to suppose that $v_m = 60$ V and $i_m = 5$ A.)