
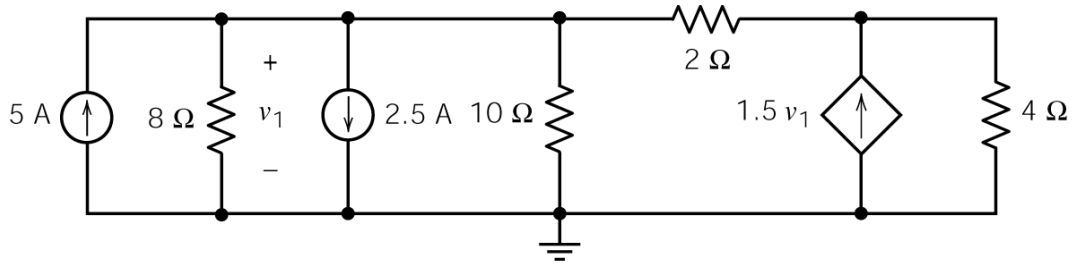


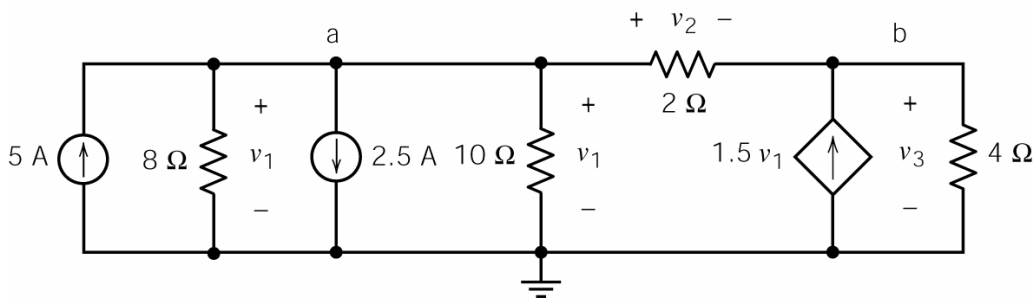**Example:** Determine the power supplied by each of the sources, independent and dependent, in this circuit:



**Solution:** We'll begin by choosing the bottom node to be the reference node. Next we'll label the other nodes and some element voltages:



Notice that the  $8\ \Omega$  resistor, the  $10\ \Omega$  resistor and the two independent current sources are all connected in parallel. Consequently, the element voltages of these elements can be labeled so that they are equal. Similarly, the  $4\ \Omega$  resistor and the dependent current source are connected in parallel so their voltages can be labeled so as to be equal.

Using Ohm's Law we see that the current directed downward in the  $8\ \Omega$  resistor is  $\frac{v_1}{8}$ , current directed downward in the  $10\ \Omega$  resistor is  $\frac{v_1}{10}$ , and the current directed from left to right in the  $2\ \Omega$  resistor is  $\frac{v_2}{2}$ . Applying Kirchhoff's Current Law (KCL) at node a gives

$$5 = \frac{v_1}{8} + 2.5 + \frac{v_1}{10} + \frac{v_2}{2} \Rightarrow 0.225 v_1 + 0.5 v_2 = 2.5 \quad (1)$$

Using Ohm's Law we see that the current directed downward in the  $4\ \Omega$  resistor is  $\frac{v_3}{4}$ . Applying Kirchhoff's Current Law (KCL) at node a gives

$$\frac{v_2}{2} + 1.5v_1 = \frac{v_3}{4} \Rightarrow 1.5v_1 + 0.5v_2 - 0.25v_3 = 0 \quad (2)$$


Applying Kirchhoff's Voltage Law (KVL) to the mesh consisting of the  $10 \Omega$  resistor, the  $2 \Omega$  resistor and the dependent source to get

$$v_2 + v_3 - v_1 = 0 \quad (3)$$

Equations 1, 2 and 3 comprise a set of three simultaneous equations in the three unknown voltages  $v_1$ ,  $v_2$  and  $v_3$ . We can write these equations in matrix form as

$$\begin{bmatrix} 0.225 & 0.5 & 0 \\ 1.5 & 0.5 & -0.25 \\ -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 2.5 \\ 0 \\ 0 \end{bmatrix}$$

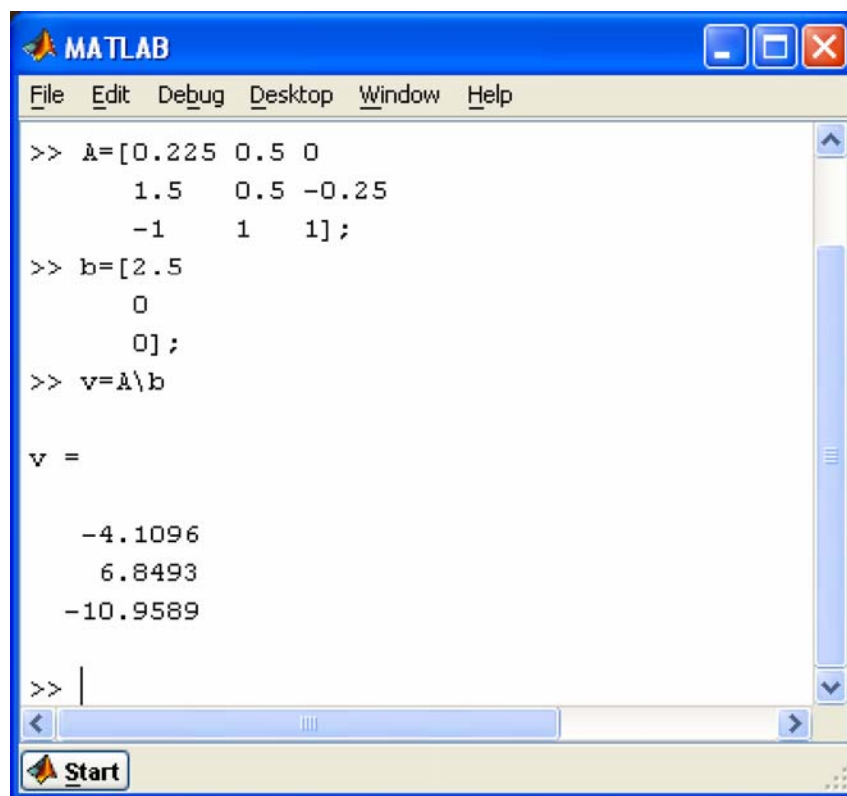We can solve this matrix equation using MATLAB:



```
MATLAB
File Edit Debug Desktop Window Help
>> A=[0.225 0.5 0
      1.5 0.5 -0.25
      -1 1 1];
>> b=[2.5
      0
      0];
>> v=A\b

v =

    -4.1096
     6.8493
    -10.9589


>> |
```

Hence

$$v_1 = -4.1096 \text{ V}, \quad v_2 = 6.8493 \text{ V} \quad \text{and} \quad v_3 = -10.9589 \text{ V}$$

The power supplied by the 5 A current source is  $5 v_1 = 5(-4.1096) = -20.548 \text{ W}$ . The power supplied by the 2.5 A current source is  $-2.5 v_1 = -2.5(-4.1096) = 10.274 \text{ W}$ . The power supplied by the dependent current source is  $(1.5 v_1) v_3 = 1.5(-4.1096)(-10.9589) = 67.555 \text{ W}$ .


**Observation:** Changing the order of the  $8 \Omega$  resistor, the  $10 \Omega$  resistor and the two independent current sources only changes the order of the terms in the KCL equation at node a. We know that addition is commutative, so change the order of the terms will not affect the values of the voltages  $v_1$ ,  $v_2$  and  $v_3$ . For example, if the positions of the 2.5 A current source and  $8 \Omega$  resistor are switched:

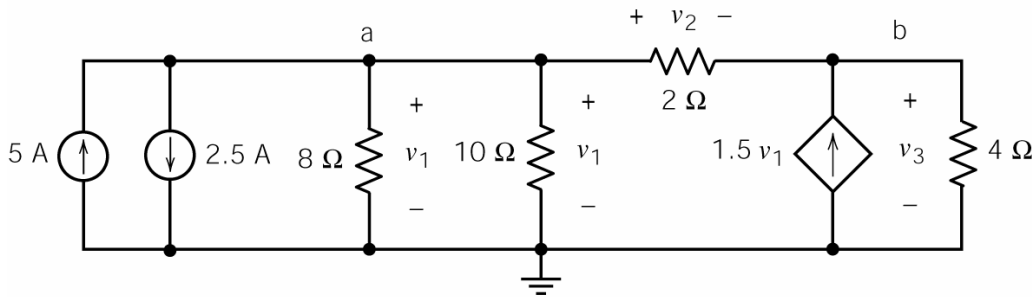

The KCL equation at node a is

$$5 = 2.5 + \frac{v_1}{8} + \frac{v_1}{10} + \frac{v_2}{2} \Rightarrow 0.225 v_1 + 0.5 v_2 = 2.5$$

Similarly, when the circuit is drawn as

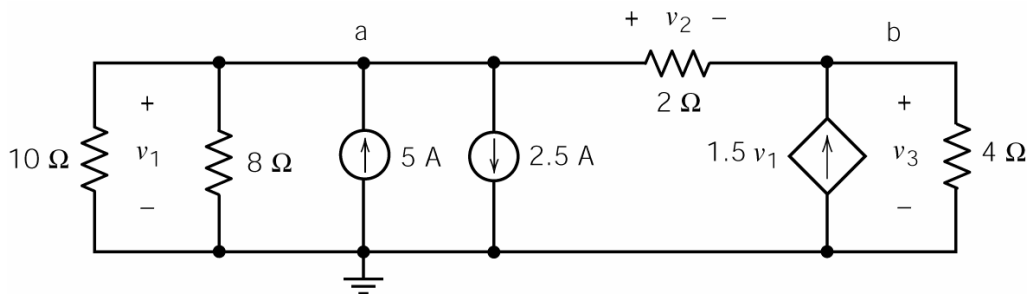


The KCL equation at node a is


$$5 = \frac{v_1}{10} + \frac{v_1}{8} + 2.5 + \frac{v_2}{2} \Rightarrow 0.225 v_1 + 0.5 v_2 = 2.5$$

The changes do not affect the values of the voltages  $v_1$ ,  $v_2$  and  $v_3$ .

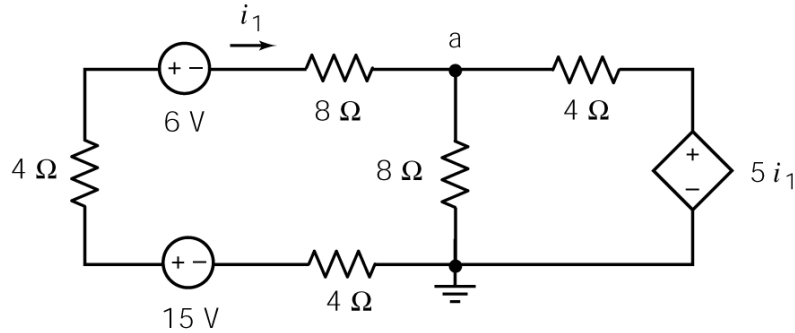**Example:** Determine the power supplied by each of the sources, independent and dependent, in this circuit:



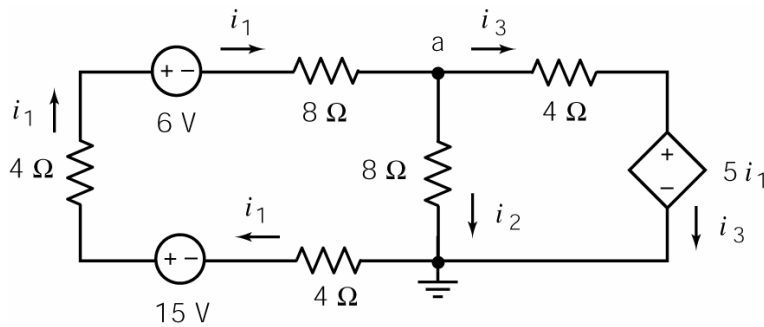**Solution:** We'll begin by choosing the bottom node to be the reference node. Next we'll label the other nodes and some element currents:



Notice that two  $4\ \Omega$  resistors, an  $8\ \Omega$  resistor and the two independent voltage sources are all connected in series. Consequently, the element currents of these elements can be labeled so that they are equal. Similarly, a  $4\ \Omega$  resistor and the dependent voltage source are connected in series so their currents can be labeled so as to be equal.

The current in each resistor has been labeled so we can use Ohm's Law to calculate resistor voltages from the resistor currents and the resistances. Apply Kirchhoff's Voltage Law (KVL) to the left mesh to get

$$6 + 8i_1 + 8i_2 + 4i_1 - 15 + 4i_1 = 0 \Rightarrow 16i_1 + 8i_2 = 9 \quad (1)$$

Apply Kirchhoff's Voltage Law (KVL) to the right mesh to get

$$4i_3 + 5i_1 - 8i_2 = 0 \quad (2)$$


Applying Kirchhoff's Current Law (KCL) at node a to get

$$i_1 = i_2 + i_3 \Rightarrow -i_1 + i_2 + i_3 = 0 \quad (3)$$

Equations 1, 2 and 3 comprise a set of three simultaneous equations in the three unknown voltages  $v_1$ ,  $v_2$  and  $v_3$ . We can write these equations in matrix form as

$$\begin{bmatrix} 16 & 8 & 0 \\ 5 & -8 & 4 \\ -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 9 \\ 0 \\ 0 \end{bmatrix}$$

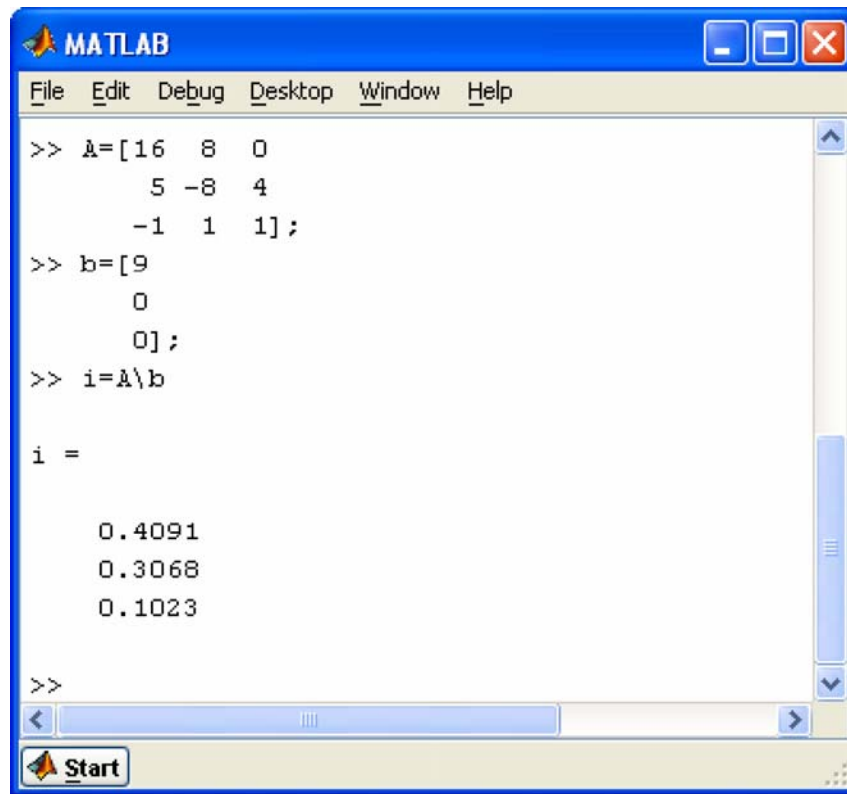We can solve this matrix equation using MATLAB:



```
MATLAB
File Edit Debug Desktop Window Help
>> A=[16 8 0
      5 -8 4
      -1 1 1];
>> b=[9
      0
      0];
>> i=A\b

i =

    0.4091
    0.3068
    0.1023


>>
```

Hence

$$i_1 = 0.4091 \text{ A}, \quad i_2 = 0.3068 \text{ A} \quad \text{and} \quad i_3 = 0.1023 \text{ A}$$

The power supplied by the 15 V voltage source is  $15i_1 = 15(0.4091) = 6.1365 \text{ W}$ . The power supplied by the 6 V voltage source is  $-6i_1 = -6(0.4091) = -2.4546 \text{ W}$ . The power supplied by the dependent voltage source is  $-(5i_2)i_3 = -5(0.3068)(0.1023) = 0.1569 \text{ W}$ .


**Observation:** Changing the order of the two  $4\ \Omega$  resistors, an  $8\ \Omega$  resistor and the two independent voltage sources in the left mesh changes the order of the terms in the KVL equation for that mesh. We know that addition is commutative, so change the order of the terms will not affect the values of the currents  $i_1$ ,  $i_2$  and  $i_3$ . For example, when the circuit is drawn as

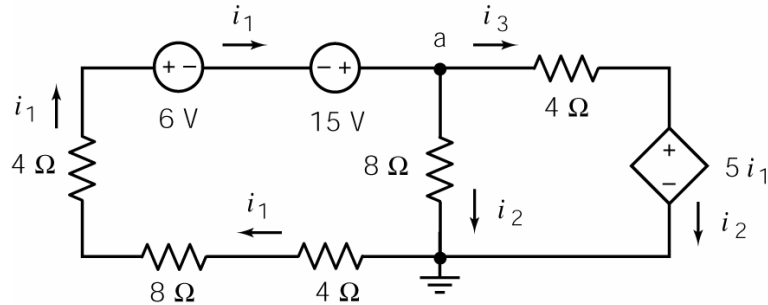

The KVL equation for the left mesh is

$$6 - 15 + 8i_2 + 4i_1 + 8i_1 + 4i_1 = 0 \Rightarrow 16i_1 + 8i_2 = 9$$

When the circuit is drawn as

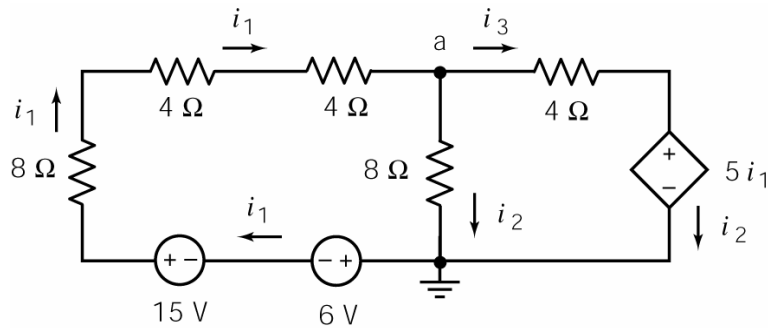

The KVL equation for the left mesh is

$$4i_1 + 4i_1 + 8i_2 + 6 - 15 + 8i_1 = 0 \Rightarrow 16i_1 + 8i_2 = 9$$

These changes do not affect the values of the currents  $i_1$ ,  $i_2$  and  $i_3$ .