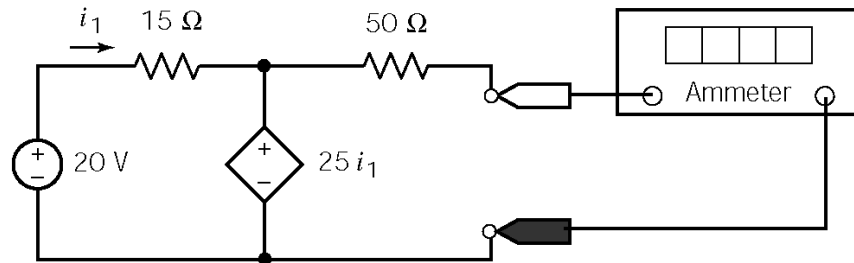


Four Examples

1. Determine the value of the current that is measured by the meter in this circuit.



Solution

We can label the circuit as shown.

The subscripts suggest a numbering of the circuit elements. Apply KVL to node the left mesh to get


$$15i_1 + 25i_1 - 20 = 0 \Rightarrow i_1 = \frac{20}{40} = 0.5 \text{ A}$$

Apply KVL to node the right mesh to get


$$v_2 - 25i_1 = 0 \Rightarrow v_2 = 25i_1 = 25(0.5) = 12.5 \text{ V}$$

Apply KCL to get $i_m = i_2$. Finally, apply Ohm's law to the 50Ω resistor to get
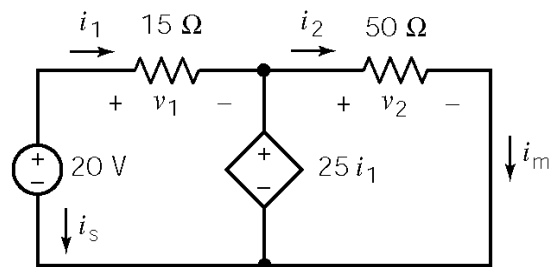
$$i_m = i_2 = \frac{v_2}{50} = \frac{12.5}{50} = 0.25 \text{ A}$$



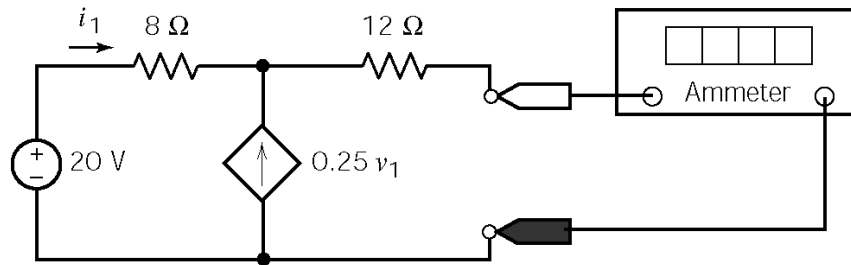2. Determine the value of the current that is measured by the meter in this circuit.




Solution

We can label the circuit as shown.

The subscripts suggest a numbering of the circuit elements. Ohm's law to the $8\ \Omega$ resistor to get

$$i_1 = \frac{v_1}{8}$$

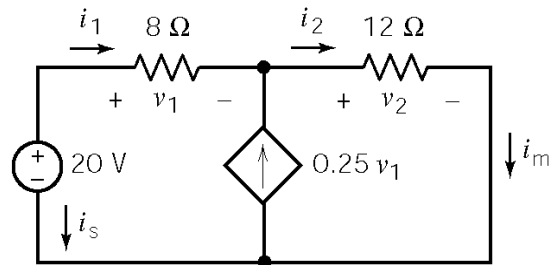

Apply KCL at the top node of the CCCS to get

$$i_1 + 0.25v_1 = i_2 \Rightarrow i_2 = i_1 + 0.25v_1 = \frac{v_1}{8} + 0.25v_1 = 0.375v_1$$

Ohm's law to the $8\ \Omega$ resistor to get

$$v_2 = 12i_2 = 12(0.375v_1) = 4.5v_1$$


Apply KVL to the outside to get

$$v_1 + v_2 - 20 = 0 \Rightarrow v_1 + 4.5v_1 = 20 \Rightarrow v_1 = \frac{20}{5.5} = 3.636\ \text{V}$$

Apply KCL to get $i_m = i_2$. Finally, apply Ohm's law to the $12\ \Omega$ resistor to get

$$i_m = i_2 = \frac{v_2}{12} = \frac{4.5v_1}{12} = \frac{4.5(3.636)}{12} = 1.634\ \text{A}$$

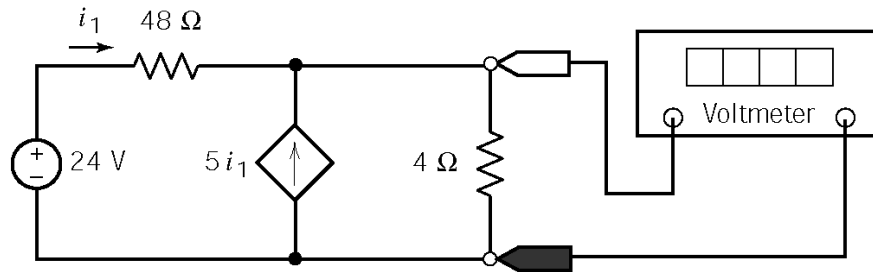3. Determine the value of the voltage that is measured by the meter in this circuit




Solution

We can label the circuit as shown.

The subscripts suggest a numbering of the circuit elements. Ohm's law to the 48 Ω resistor to get

$$v_1 = 48i_1$$

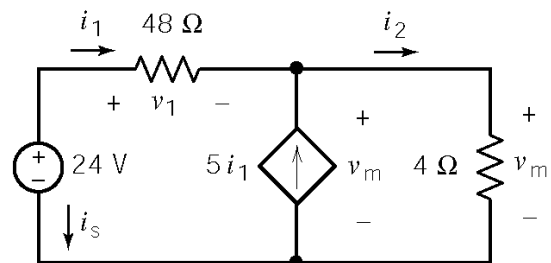

Apply KCL at the top node of the CCCS to get

$$i_1 + 5i_1 = i_2 \Rightarrow i_2 = 6i_1$$

Ohm's law to the 4 Ω resistor to get

$$v_m = 4i_2 = 4(6i_1) = 24i_1$$


Apply KVL to the outside loop to get

$$v_1 + v_m - 24 = 0 \Rightarrow 48i_1 + 24i_1 = 24 \Rightarrow i_1 = \frac{24}{72} = \frac{1}{3} \text{ A}$$

Finally,

$$v_m = 24i_1 = 24\left(\frac{1}{3}\right) = 8 \text{ V}$$

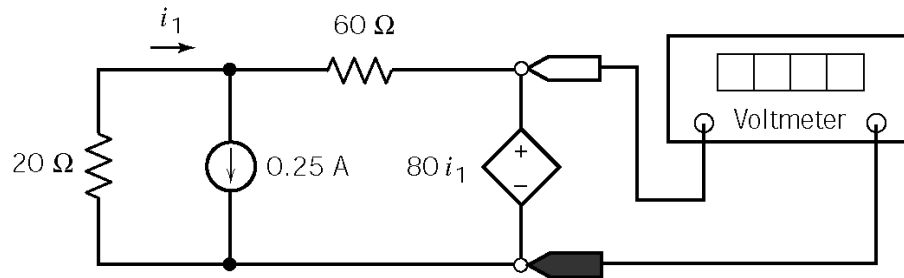4. Determine the value of the voltage that is measured by the meter in this circuit.




Solution

We can label the circuit as shown.

The subscripts suggest a numbering of the circuit elements. Apply KCL at the top node of the current source to get

$$i_1 = i_2 + 0.25$$

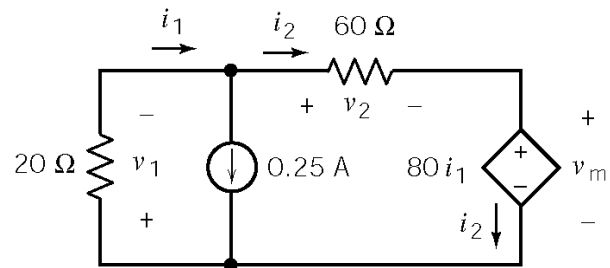

Ohm's law to the resistors to get

$$v_1 = 20i_1 \text{ and } v_2 = 60i_2 = 60(i_1 - 0.25) = 60i_1 - 15$$

Apply KVL to the outside to get

$$v_2 + 80i_1 + v_1 = 0 \Rightarrow (60i_1 - 15) + 80i_1 + 20i_1 = 0 \Rightarrow i_1 = \frac{15}{160} = 0.09375 \text{ A}$$

Finally,

$$v_m = 80i_1 = 80(0.09375) = 7.5 \text{ V}$$