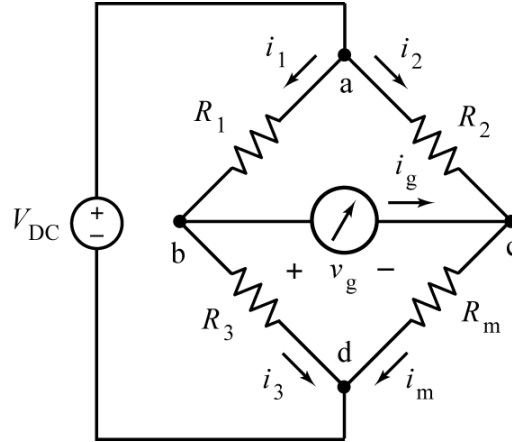


The Wheatstone Bridge

The Wheatstone Bridge consists of a dc voltage source, four resistors and a detector. The detector is a type of ammeter called a galvanometer.



The galvanometer is used to detect the condition $i_g = 0$. When the circuit satisfies the condition $i_g = 0$ we say that “the bridge is balanced”.

Because the galvanometer is a type of ammeter, $v_g = 0$. (It’s always true that $v_g = 0$, whether the bridge is balanced or not. When the bridge is balanced it is also true that $i_g = 0$.) Apply KVL to the top mesh of the bridge to get

$$R_2 i_2 - v_g - R_1 i_1 = 0 \Rightarrow R_1 i_1 = R_2 i_2 \quad (1)$$

Apply KVL to the bottom mesh of the bridge to get

$$v_g + R_m i_m - R_3 i_3 = 0 \Rightarrow R_3 i_3 = R_m i_m \quad (2)$$

When the bridge is balanced $i_g = 0$. Apply KCL to node b of the balanced bridge to get

$$i_1 = i_g + i_3 = 0 \Rightarrow i_1 = i_3 \quad (3)$$

Apply KCL to node c of the balanced bridge to get

$$i_2 + i_g = i_m \Rightarrow i_2 = i_m \quad (4)$$

Using equations 3 and 4 to substitute for the currents in equation 2 gives

$$R_3 i_1 = R_m i_2 \quad (5)$$

Dividing equation 5 by equation 1 gives

$$\frac{R_3}{R_1} = \frac{R_m}{R_2} \quad (6)$$

Now and solving for R_m we get

$$R_m = \frac{R_2}{R_1} R_3 \quad (6)$$

Typically, R_1 and R_2 are fixed resistors and R_3 is a variable resistor. R_m is the resistance that is being measured. R_3 is adjusted until the detector indicates that the bridge is balanced. Then the value of R_m is determined using equation 6.

Example

Consider using a Wheatstone bridge having $R_1 = 200 \Omega$ and $R_2 = 2000 \Omega$ to measure a resistance R_m . The bridge is balanced by adjusting R_3 until $R_3 = 250 \Omega$. What is the value of R_m ?

Solution

From equation 6

$$R_m = \frac{R_2}{R_1} R_3 = \frac{2000}{200} 250 = 2500 \Omega$$

Example

Consider using a Wheatstone bridge having $R_1 = 200 \Omega$ and $R_2 = 2000 \Omega$ to measure a resistance, R_m , of a temperature sensor. Suppose the resistance of the temperature sensor, R_m , in Ω , is related to the temperature T , in $^{\circ}\text{C}$, by the equation

$$R_m = 1500 + 25T$$

The bridge is balanced by adjusting R_3 until $R_3 = 250 \Omega$. What is the value of the temperature?

Solution

From equation 6

$$R_m = \frac{R_2}{R_1} R_3 = \frac{2000}{200} 250 = 2500 \Omega$$

Next, the temperature in $^{\circ}\text{C}$ is given by

$$T = \frac{R_m - 1500}{25} = \frac{2500 - 1500}{25} = \frac{1000}{25} = 40 \text{ }^{\circ}\text{C}$$

Example

Consider using a Wheatstone bridge having $R_1 = 200 \Omega$ and $R_2 = 2000 \Omega$ to measure a resistance, R_m , of a temperature sensor. Suppose the resistance of the temperature sensor, R_m , in Ω , is related to the temperature T , in $^\circ\text{C}$, by the equation

$$R_m = 1500 + 25T$$

The temperature is expected to vary over the range 0 to 100 $^\circ\text{C}$. Over what range must R_3 vary in order for the bridge to measure temperature over the range 0 to 100 $^\circ\text{C}$?

Solution:

Solve equation 6 for R_3 :

$$R_3 = \frac{R_1}{R_2} R_m \quad (7)$$

When $T = 0 \text{ }^\circ\text{C}$, $R_m = 1500 \Omega$ and

$$R_3 = \frac{R_1}{R_2} R_m = \frac{200}{2000} 1500 = 150 \Omega$$

When $T = 100 \text{ }^\circ\text{C}$, $R_m = 1500 + 25(100) = 4000 \Omega$ and

$$R_3 = \frac{R_1}{R_2} R_m = \frac{200}{2000} 4000 = 400 \Omega$$

R_3 could be implemented as a 150 Ω resistor in series with a 250 Ω potentiometer:

