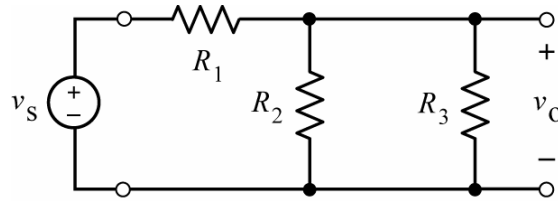


## DC Circuit with Specifications

### Example:

Consider this circuit:




The input to this circuit is the voltage of the voltage source,  $v_s$ . The output is the voltage  $v_o$ . We want to choose values of the resistances  $R_1$ ,  $R_2$  and  $R_3$  to satisfy the following specifications:

### Specifications:

1.  $v_o = A v_s$  where  $A = \frac{v_o}{v_s}$  is the gain of the circuit.
2. The value of the gain is  $A = \frac{3}{4}$  V/V.
3. All three resistors are quarter watt resistors.
4. The value of the input is restricted by  $|v_s| \leq 10$  V.
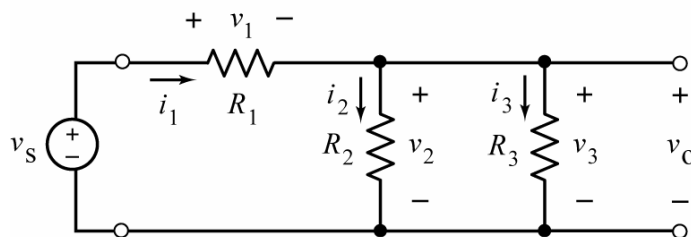
### Analysis:

Let's label the element voltage and current of each of the resistors. (In anticipation of using Ohm's law, we will choose the element current and voltage of each resistor to adhere to the passive convention.)



Notice that

$$v_2 = v_3 = v_o$$

It's reasonable to choose  $R_2 = R_3$ . (Otherwise the resistor with the smaller resistance will receive more power than the resistor having the larger resistance. Consequently, specification 3 will be harder to satisfy.) Then

$$i_2 = \frac{v_2}{R_2} = \frac{v_o}{R_2} = \frac{v_o}{R_3} = \frac{v_3}{R_3} = i_3$$

Next, apply KCL at the node where resistors  $R_1$ ,  $R_2$  and  $R_3$  are connected together to get

$$i_1 = i_2 + i_3 = i_2 + i_2 = 2i_2 \Rightarrow i_2 = i_3 = \frac{i_1}{2}$$

Now apply KVL to the loop consisting of the voltage source and resistors  $R_1$  and  $R_2$  to get

$$v_1 + v_2 - v_s = 0 \Rightarrow R_1 i_1 + R_2 i_2 - v_s = 0 \Rightarrow v_s = R_1 i_1 + R_2 i_2 = i_1 \left( R_1 + \frac{R_2}{2} \right)$$

So

$$i_1 = \frac{v_s}{R_1 + \frac{R_2}{2}} = \frac{2v_s}{2R_1 + R_2}$$

And

$$i_2 = i_3 = \frac{i_1}{2} = \frac{v_s}{2R_1 + R_2}$$

Finally, use Ohm's law to write

$$v_o = R_3 i_3 = R_2 i_2 = \frac{R_2 v_s}{2R_1 + R_2} = \frac{R_2}{2R_1 + R_2} v_s$$

Thus, specification 1 is satisfied with

$$A = \frac{R_2}{2R_1 + R_2}$$

From specification 2, we require

$$\frac{3}{4} = A = \frac{R_2}{2R_1 + R_2} \Rightarrow 3(2R_1 + R_2) = 4R_2 \Rightarrow 6R_1 = R_2$$

**Partial Result:**

Specifications 1 and 2 are satisfied by choosing resistances  $R_1$ ,  $R_2$  and  $R_3$  to satisfy

$$R_1 = R \quad \text{and} \quad R_2 = R_3 = 6R$$

This observation reduces the problem from one of finding three values;  $R_1$ ,  $R_2$  and  $R_3$ ; to one of finding a single value,  $R$ .

**More Analysis:**

Now let's consider the power supplied by each resistor. The power supplied by resistor  $R_1$  is given by

$$p_1 = R_1 i_1^2 = R_1 \left( \frac{2v_s}{2R_1 + R_2} \right)^2 = R \left( \frac{2v_s}{2R + 6R} \right)^2 = \left( \frac{1}{16} \right) \frac{v_s^2}{R}$$

Observe that  $p_1$  will be maximum when  $v_s$  is maximum. In view of specifications 3 and 4, we require  $p_1 \leq 0.25$  when  $v_s = 10$ . That is

$$0.25 \geq \left( \frac{1}{16} \right) \frac{v_s^2}{R} = \frac{100}{16R} = \frac{25}{4R} \Rightarrow R \geq 25$$

The power supplied by resistor  $R_2$  is given by

$$p_2 = R_2 i_2^2 = R_2 \left( \frac{v_s}{2R_1 + R_2} \right)^2 = 6R \left( \frac{v_s}{2R + 6R} \right)^2 = \left( \frac{3}{32} \right) \frac{v_s^2}{R}$$

Again,  $p_2$  will be maximum when  $v_s$  is maximum. In view of specifications 3 and 4, we require  $p_2 \leq 0.25$  when  $v_s = 10$ . That is

$$0.25 \geq \left( \frac{3}{32} \right) \frac{v_s^2}{R} = \frac{300}{32R} = \frac{75}{8R} \Rightarrow R \geq 37.5$$

The power supplied by resistor  $R_3$  is given by

$$p_3 = R_3 i_3^2 = R_3 \left( \frac{v_s}{2R_1 + R_2} \right)^2 = 6R \left( \frac{v_s}{2R + 6R} \right)^2 = \left( \frac{3}{32} \right) \frac{v_s^2}{R}$$

Once again,  $p_3$  will be maximum when  $v_s$  is maximum. In view of specifications 3 and 4, we require  $p_3 \leq 0.25$  when  $v_s = 10$ . That is

$$0.25 \geq \left( \frac{3}{32} \right) \frac{v_s^2}{R} = \frac{300}{32R} = \frac{75}{8R} \Rightarrow R \geq 37.5$$

**Result:**

All the specifications can be satisfied by choosing resistances  $R_1$ ,  $R_2$  and  $R_3$  to satisfy

$$R_1 = R \quad \text{and} \quad R_2 = R_3 = 6R$$

and

$$R \geq 37.5 \Omega$$

**Checking the Result:**

Let  $R = 40 \Omega$ . Then  $R_1 = 40 \Omega$  and  $R_2 = R_3 = 240 \Omega$ . Let  $v_s = 10 \text{ V}$ . In this case, we expect that the specifications will be satisfied. Analysis of the circuit gives

$$i_1 = 62.5 \text{ mA} \quad \text{and} \quad i_2 = i_3 = 31.25 \text{ mA}$$
$$v_1 = 2.5 \text{ V} \quad \text{and} \quad v_2 = v_3 = 7.5 \text{ V}$$

So

$$A = \frac{v_o}{v_s} = \frac{v_3}{v_s} = \frac{7.5}{10} = 0.75 \text{ V/V}$$

$$p_1 = 0.0625 \times 2.5 = 0.15625 \text{ W} \quad \text{and} \quad p_2 = p_3 = 0.03125 \times 7.5 = 0.234375 \text{ W}$$

The gain is correct and all of the resistor receive less than a quarter watt so the specifications are indeed satisfied.

As a second check, let  $R = 25 \Omega$ . Then  $R_1 = 25 \Omega$  and  $R_2 = R_3 = 150 \Omega$ . Let  $v_s = 10 \text{ V}$ . In this case, we expect the gain to be  $0.75 \text{ V/V}$  and resistor  $R_1$  to receive exactly one quarter watt of power. We also expect that resistors  $R_2$  and  $R_3$  to receive more than a quarter watt of power, so the specifications will not be satisfied. Analysis of the circuit gives

$$i_1 = 100 \text{ mA} \quad \text{and} \quad i_2 = i_3 = 50 \text{ mA}$$
$$v_1 = 2.5 \text{ V} \quad \text{and} \quad v_2 = v_3 = 7.5 \text{ V}$$

So

$$A = \frac{v_o}{v_s} = \frac{v_3}{v_s} = \frac{7.5}{10} = 0.75 \text{ V/V}$$

$$p_1 = 0.1 \times 2.5 = 0.25 \text{ W} \quad \text{and} \quad p_2 = p_3 = 0.05 \times 7.5 = 0.375 \text{ W}$$

The gain is correct but resistors  $R_2$  and  $R_3$  each receive more than a quarter watt of power, so the specifications are not satisfied.