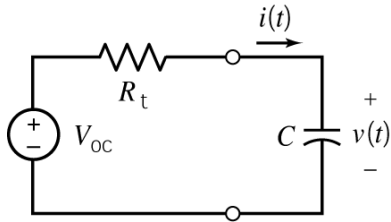


First-Order Dynamic Circuits

A Table at the end of Chapter 8 of Introduction to Electric Circuits indicates that the response of a first-order circuit can be obtained using Thevenin or Norton equivalent circuits:




When the open circuit voltage, V_{oc} , is constant after $t = 0$, the capacitor voltage is given by

$$v(t) = V_{oc} + (v(0) - V_{oc})e^{-at} \quad \text{for } t \geq 0$$

where

$$a = \frac{1}{R_t C}$$

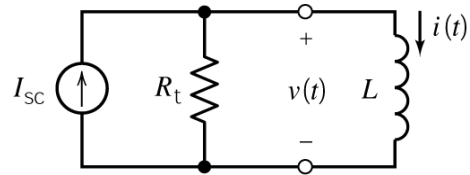

When the open circuit voltage, I_{sc} , is constant after $t = 0$, the inductor current is given by

$$i(t) = I_{sc} + (i(0) - I_{sc})e^{-at} \quad \text{for } t \geq 0$$

where

$$a = \frac{R_t}{L}$$


Example 1:

This diagram represents a circuit for time $t \geq 0$. Given the initial condition

$$i(0) = 2.4 \text{ A}$$

and the inductance

$$L = 6 \text{ H}$$

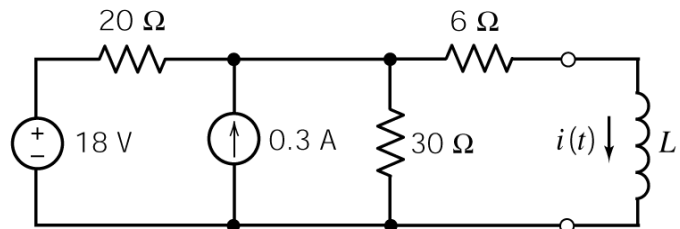

Represent the inductor current $i(t)$ as a function of t for $t \geq 0$.


Example 2:

This diagram represents a circuit for time $t \geq 0$. Given the initial condition

$$v(0) = 2 \text{ V}$$

and the capacitance

$$C = 0.1 \text{ F}$$





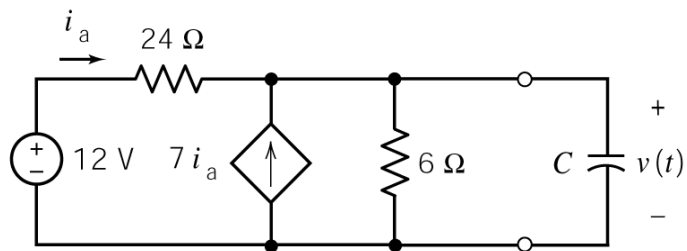




Represent the capacitor voltage $v(t)$ as a function of t for $t \geq 0$.

Solutions

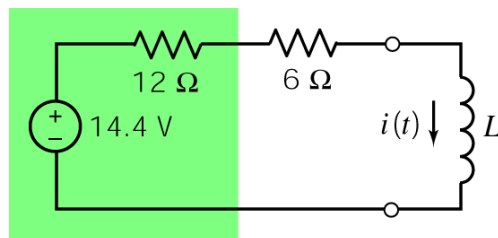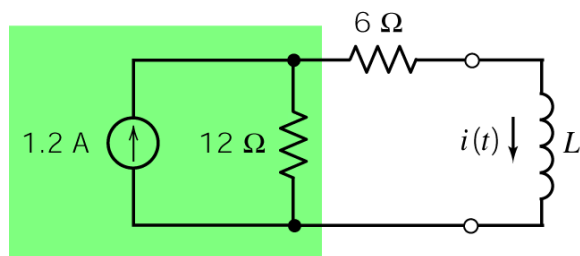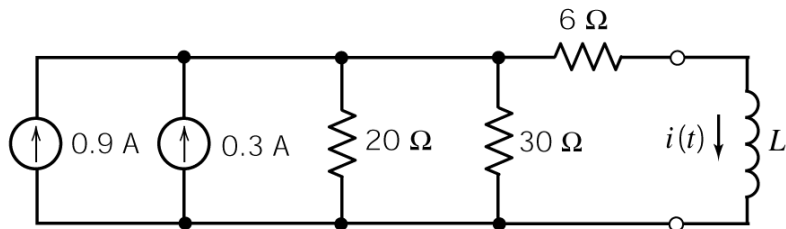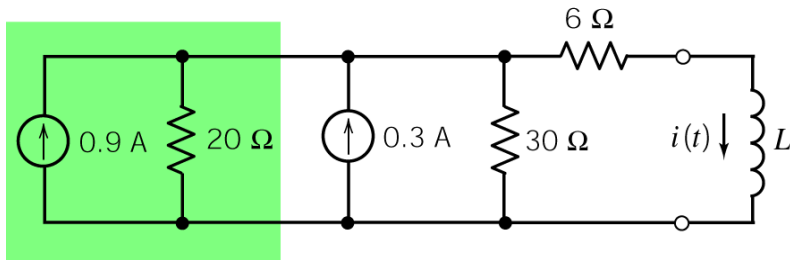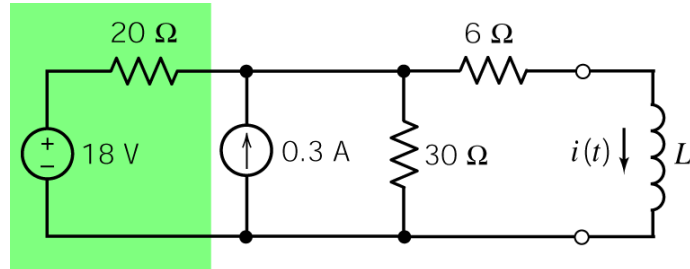Example 1.

Use source transformations and equivalent resistances to simplify the part of the circuit connected to inductor until it is a Norton equivalent circuit.



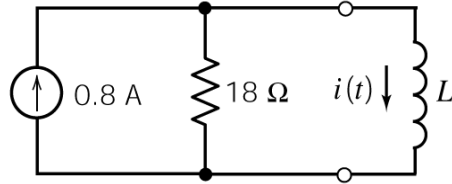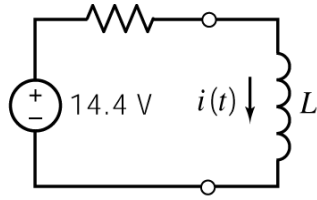

Now recognize that

$$I_{sc} = 0.8\text{ A} \quad \text{and} \quad R_t = 18\ \Omega$$

Then


$$a = \frac{R_t}{L} = \frac{18}{6} = 3\ \frac{1}{s}$$

Finally

$$i(t) = I_{sc} + (i(0) - I_{sc})e^{-at} = 0.8 + (2.4 - 0.8)e^{-3t} = 0.8 + 1.6e^{-3t} \quad \text{for } t \geq 0$$

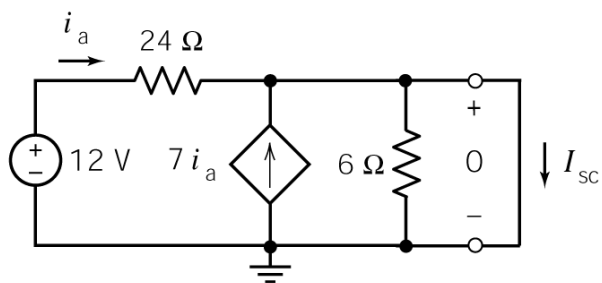
Example 2

We need to determine the values of I_{sc} , V_{oc} and R_t :




$$i_a = \frac{12-0}{24} = 0.5 \text{ A} . \text{ Then } (7+1) 0.5 = \frac{0}{6} + I_{sc}$$

$$I_{sc} = 4 \text{ A}$$

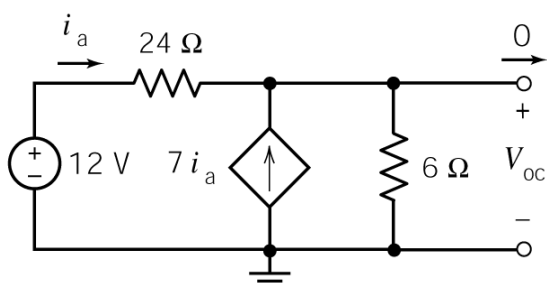

$$i_a = \frac{12-V_{oc}}{24} . \text{ Then } (7+1) \left(\frac{12-V_{oc}}{24} \right) = \frac{V_{oc}}{6}$$
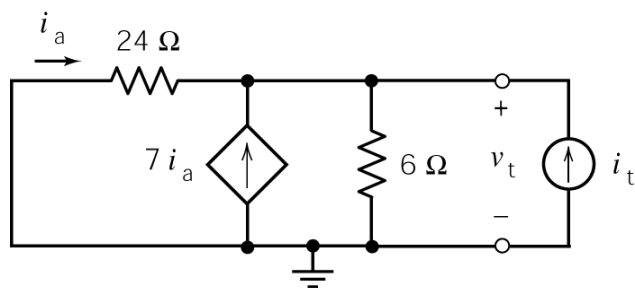
$$V_{oc} = \left(\frac{7+1}{7+5} \right) 12 = 8 \text{ V}$$



$$i_a = -\frac{v_t}{24} . \text{ Then } i_t + 7 \left(-\frac{v_t}{24} \right) = \frac{v_t}{24} + \frac{v_t}{6}$$

$$R_t = \frac{v_t}{i_t} = \frac{24}{7+5} = 2 \Omega$$

Using $v_{oc} = 8 \text{ V}$ and $R_t = 2 \Omega$ we have

$$a = \frac{1}{R_t C} = \frac{1}{2 \cdot 0.1} = 5 \frac{1}{s}$$

and

$$v(t) = V_{oc} + (v(0) - V_{oc}) e^{-at} = 8 + (2 - 8) e^{-5t} = 8 - 6e^{-5t} \text{ for } t \geq 0$$