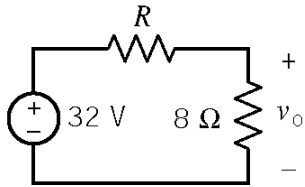


## ES 250 First Midterm Practice Exam 1

1. a. To cause  $v_o = 17.07$  V choose  $R = \underline{\quad 7 \quad} \Omega$ .




- b. To cause  $v_o = 9.143$  V choose  $R = \underline{\quad 20 \quad} \Omega$ .

- c. If  $R = 14 \Omega$  then  $v_o = \underline{\quad 11.6 \quad} \text{V}$


- d. If  $v_o = 14.22$  V the voltage source supplies  $\underline{\quad 56.9 \quad} \text{W}$  of power.

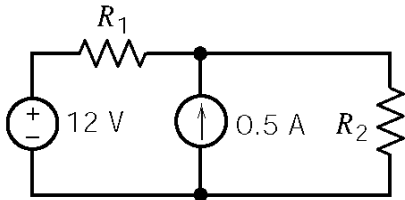2. The voltage source supplies 4.8 W of power and the current source supplies 3.6 W of power.



$$R_1 = \underline{\quad 12 \quad} \Omega \text{ and } R_2 = \underline{\quad 8 \quad} \Omega$$

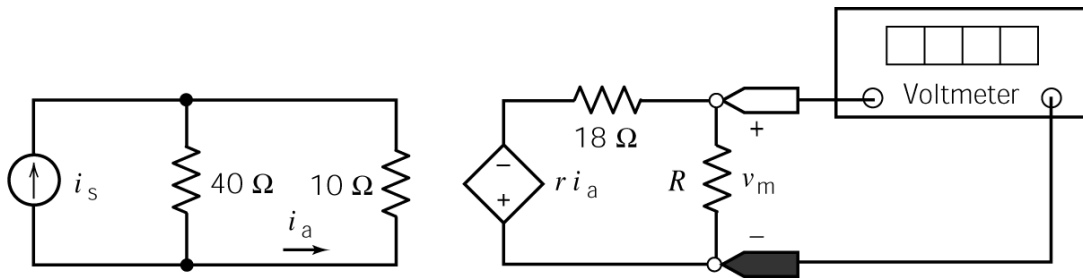3. The input to this circuit is the current of the current source,  $i_s$ . The output is the voltage measured by the meter,  $v_m$ . The output is proportional to the input, that is  $v_m = k i_s$ , where  $k$  is the constant of proportionality.




- a. When  $i_s = 3$  A,  $R = 12 \Omega$  and  $r = 10$  V/A, then  $i_a = \underline{\quad 2.4 \quad} \text{A}$  and  $v_m = \underline{\quad 9.6 \quad} \text{V}$ .

- b. When  $R = 12 \Omega$ , then  $r = \underline{\quad 6.25 \quad} \text{V/A}$  is required to cause  $v_m = 2 i_s$ .

- c. When  $r = 10$  V/A then  $R = \underline{\quad 6 \quad} \Omega$  is required to cause  $v_m = 2 i_s$ .

- d. When  $R = 12 \Omega$  and  $i_s = 5$  A, then  $r = \underline{\quad 7.5 \quad} \text{V/A}$  is required to cause  $v_m = 12$  V.

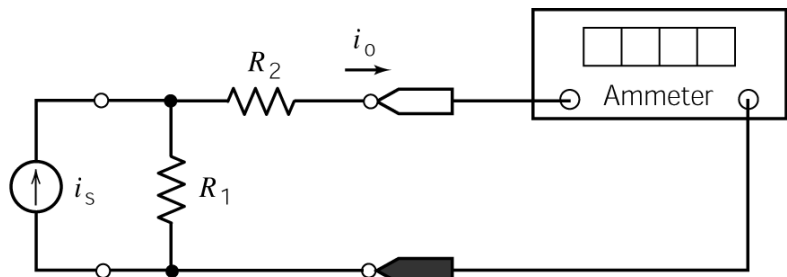4. The input to this circuit is the source current,  $i_s$ . The output is the current measured by the meter,  $i_o$ . A current divider connects the source to the meter.




Given these observations:

- A. The input  $i_s = 5$  A causes the output to be  $i_o = 2$  A.

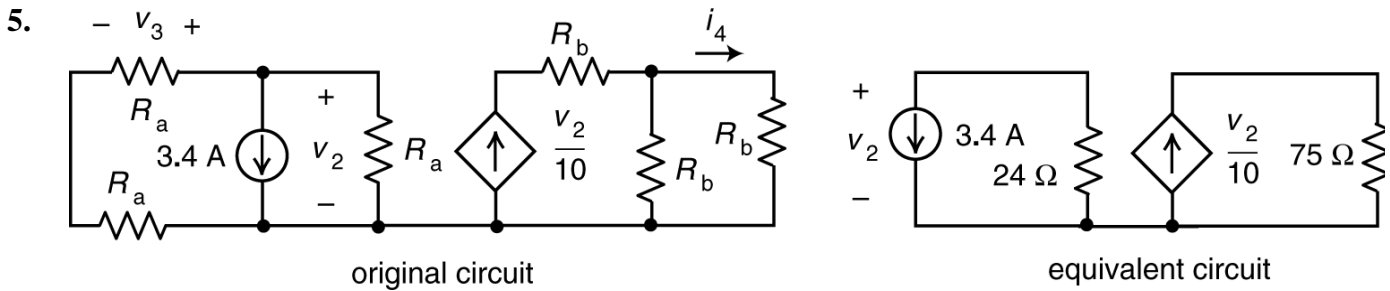B. When  $i_s = 2$  A the source supplies 48 W.

The values of the resistances are  $R_1 = \underline{20} \Omega$  and  $R_2 = \underline{30} \Omega$ .



The equivalent circuit on the right is obtained from the original circuit on the left by replacing series and parallel combinations of resistors by equivalent resistors. The original circuit contains 3 equal resistances labeled  $R_a$  and another 3 equal resistances labeled  $R_b$ . Determine the values of  $R_a$  and  $R_b$ . Given that

$v_2 = -81.6$  V, determine the values of  $v_3$  and  $i_4$ .

$R_a = \underline{36} \Omega$ ,  $R_b = \underline{50} \Omega$ ,  $v_3 = \underline{-40.8} \text{ V}$  and  $i_4 = \underline{-4.08} \text{ A}$ .

6. Given that


$v_a = 8$  V,

Determine the values of  $R_1$  and  $v_o$ :


$R_1 = \underline{10} \Omega$ ,

and

$v_o = \underline{-3.2} \text{ V}$

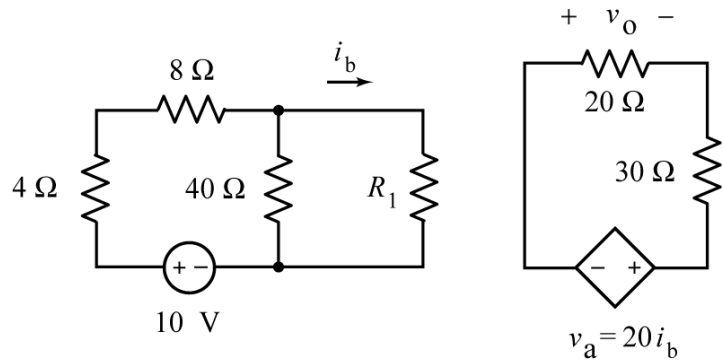

7.

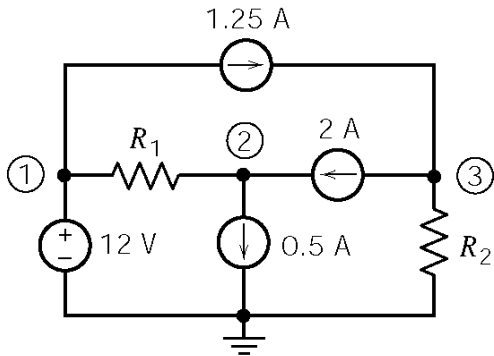

The encircled numbers are node numbers. The corresponding node voltages are

$v_1 = 12$  V,  $v_2 = 21$  V and  $v_3 = -3$  V,

- The 0.5 A current source **supplies**  $\underline{-10.5}$  W of power.
- The 2 A current source **supplies**  $\underline{48}$  W of power.
- $R_1 = \underline{6} \Omega$  and  $R_2 = \underline{4} \Omega$
- The voltage source **supplies**  $\underline{-3}$  W of power.