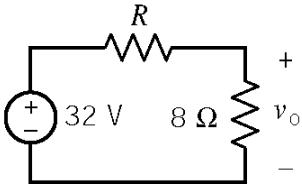


## ES 250 First Midterm Practice Exam 1

1.



a. To cause  $v_o = 17.07$  V choose  $R = \underline{\quad 7 \quad} \Omega$ .

b. To cause  $v_o = 9.143$  V choose  $R = \underline{\quad 20 \quad} \Omega$ .

c. If  $R = 14 \Omega$  then  $v_o = \underline{\quad 11.6 \quad} \text{V}$


d. If  $v_o = 14.22$  V the voltage source supplies  $\underline{\quad 56.9 \quad} \text{W}$  of power.

$v_o = \left(\frac{8}{8+R}\right)32$ . When  $v_o = 17.07$  V, then  $17.07 = \left(\frac{8}{8+R}\right)32 \Rightarrow R = \frac{(8)32}{17.07} - 8 = 6.997 \approx 7 \Omega$ . When

$v_o = 9.143$  V then  $9.143 = \left(\frac{8}{8+R}\right)32 \Rightarrow R = \frac{(8)32}{9.143} - 8 = 19.999 \approx 20 \Omega$ . When  $R = 14 \Omega$  then

$v_o = \left(\frac{8}{8+14}\right)32 = 11.6363$  V. The power supplied by the voltage source is given by  $32 \frac{v_o}{8} = 4v_o$  since  $\frac{v_o}{8}$  is the current in each of the series elements. When  $v_o = 14.22$  V the voltage source supplies 56.88 W.

2.

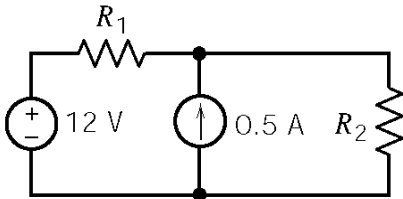


The voltage source supplies 4.8 W of power and the current source supplies 3.6 W of power.

$R_1 = \underline{\quad 12 \quad} \Omega$  and  $R_2 = \underline{\quad 8 \quad} \Omega$


Use the given power values to determine that

$i = \frac{4.8}{12} = 0.4$  A and  $v = \frac{3.6}{0.5} = 7.2$  V. Then

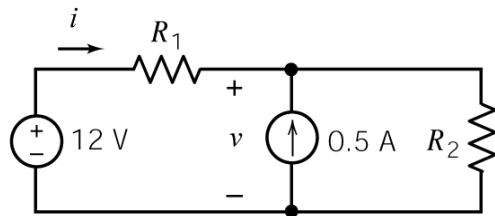$R_1 = \frac{12-7.2}{0.4} = 12 \Omega$  and  $R_2 = \frac{7.2}{0.4+0.5} = 8 \Omega$ .



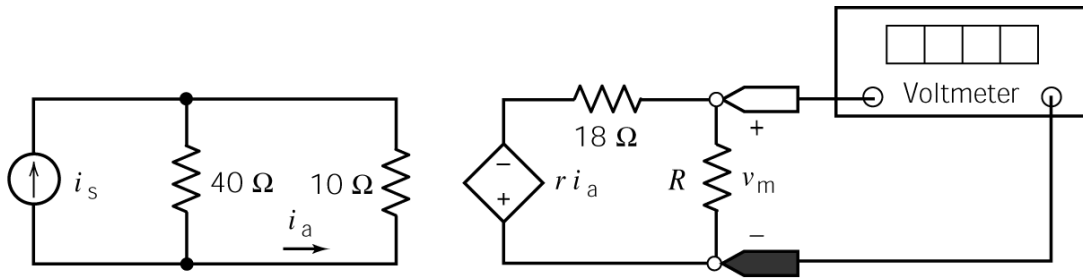3. The input this circuit is the current of the current source,  $i_s$ . The output is the voltage measured by the meter,  $v_m$ . The output is proportional to the input, that is  $v_m = k i_s$ , where  $k$  is the constant of proportionality.



a. When  $i_s = 3$  A,  $R = 12 \Omega$  and  $r = 10$  V/A, then  $i_a = \underline{\quad 2.4 \quad}$  A and  $v_m = \underline{\quad 9.6 \quad}$  V.

b. When  $R = 12 \Omega$ , then  $r = \underline{\quad 6.25 \quad}$  V/A is required to cause  $v_m = 2 i_s$ .

c. When  $r = 10$  V/A then  $R = \underline{\quad 6 \quad}$   $\Omega$  is required to cause  $v_m = 2 i_s$ .

d. When  $R = 12 \Omega$  and  $i_s = 5$  A, then  $r = \underline{\quad 7.5 \quad}$  V/A is required to cause  $v_m = 12$  V.

From current division  $i_a = -\left(\frac{40}{40+10}\right)i_s = -\left(\frac{4}{5}\right)i_s$ . From voltage division  $v_m = -\left(\frac{R}{R+18}\right)(r i_a)$ . Combining these equations gives  $v_m = -\left(\frac{R}{R+18}\right)(r)\left(-\frac{4}{5}\right)i_s$ .

When  $i_s = 3$  A,  $R = 12 \Omega$  and  $r = 10$  V/A,  $i_a = -\left(\frac{4}{5}\right)(3) = -2.4$  A and  $v_m = -\left(\frac{R}{R+18}\right)(10)(-2.4) = 9.6$  V.


When  $R = 12 \Omega$  and  $v_m = 2 i_s$  then  $2 = -\left(\frac{12}{12+18}\right)(r)\left(-\frac{4}{5}\right) \Rightarrow r = 2\left(\frac{30}{12}\right)\left(\frac{5}{4}\right) = 6.25$  V/A.

When  $r = 10$  V/A and  $v_m = 2 i_s$  then  $2 = -\left(\frac{R}{R+18}\right)(10)\left(-\frac{4}{5}\right) \Rightarrow R+18 = \left(\frac{R}{2}\right)(10)\left(\frac{4}{5}\right) \Rightarrow R = 6 \Omega$ .

When  $R = 12 \Omega$ ,  $i_s = 5$  A and  $v_m = 12$  V then  $12 = -\left(\frac{12}{12+18}\right)(r)\left(-\frac{4}{5}\right)5 \Rightarrow r = \left(\frac{12}{4}\right)\left(\frac{30}{12}\right) = 7.5$  V/A.

4. The input to this circuit is the source current,  $i_s$ . The output is the current measured by the meter,  $i_o$ . A current divider connects the source to the meter.

Given these observations:

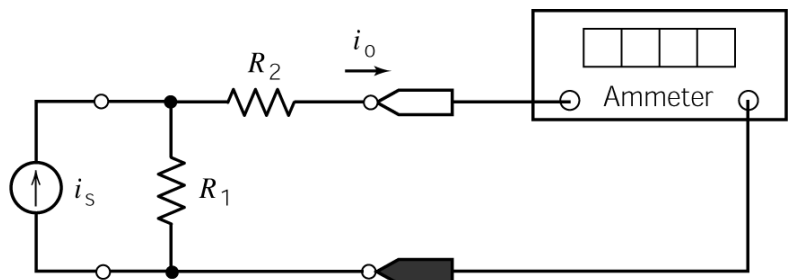

A. The input  $i_s = 5$  A causes the output to be  $i_o = 2$  A.

B. When  $i_s = 2$  A the source supplies 48 W.


The values of the resistances are  $R_1 = \underline{\hspace{2cm}}$   $\Omega$  and  $R_2 = \underline{\hspace{2cm}}$   $\Omega$ .

From current division,  $i_o = \left( \frac{R_1}{R_1 + R_2} \right) i_s$ . When  $i_s = 5$  A and  $i_o = 2$  A then  $\frac{2}{5} = \frac{R_1}{R_1 + R_2}$  so

$2(R_1 + R_2) = 5R_1$  or  $2R_2 = 3R_1$ . The power supplied by the source is given by  $i_s \left[ \left( \frac{R_1 R_2}{R_1 + R_2} \right) i_s \right]$ . When

$i_s = 2$  A the source supplies 48 W, so  $48 = 2 \left[ \left( \frac{R_1 R_2}{R_1 + R_2} \right) 2 \right] \Rightarrow 12 = \frac{R_1 R_2}{R_1 + R_2}$ .

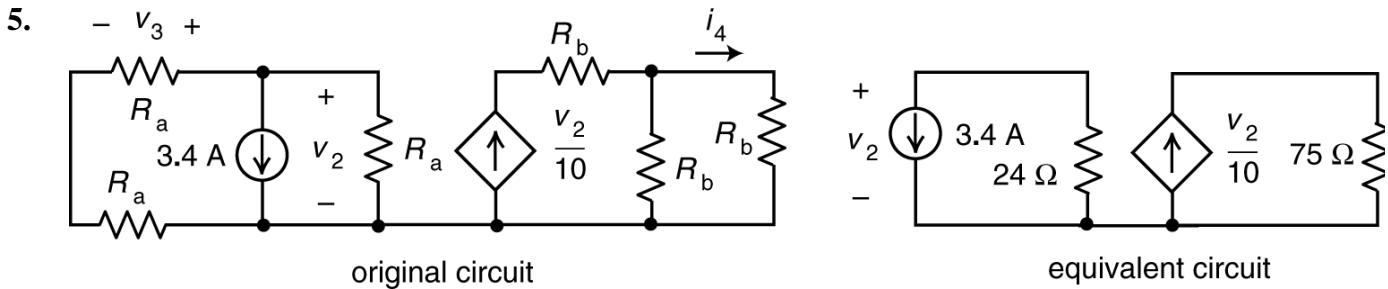Then  $12 = \frac{R_1 \left( \frac{3}{2} R_1 \right)}{R_1 + \left( \frac{3}{2} R_1 \right)} = \frac{\frac{3}{2} R_1^2}{\frac{5}{2} R_1} = \frac{3}{5} R_1 \Rightarrow R_1 = \frac{5}{3} (12) = 20 \Omega$  and  $\frac{3R_1}{2} = 30 \Omega$ .



The equivalent circuit on the right is obtained from the original circuit on the left by replacing series and parallel combinations of resistors by equivalent resistors. The original circuit contains 3 equal resistances labeled  $R_a$  and another 3 equal resistances labeled  $R_b$ . Determine the values of  $R_a$  and  $R_b$ . Given that

$v_2 = -81.6$  V, determine the values of  $v_3$  and  $i_4$ .

$R_a = \underline{\quad 36 \quad} \Omega$ ,  $R_b = \underline{\quad 50 \quad} \Omega$ ,  $v_3 = \underline{\quad -40.8 \quad} \text{V}$  and  $i_4 = \underline{\quad -4.08 \quad} \text{A}$ .

$$R_a \parallel 2R_a = \frac{2}{3} R_a = 24 \Rightarrow R_a = 24 \left( \frac{3}{2} \right) = 36 \Omega$$

and

$$R_b + \frac{R_b}{2} = \frac{3}{2} R_b = 75 \Rightarrow R_b = 50 \Omega$$

$$v_2 = -24(3.4) = -81.6 \text{ V}, v_3 = \frac{1}{2} v_2 = \frac{1}{2} (-81.6) = -40.8 \text{ V} \text{ and } i_4 = \frac{1}{2} \left( \frac{v_2}{10} \right) = \frac{-81.6}{20} = -4.08 \text{ A}$$

6. Given that



$$v_a = 8 \text{ V},$$

Determine the values of  $R_1$  and  $v_o$ :

$$R_1 = \underline{10} \text{ } \Omega,$$

and


$$v_o = \underline{-3.2} \text{ V}$$

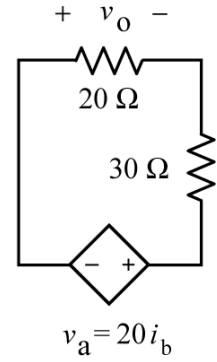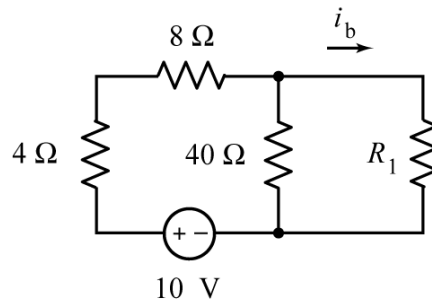

First,

$$v_o = -\frac{20}{20+30}8 = -3.2 \text{ V}$$

Next,

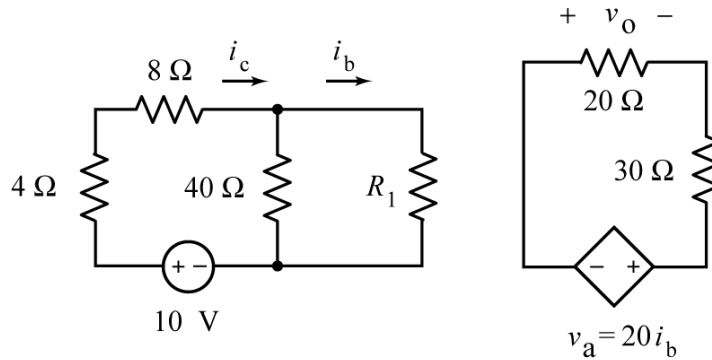


$$\frac{8}{20} = i_b = \frac{40}{40+R_1} i_c = \frac{40}{40+R_1} \left( \frac{10}{12+40 \parallel R_1} \right) = \frac{40}{40+R_1} \left( \frac{10}{12+\frac{40R_1}{40+R_1}} \right) = \frac{400}{12(40+R_1)+40R_1} = \frac{400}{480+52R_1}$$

then

$$\frac{8}{20} = \frac{400}{480+52R_1} \Rightarrow 480+52R_1 = \frac{400(20)}{8} = 1000 \Rightarrow \frac{1000-480}{52} = 10 \text{ } \Omega$$

7.

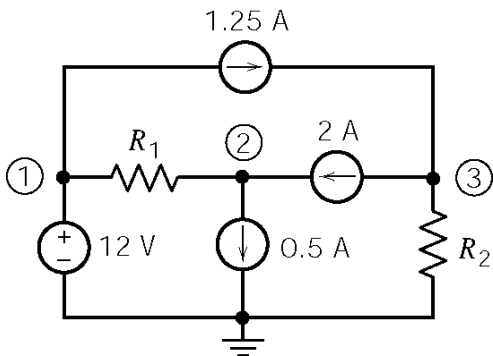

The encircled numbers are node numbers. The corresponding node voltages are

$$v_1 = 12 \text{ V}, v_2 = 21 \text{ V and } v_3 = -3 \text{ V},$$

- The 0.5 A current source **supplies**  $\underline{-10.5}$  W of power.
- The 2 A current source **supplies**  $\underline{48}$  W of power.
- $R_1 = \underline{6} \text{ } \Omega$  and  $R_2 = \underline{4} \text{ } \Omega$
- The voltage source **supplies**  $\underline{-3}$  W of power.

The power **received** by the 0.5 A current source is  $v_2(0.5) = 21(0.5) = 10.5 \text{ W}$  W of power.

The 2 A current source **supplies**  $(v_2 - v_3)(2) = [21 - (-3)](2) = 48$  W of power.

$$R_1 = \frac{v_2 - v_1}{2 - 0.5} = \frac{21 - 12}{2 - 0.5} = 6 \Omega \text{ and } R_2 = \frac{v_3}{1.25 - 2} = \frac{-3}{-0.75} = 4 \Omega$$

The voltage source **supplies**  $12[1.25 + 0.5 - 2] = 12(-0.25) = -3$  W of power.