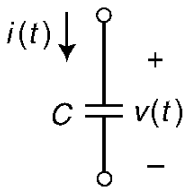


Element Equations


Capacitor:



$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$i(t) = C \frac{dv(t)}{dt}$$





Inductor:

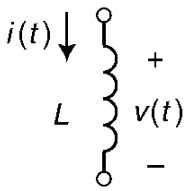

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$v(t) = L \frac{di(t)}{dt}$$

First-Order Circuits

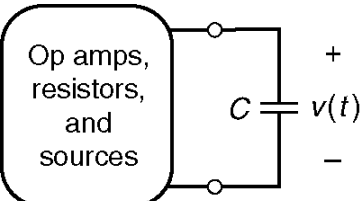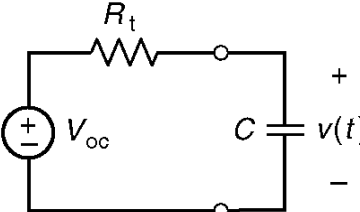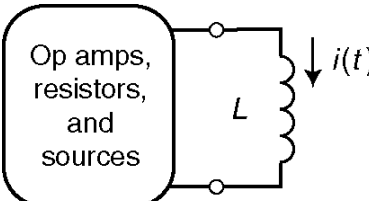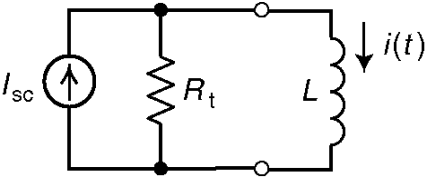FIRST-ORDER CIRCUIT CONTAINING A CAPACITOR	FIRST-ORDER CIRCUIT CONTAINING AN INDUCTOR
 <p>Replace the circuit consisting of op amps, resistors, and sources by its Thévenin equivalent circuit:</p>  <p>The capacitor voltage is:</p> $v(t) = V_{oc} + (v(0) - V_{oc}) e^{-\frac{t}{\tau}}$ <p>where the time constant, τ, is</p> $\tau = R_t C$ <p>and the initial condition, $v(0)$, is the capacitor voltage at time $t = 0$.</p>	 <p>Replace the circuit consisting of op amps, resistors, and sources by its Norton equivalent circuit:</p>  <p>The inductor current is</p> $i(t) = I_{sc} + (i(0) - I_{sc}) e^{-\frac{t}{\tau}}$ <p>where the time constant, τ, is</p> $\tau = \frac{L}{R_t}$ <p>and the initial condition, $i(0)$, is the inductor current at time $t = 0$.</p>