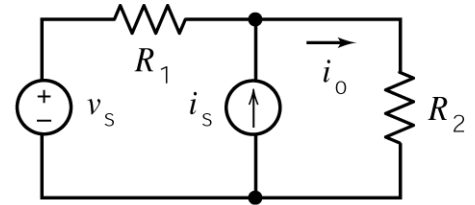


Another Sample ES 250 Second Midterm Exam

1. This circuit has two inputs, v_s and i_s , and one output i_o . The output is related to the inputs by the equation

$$i_o = a i_s + b v_s$$



Given the following two facts:

The output is $i_o = 0.45$ A when the inputs are $i_s = 0.25$ A and $v_s = 15$ V.

and

The output is $i_o = 0.30$ A when the inputs are $i_s = 0.50$ A and $v_s = 0$ V.

Determine the following:

The values of the constants a and b are $a = \underline{0.6}$ and $b = \underline{0.02}$ A/V.

The values of the resistances are $R_1 = \underline{30}$ Ω and $R_2 = \underline{20}$ Ω .

From the 1st fact: $0.45 = a(0.25) + b(15)$

From the 2nd fact: $0.30 = a(0.50) + b(0) \Rightarrow a = \frac{0.30}{0.50} = 0.60$

Substituting gives $0.45 = (0.60)(0.25) + b(15) \Rightarrow b = \frac{0.45 - (0.60)(0.25)}{15} = 0.02$

Next, consider the circuit:

$$a i_s = i_{o1} = i_o \Big|_{v_s=0} = \left(\frac{R_1}{R_1 + R_2} \right) i_s$$

so



$$0.60 = \frac{R_1}{R_1 + R_2} \Rightarrow 2R_1 = 3R_2$$

and

$$b v_s = i_{o2} = i_o \Big|_{i_s=0} = \frac{v_s}{R_1 + R_2}$$

so
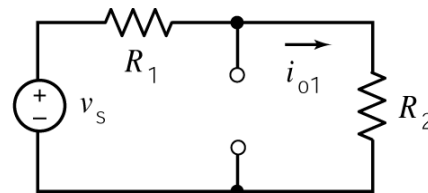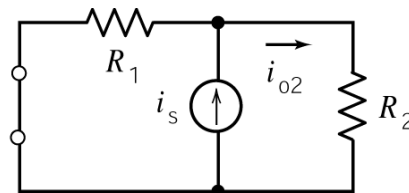
$$0.02 = \frac{1}{R_1 + R_2} \Rightarrow R_1 + R_2 = \frac{1}{0.02} = 50 \Omega$$




Solving these equations gives $R_1 = 30 \Omega$ and $R_2 = 20 \Omega$.

2. Fill in the blanks in the following statements:




When $R = 9 \Omega$ then $v_R = \underline{\quad 3 \quad}$ V.

When $R = \underline{\quad 27 \quad} \Omega$ then $v_R = 5.4$ V.

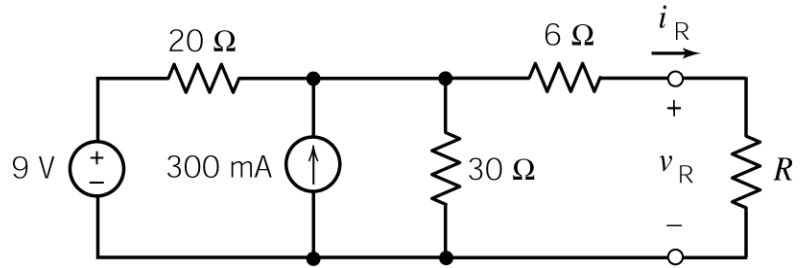When $R = \underline{\quad 12 \quad} \Omega$ then $i_R = 300$ mA.



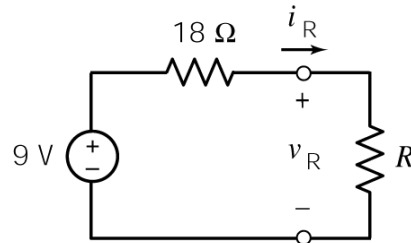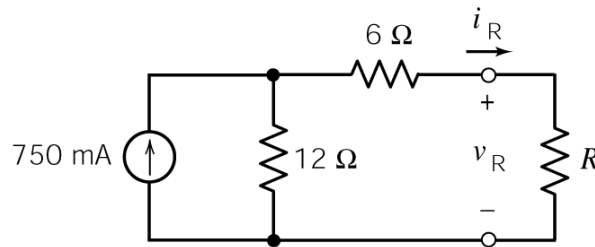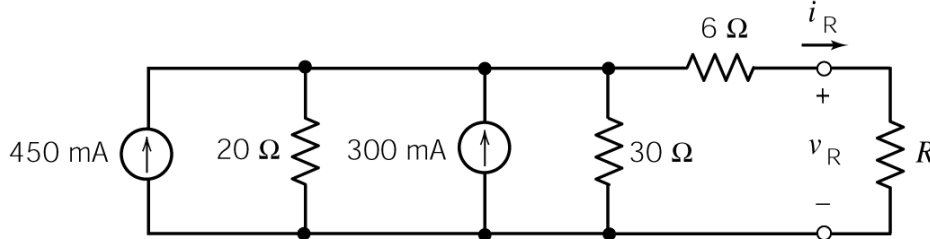Reduce this circuit using source transformations and equivalent resistance:



Now $v_R = \left(\frac{R}{R+18}\right)9$ and $i_R = \frac{9}{R+18}$ so the questions can be easily answered.

3. Determine the values of the node voltages v_a , v_b , v_c and v_o :

$$v_a = \underline{\quad 2.75 \quad} \text{ V, } v_b = \underline{\quad 2.8125 \quad} \text{ V,}$$


$$v_c = \underline{\quad 2.25 \quad} \text{ V, and } v_o = \underline{\quad 2.50 \quad} \text{ V.}$$

Due to the properties of the ideal op amp, $v_a = 2.75$ V and $v_c = 2.25$ V. The node equation at node c is


$$\frac{v_b - v_c}{10 \times 10^3} = \frac{v_c}{40 \times 10^3} \Rightarrow v_b = \frac{5}{4}v_c = 2.8125 \text{ V}$$

The node equation at node o is
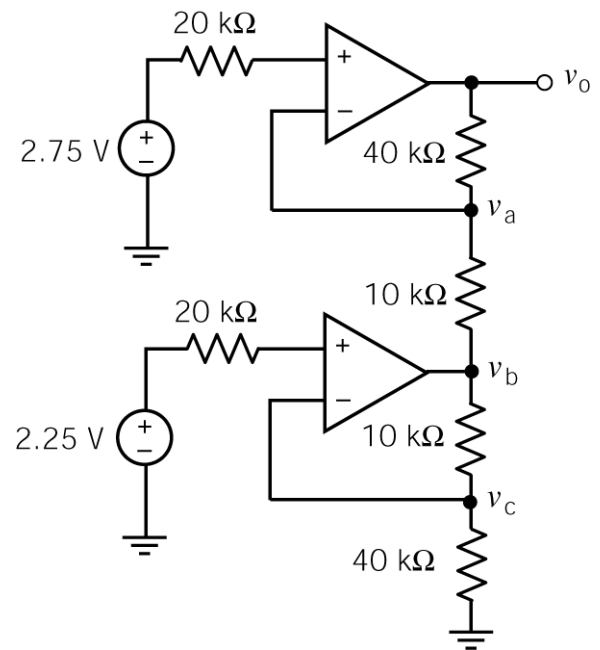
$$\frac{v_o - v_a}{40 \times 10^3} = \frac{v_a - v_b}{10 \times 10^3} \Rightarrow v_o = 5v_a - 4v_b = 2.5 \text{ V}$$



4.

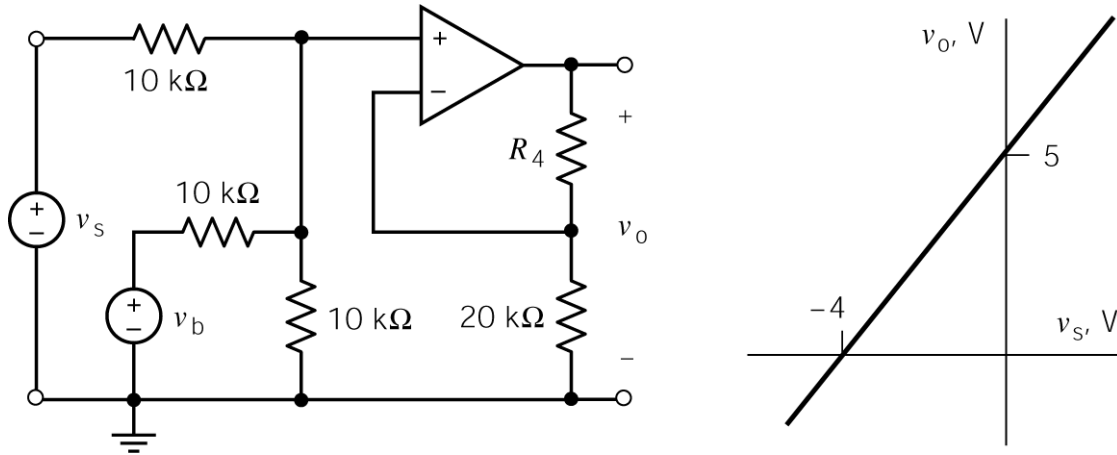

The input to this circuit is the voltage, v_s . The output is the voltage v_o . The voltage v_b is used to adjust the relationship between the input and output. Determine values of R_4 and v_b that cause the circuit input and output have the relationship specified by the graph


$$v_b = \underline{\quad 4 \quad} \text{ V and } R_4 = \underline{\quad 55 \quad} \text{ k}\Omega.$$

(a) Label the node voltages as shown. The node equations are

$$\frac{v_s - v_a}{R_1} + \frac{v_b - v_a}{R_2} = \frac{v_a}{R_3}$$

and
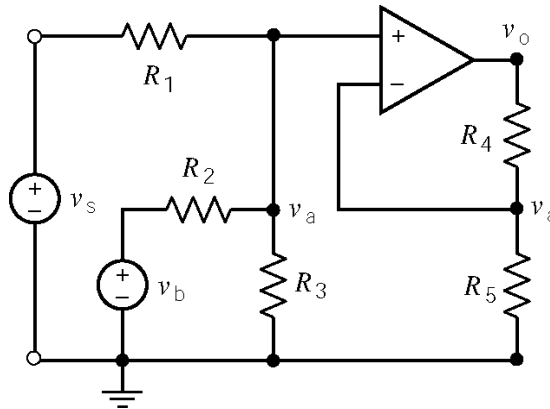
$$\frac{v_a}{R_5} = \frac{v_o - v_a}{R_4} \Rightarrow v_a = \left(\frac{R_5}{R_4 + R_5} \right) v_o$$



Solving these equations gives

$$\frac{v_s}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_a - \frac{v_b}{R_2} = \left(\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 R_2 R_3} \times \frac{R_5}{R_4 + R_5} \right) v_o - \frac{v_b}{R_2}$$

So
$$v_o = \left(\frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \times \frac{R_4 + R_5}{R_5} \right) v_s + \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \times \frac{R_4 + R_5}{R_5} \times v_b$$

When $R_1 = R_2 = R_3 = 10 \text{ k}\Omega$:
$$v_o = \left(\frac{R_4 + R_5}{3 R_5} \right) v_s + \frac{R_4 + R_5}{3 R_5} \times v_b$$

So
$$a = \frac{R_4 + R_5}{3 R_5} \text{ and } b = \frac{R_4 + R_5}{3 R_5} \times v_b$$

(b) The equation of the straight line is
$$v_o = \frac{5}{4} v_s + 5$$

We require
$$\frac{R_4 + R_5}{3 R_5} = \frac{5}{4}$$

When $R_5 = 20 \text{ k}\Omega$ then $R_4 = 55 \text{ k}\Omega$. Next we require

$$5 = \frac{R_4 + R_5}{3R_5} \times v_b = \frac{5}{4} v_b$$

i.e.


$$v_b = 4 \text{ V}$$

5. The input to this circuit is the voltage: $v(t) = 4e^{-20t} \text{ V}$ for $t > 0$

The output is the current: $i(t) = -1.2e^{-20t} - 1.5 \text{ A}$ for $t > 0$

The initial condition is $i_L(0) = -3.5 \text{ A}$. Determine the values of the resistance and inductance:
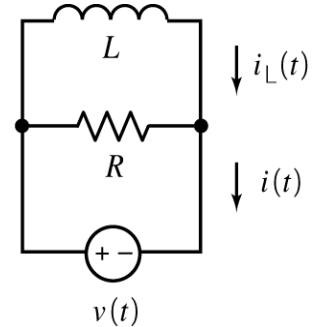
$$R = \underline{\quad 5 \quad} \Omega \quad \text{and} \quad L = \underline{\quad 0.1 \quad} \text{H}.$$



Solution: Apply KCL at either node to get

$$i(t) = \frac{v(t)}{R} + i_L(t) = \frac{v(t)}{R} + \left[\frac{1}{L} \int_0^t v(\tau) d\tau + i(0) \right]$$

That is

$$\begin{aligned} -1.2e^{-20t} - 1.5 &= \frac{4e^{-20t}}{R} + \frac{1}{L} \int_0^t 4e^{-20\tau} d\tau - 3.5 = \frac{4e^{-20t}}{R} + \frac{4}{L(-20)}(e^{-20t} - 1) - 3.5 \\ &= \left(\frac{4}{R} - \frac{1}{5L} \right) e^{-20t} + \frac{1}{5L} - 3.5 \end{aligned}$$

Equating coefficients gives $-1.5 = \frac{1}{5L} - 3.5 \Rightarrow L = 0.1 \text{ H}$

And $-1.2 = \frac{4}{R} - \frac{1}{5L} = \frac{4}{R} - \frac{1}{5(0.1)} = \frac{4}{R} - 2 \Rightarrow R = 5 \Omega$

6. The initial inductor current is $i(0) = 25$ mA.


Determine the values of the inductor current at 2, 3, 6 and 9 seconds:

$i(2) = \underline{\quad -15 \quad}$ mA,

$i(3) = \underline{\quad -55 \quad}$ mA,

$i(6) = \underline{\quad 5 \quad}$ mA,

$i(9) = \underline{\quad 65 \quad}$ mA.

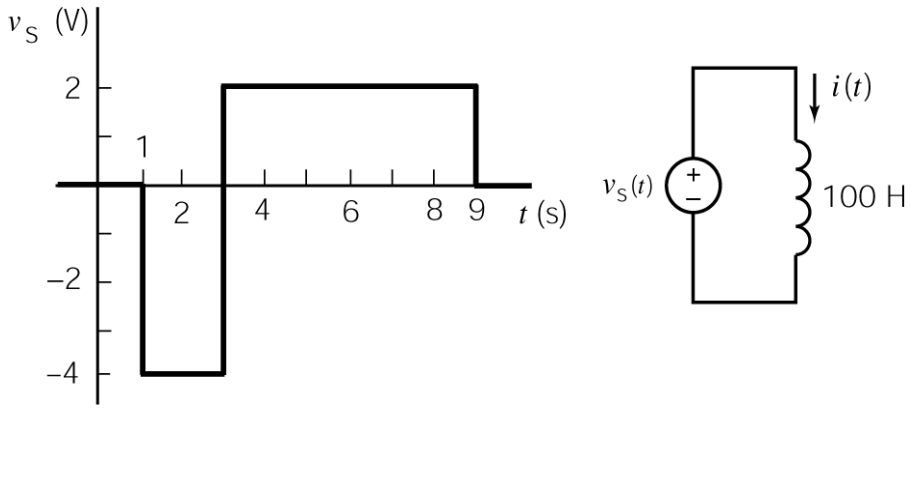

$$i(t) = \frac{1}{100} \int_0^t 0 \, d\tau + 0.025 = 0.025 \quad \text{for} \quad 0 < t < 1$$

so $i(1) = 0.025$ A

$$i(t) = \frac{1}{100} \int_1^t -4 \, d\tau + 0.025 = \frac{-4(t-1)}{100} \quad \text{for} \quad 1 < t < 3$$

so $i(2) = -0.015$ A, and $i(3) = -0.055$ A

$$i(t) = \frac{1}{100} \int_3^t 2 \, d\tau - 0.055 = \frac{2(t-3)}{100} - 0.055 \quad \text{for} \quad 3 < t < 9$$


so $i(9) = 0.065$ A

$$i(t) = \frac{1}{100} \int_9^t 0 \, d\tau + 0.065 = 0.065 \quad \text{for} \quad t > 9$$

7.

a. When $C = 10$ F then $C_{eq} = \underline{\quad 25 \quad}$ F.

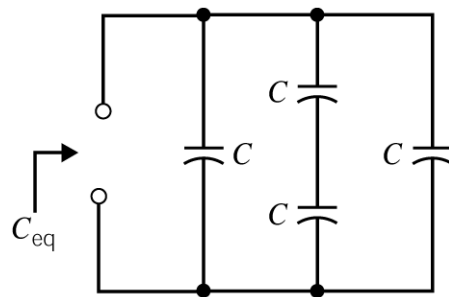b. When $C = \underline{\quad 3.2 \quad}$ F then $C_{eq} = 8$ F.



$$C_{eq} = C + \frac{C \times C}{C + C} + C = \frac{5}{2} C$$

8. This circuit has reached steady state before the switch opens at time $t = 0$. Determine the values of $i_L(t)$, $v_C(t)$ and $v_R(t)$ immediately before the switch opens:


$$i_L(0^-) = \underline{\quad 1 \quad} \text{A}, \quad v_C(0^-) = \underline{\quad 20 \quad} \text{V}$$

and

$$v_R(0^-) = \underline{\quad -5 \quad} \text{V}$$

Determine the value of $v_R(t)$ immediately after the switch opens:
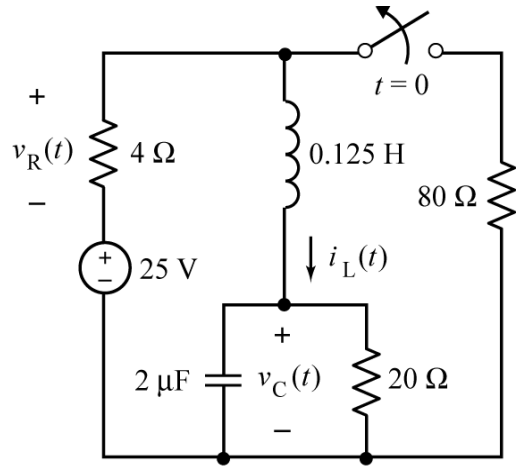
$$v_R(0^+) = \underline{\quad -4 \quad} \text{V}$$



Solution: Because

- This **circuit has reached steady state** before the switch opens at time $t = 0$.
- The only source is a **constant voltage source**.


At $t = 0^-$, the **capacitor acts like an open circuit** and the **inductor acts like a short circuit**. From the circuit

$$i_1(0^-) = \frac{25}{4 + (20 \parallel 80)} = \frac{25}{4 + 16} = 1.25 \text{ A},$$

$$i_L(0^-) = \left(\frac{80}{20 + 80} \right) i_1(0^-) = 1 \text{ A}, \quad v_C(0^-) = 20 i_L(0^-) = 20 \text{ V}$$

and
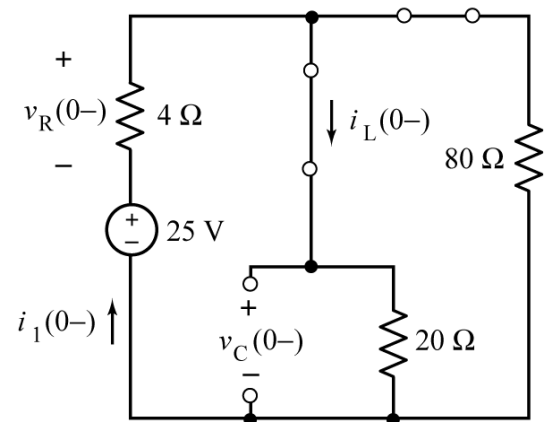
$$v_R(0^-) = -4 i_1(0^-) = -5 \text{ V}$$



The **capacitor voltage and inductor current don't change instantaneously** so

$$v_C(0^+) = v_C(0^-) = 20 \text{ V} \quad \text{and} \quad i_L(0^+) = i_L(0^-) = 1 \text{ A}$$


Apply KCL at the top node to see that

$$i_1(0^+) = i_L(0^+) = 1 \text{ A}$$


From Ohm's law

$$v_R(0^+) = -4 i_1(0^+) = -4 \text{ V}$$

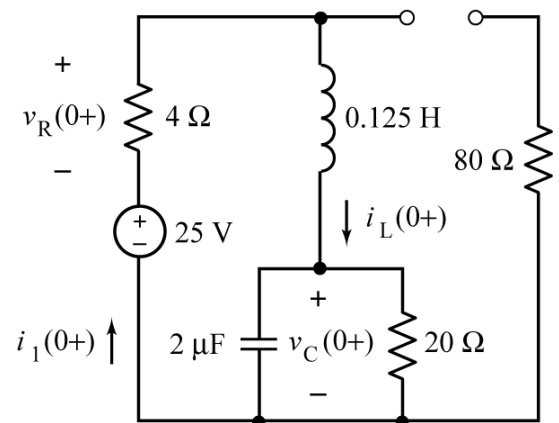(Notice that the resistor voltage did change instantaneously.)



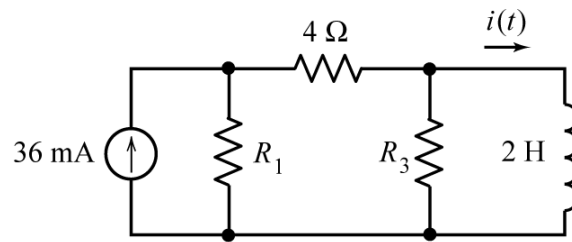9. After time $t = 0$, a given circuit is represented by this circuit diagram.



a. Suppose that the inductor current is

$$i(t) = 21.6 + 28.4e^{-4t} \text{ mA for } t \geq 0$$

Determine the values of R_1 and R_3 : $R_1 = \underline{6} \Omega$ and $R_3 = \underline{40} \Omega$.

b. Suppose instead that $R_1 = 16 \Omega$, $R_3 = 20 \Omega$, the initial condition is $i(0) = 10 \text{ mA}$, and the inductor current is $i(t) = A - Be^{-at}$ for $t \geq 0$. Determine the values of the constants A , B , and a :

$$A = \underline{28.8} \text{ mA}, \quad B = \underline{-18.8} \text{ mA} \quad \text{and} \quad a = \underline{5} \text{ s}^{-1}$$

Solution:

The inductor current is given by $i(t) = i_{sc} + (i(0) - i_{sc})e^{-at}$ for $t \geq 0$ where $a = \frac{1}{\tau} = \frac{R_t}{L}$.

a. Comparing this to the given equation gives $21.6 = i_{sc} = \frac{R_1}{R_1 + 4}(36) \Rightarrow R_1 = 6 \Omega$ and

$$4 = \frac{R_t}{2} \Rightarrow R_t = 8 \Omega. \text{ Next } 8 = R_t = (R_1 + 4) \parallel R_3 = 10 \parallel R_3 \Rightarrow R_3 = 40 \Omega.$$

b. $R_t = (16 + 4) \parallel 20 = 10 \Omega$ so $a = \frac{1}{\tau} = \frac{10}{2} = 5 \text{ s}^{-1}$. also $i_{sc} = \frac{16}{16 + 4}(36) = 28.8 \text{ mA}$. Then


$$i(t) = i_{sc} + (i(0) - i_{sc})e^{-at} = 28.8 + (10 - 28.8)e^{-5t} = 28.8 - 18.8e^{-5t}.$$

10. a) Determine the time constant, τ , and the steady state capacitor voltage, $v(\infty)$, when the switch is **open**:

$$\tau = \underline{3} \text{ s} \quad \text{and} \quad v(\infty) = \underline{24} \text{ V}$$

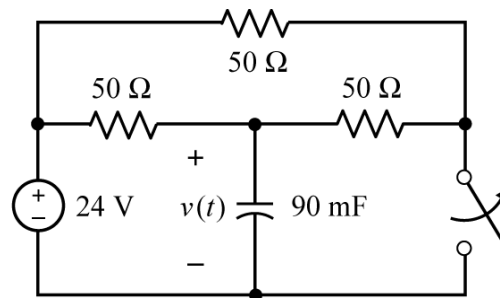
b) Determine the time constant, τ , and the steady state capacitor voltage, $v(\infty)$, when the switch is **closed**:

$$\tau = \underline{2.25} \text{ s} \quad \text{and} \quad v(\infty) = \underline{12} \text{ V}$$



Solution:

a.) When the switch is open we have

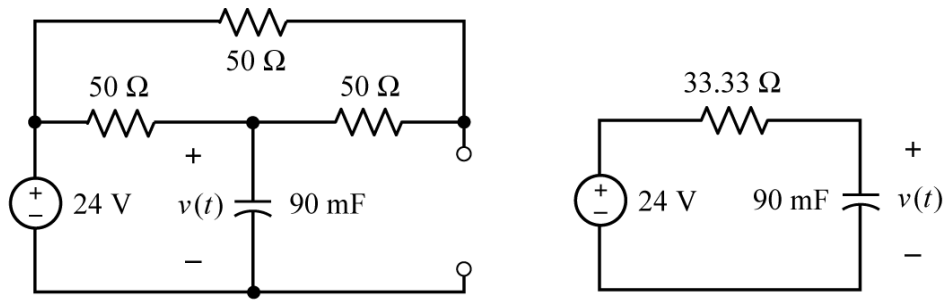


After replacing series and parallel resistors by equivalent resistors, the part of the circuit connected to the capacitor is a Thevenin equivalent circuit with $R_t = 33.33 \Omega$. The time constant is


$$\tau = R_t C = 33.33(0.090) = 3 \text{ s.}$$

Since the input is constant, the capacitor acts like an open circuit when the circuit is at steady state. Consequently, there is zero current in the 33.33Ω resistor and KVL gives $v(\infty) = 24 \text{ V}$.


b.) When the switch is closed we have

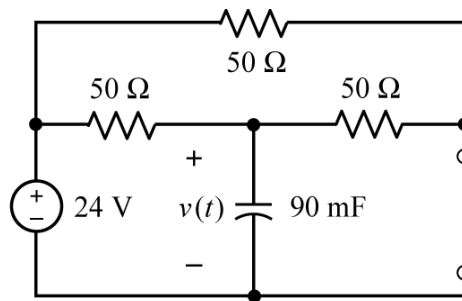

This circuit can be redrawn as

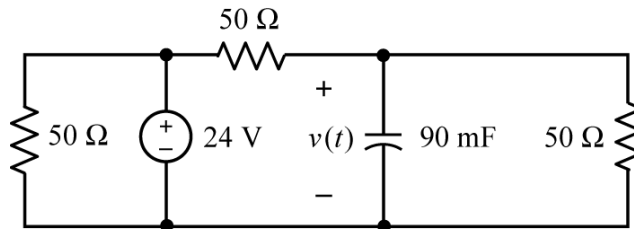

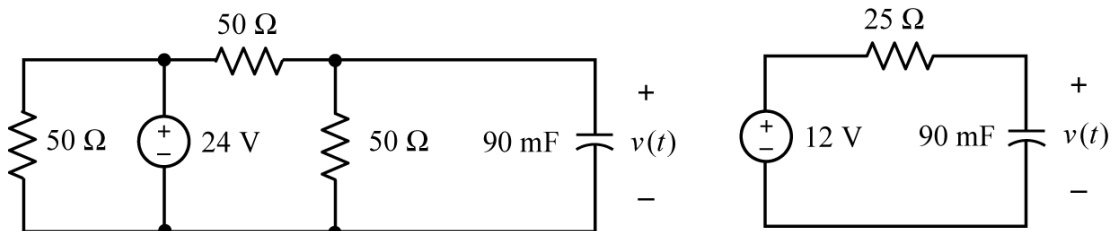Now we find the Thevenin equivalent of the part of the circuit connected to the capacitor:



So $R_t = 25 \Omega$ and

$$\tau = R_t C = 25(0.090) = 2.25 \text{ s}$$

Since the input is constant, the capacitor acts like an open circuit when the circuit is at steady state. Consequently, there is zero current in the 25Ω resistor and KVL gives $v(\infty) = 12 \text{ V}$.