

Solutions

P1 Use the properties of the ideal op amp to label the circuit as shown.

Then


$$i_6 = \frac{v_2 - v_1}{R_6}$$

and


$$v_o + (R_5 + R_6 + R_7)i_6 = 0$$

so
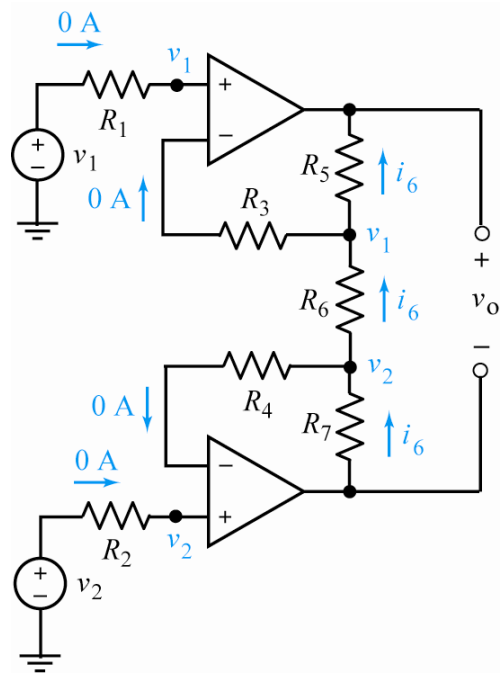
$$\begin{aligned} v_o &= -(R_5 + R_6 + R_7) \frac{v_2 - v_1}{R_6} \\ &= -\frac{R_5 + R_6 + R_7}{R_6} (v_2 - v_1) \end{aligned}$$



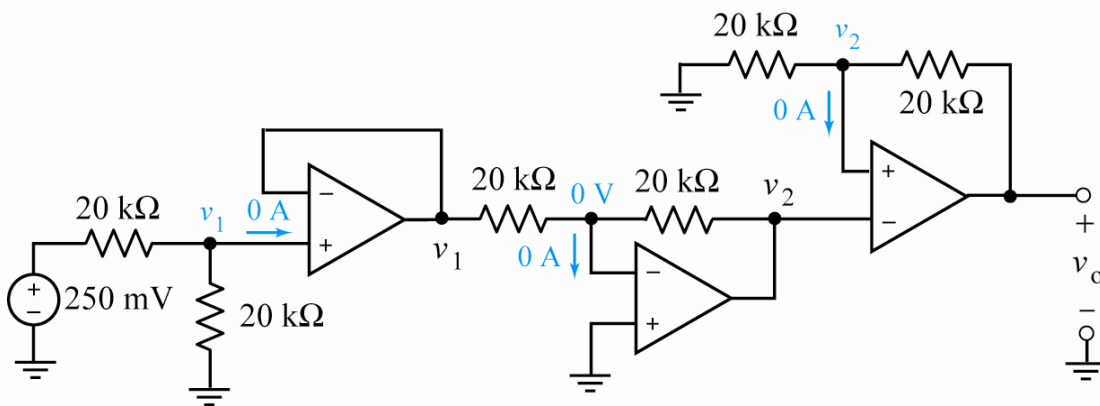P2 Use the properties of the ideal op amp to label the circuit as shown.



Then

$$\frac{0.25 - v_1}{20 \times 10^3} = \frac{v_1}{20 \times 10^3} + 0 \Rightarrow v_1 = 0.125 \text{ V} = 125 \text{ mV}$$

$$\frac{v_1}{20 \times 10^3} + \frac{v_2}{20 \times 10^3} = 0 \Rightarrow v_2 = -v_1 = -0.125 \text{ V} = -125 \text{ mV}$$

$$\frac{v_o - v_2}{20 \times 10^3} = \frac{v_2}{20 \times 10^3} + 0 \Rightarrow v_o = 2v_2 = -0.25 \text{ V} = -25 \text{ mV}$$