

P1


Node equations:

$$\frac{v_a - v_2}{R_5} = \frac{v_2}{R_6} \Rightarrow v_a = \left(\frac{R_5 + R_6}{R_6} \right) v_2$$


$$\frac{v_o - v_1}{R_3} = \frac{v_1 - v_a}{R_4} \Rightarrow v_o = \left(1 + \frac{R_3}{R_4} \right) v_1 - \left(\frac{R_3}{R_4} \right) v_a$$

Substituting for v_a gives
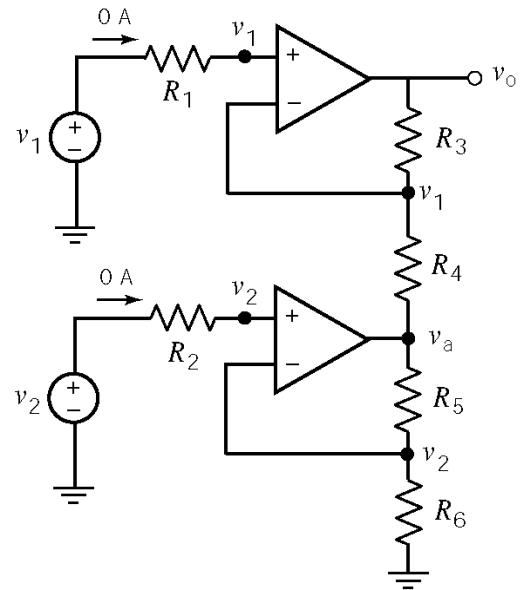
$$v_o = \left(1 + \frac{R_3}{R_4} \right) v_1 - \left(\frac{R_3}{R_4} \right) \left(\frac{R_5 + R_6}{R_6} \right) v_2$$



P2

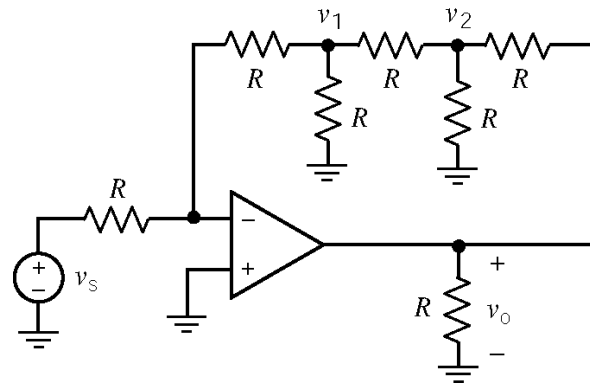

Writing node equations:


$$\frac{v_s}{R} + \frac{v_1}{R} = 0 \Rightarrow v_1 = -v_s$$

$$\frac{v_1}{R} + \frac{v_1}{R} + \frac{v_1 - v_2}{R} = 0 \Rightarrow v_2 = 3v_1 = -3v_s$$

$$\frac{v_2 - v_1}{R} + \frac{v_2}{R} + \frac{v_2 - v_o}{R} = 0 \Rightarrow v_o = 3v_2 - v_1 = -8v_s$$

P3

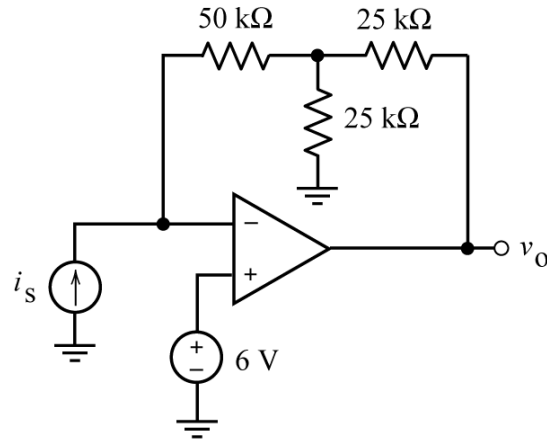The input to this circuit is the voltage source voltage v_s . The output is the node voltage v_o . The output is related to the input by the equation $v_o = m i_s + b$ where m and b are constants. Determine the values of m and b .



P4

The values of the node voltages v_1 , v_2 and v_o in this circuit are $v_1 = 6.25$ V, $v_2 = 3.75$ V and $v_o = -15$ V. Determine the value of the resistances R_1 , R_2 and R_3 :

