

ES 250 Practice Final Exam

1. Given that


$$v_a = 8 \text{ V},$$

Determine the values of R_1 and v_o :

$$R_1 = \underline{\quad 10 \quad} \Omega,$$

and
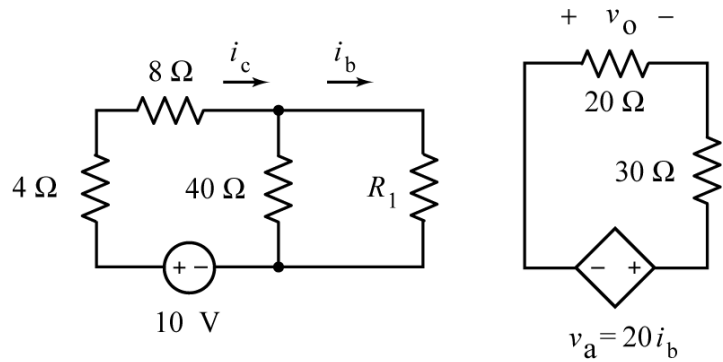
$$v_o = \underline{\quad -3.2 \quad} \text{ V}$$




2. Given that $0 \leq R \leq \infty$ in this circuit, consider these two observations:

When $R = 2 \Omega$ then $v_R = 4 \text{ V}$ and $i_R = 2 \text{ A}$.


When $R = 6 \Omega$ then $v_R = 6 \text{ V}$ and $i_R = 1 \text{ A}$.

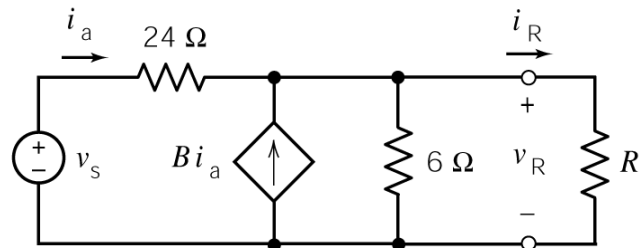Fill in the blanks in the following statements:



- The maximum value of i_R is $\underline{\quad 4 \quad}$ A.
- The maximum value of v_R is $\underline{\quad 8 \quad}$ V.
- The maximum value of $p_R = i_R v_R$ occurs when $R = \underline{\quad 2 \quad}$ Ω .
- The maximum value of $p_R = i_R v_R$ is $\underline{\quad 8 \quad}$ W.

3.

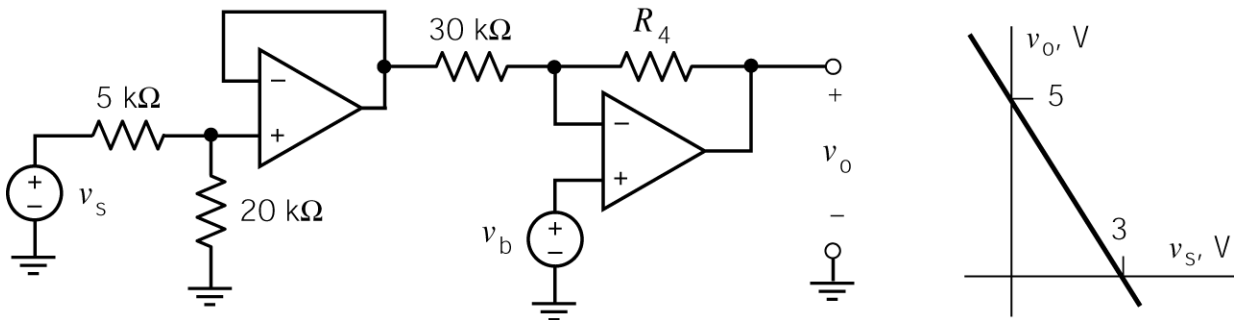


The input to this circuit is the voltage, v_s . The output is the voltage v_o . The voltage v_b is used to adjust the relationship between the input and output. Determine values of R_4 and v_b that cause the circuit input and output have the relationship specified by the graph

$$v_b = \underline{\quad 1.62 \quad} \text{ V and } R_4 = \underline{\quad 62.5 \quad} \text{ k}\Omega.$$

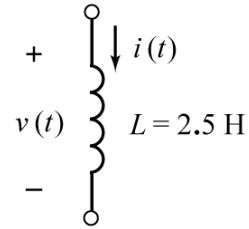4. Consider this inductor. The current and voltage are given by


$$i(t) = \begin{cases} 5t - 4.6 & 0 \leq t \leq 0.2 \\ at + b & 0.2 \leq t \leq 0.5 \\ c & t \geq 0.5 \end{cases} \quad \text{and} \quad v(t) = \begin{cases} 12.5 & 0 < t < 0.2 \\ 25 & 0.2 < t < 0.5 \\ 0 & t > 0.5 \end{cases}$$



where a, b and c are real constants. (The current is given in Amps, the voltage in Volts and the time in seconds.) Determine the values of the constants:

$$a = \underline{10} \text{ A/s}, \quad b = \underline{-5.6} \text{ A} \quad \text{and} \quad c = \underline{-0.6} \text{ A}$$

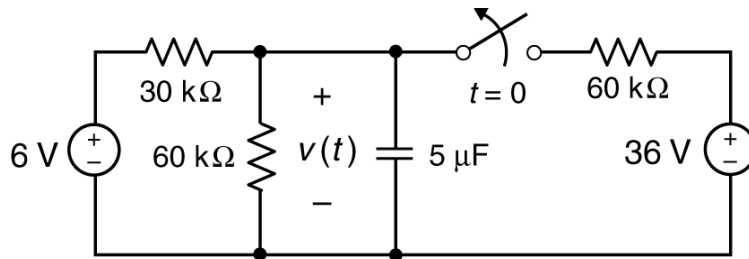5. This circuit is at steady state when the switch opens at time $t = 0$.



The capacitor voltage is $v(t) = A + B e^{-at}$ for $t \geq 0$. Determine the values of the constants A, B, and a:

$$A = \underline{4} \text{ V}, \quad B = \underline{8} \text{ V} \quad \text{and} \quad a = \underline{10} \text{ s}^{-1}$$

6. This circuit is at steady state before the switch closes at time $t = 0$. After the switch closes, the inductor current is given by


$$i(t) = 0.6 - 0.2 e^{-5t} \text{ A} \quad \text{for } t \geq 0$$

Determine the values of R_1 , R_2 and L :

$$R_1 = \underline{20} \text{ } \Omega, \quad R_2 = \underline{10} \text{ } \Omega$$

and

$$L = \underline{4} \text{ H}$$

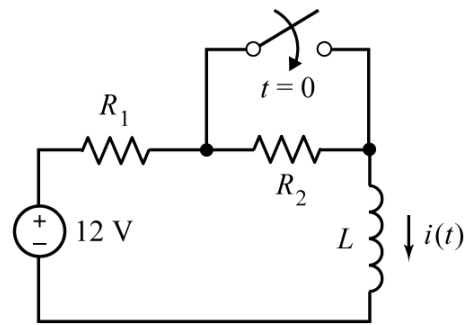


7. The voltage and current for this circuit are given by


$$v(t) = 20 \cos(20t + 15^\circ) \text{ V} \quad \text{and} \quad i(t) = 1.49 \cos(20t + 63^\circ) \text{ A}$$

Determine the values of the resistance, R, and capacitance, C:
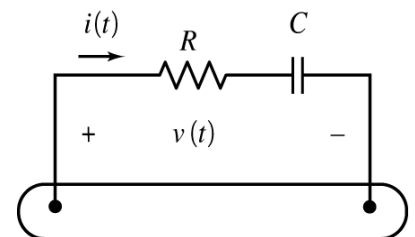
$$R = \underline{9} \text{ } \Omega \quad \text{and} \quad C = \underline{5} \text{ } \mu\text{F}$$



8.

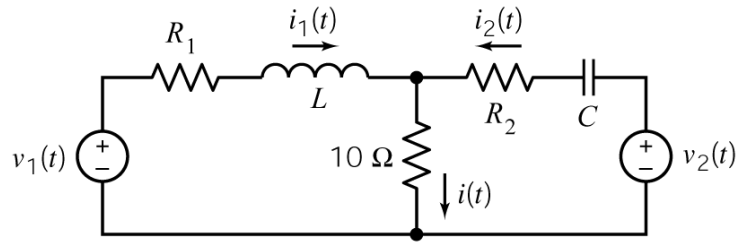

This circuit is at steady state. The voltage source voltages are given by

$$v_1(t) = 12 \cos(2t - 90^\circ) \text{ V} \quad \text{and} \quad v_2(t) = 5 \cos(2t + 90^\circ) \text{ V}$$

The currents are given by

$$i_1(t) = 744 \cos(2t - 118^\circ) \text{ mA}, \quad i_2(t) = 540.5 \cos(2t + 100^\circ) \text{ mA} \quad \text{and} \quad i(t) = A \cos(2t - 164^\circ) \text{ mA}$$

Determine the values of A , R_1 , R_2 , L and C :


$$A = \underline{\underline{460}} \text{ mA}, \quad R_1 = \underline{\underline{10}} \text{ } \Omega, \quad R_2 = \underline{\underline{10}} \text{ } \Omega, \quad L = \underline{\underline{6}} \text{ H} \quad \text{and} \quad C = \underline{\underline{50}} \text{ mF}.$$

9. The input this circuit is the current

$$i_s(t) = 2 \cos(5t + 15^\circ) \text{ A}.$$

In the frequency domain, this circuit is represented by the node equation
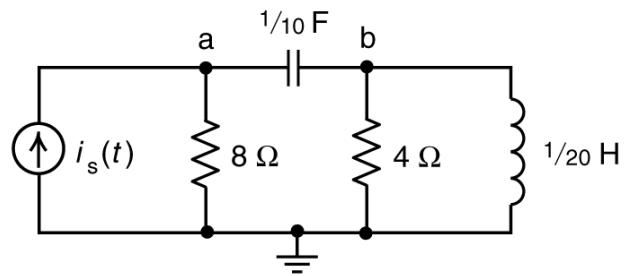
$$\begin{bmatrix} d + j0.5 & -j0.5 \\ -j0.5 & 0.25 + je \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} 2 \angle 15^\circ \\ 0 \end{bmatrix}$$



where \mathbf{V}_a and \mathbf{V}_b are the phasor node voltages and d and e are real numbers. Determine the values of d and e .

$$d = \underline{\underline{0.125}} \text{ } \Omega \quad \text{and} \quad e = \underline{\underline{-3.5}} \text{ } \Omega$$