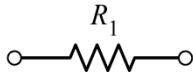


## Monte Carlo Analysis



$R_{1 \text{ nom}}$  = nominal resistance

$rand$  = random number  $\in (0,1]$

$2 * rand - 1$  = random number  $\in (-1,1]$

$t_1$  = tolerance in %


$$R_1 = R_{1 \text{ nom}} \left( 1 + (2 * rand - 1) \left( \frac{t_1}{100} \right) \right) = \text{actual resistance}$$

Notice that

$$R_{1 \text{ nom}} \left( 1 - \frac{t_1}{100} \right) < R_1 \leq R_{1 \text{ nom}} \left( 1 + \frac{t_1}{100} \right)$$

Voltage Divider:
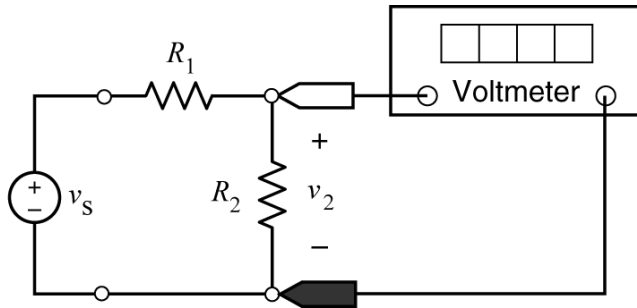
$$v_2 = \left( \frac{R_2}{R_1 + R_2} \right) v_s \triangleq G v_s$$



$$G = \frac{R_2}{R_1 + R_2} = \frac{R_{2 \text{ nom}} \left( 1 + (2 * rand_2 - 1) \left( \frac{t_2}{100} \right) \right)}{R_{1 \text{ nom}} \left( 1 + (2 * rand_1 - 1) \left( \frac{t_1}{100} \right) \right) + R_{1 \text{ nom}} \left( 1 + (2 * rand_2 - 1) \left( \frac{t_2}{100} \right) \right)}$$

**Example:** Consider a voltage divider with nominal resistances  $R_{1 \text{ nom}} = 100 \Omega$  and  $R_{2 \text{ nom}} = 400 \Omega$  and tolerances  $t_1 = t_2 = 5\%$ . Suppose the first two calls to  $rand$  return  $rand_1 = 0.21347$  and  $rand_2 = 0.83721$ .

Determine the actual values of the resistances:  $R_1 = \underline{\hspace{2cm}} \Omega$  and  $R_2 = \underline{\hspace{2cm}} \Omega$ .

$$\begin{aligned} R_1 &= R_{1 \text{ nom}} \left( 1 + (2 * rand - 1) \left( \frac{t_1}{100} \right) \right) = 100 \left( 1 + (2 * 0.21347 - 1) \left( \frac{5}{100} \right) \right) \\ &= 100(1 - 0.57306(0.05)) = 97.1347 \Omega \end{aligned}$$

and

$$R_2 = R_{2 \text{ nom}} \left( 1 + (2 * rand_2 - 1) \left( \frac{t_2}{100} \right) \right) = 400 \left( 1 + (2 * 0.83721 - 1) \left( \frac{5}{100} \right) \right) \\ = 400(1 + 0.67442(0.05)) = 413.4884 \Omega$$

Determine the nominal and actual values of gain of the voltage divider:

$$G_{\text{nom}} = \underline{\hspace{2cm}} \text{ V/V and } G_{\text{act}} = \underline{\hspace{2cm}} \text{ V/V}$$

$$G_{\text{nom}} = \frac{R_{2 \text{ nom}}}{R_{1 \text{ nom}} + R_{2 \text{ nom}}} = \frac{400}{100 + 400} = 0.8 \text{ V/V}$$

and

$$G_{\text{act}} = \frac{R_2}{R_1 + R_2} = \frac{413.4884}{97.1374 + 413.4884} = 0.809772 \text{ V/V}$$

Here's a MATLAB script that performs a Monte Carlo analysis of a voltage divider:

```
%vdivMonte.m
R1nom=750; %Nominal resistance values
R2nom=250;
t1=2; %Resistor tolerances in %
t2=2;
Gnom=R2nom/(R1nom+R2nom); %nominal gain
tg=1.5; %Gain tolerance
n=15; %Number of trials
m=0; %

fprintf('\n')
fprintf(' R1 R2 vo/vs \n')
fprintf('-----\n')
for i=1:n
    R1=(1+(2*rand-1)*t1/100)*R1nom; %actual resistance values
    R2=(1+(2*rand-1)*t1/100)*R2nom;
    G = R2/(R1+R2); %voltage divider gain
    if abs(G-Gnom)/Gnom<tg/100
        m=m+1;
    end
    fprintf(' %6.3f %6.3f %6.4f \n',R1,R2,G)
end
fprintf('\n%4.1f%% of the voltage dividers have a ',100*m/n)
fprintf('gain\nthat is within %3.1f%% of %4.2f.\n',tg,Gnom)
```

Here's what happens when we execute that MATLAB script:

```
>> vdivMonte
```

R1	R2	vo/vs
763.504	247.311	0.2447
753.205	249.860	0.2491
761.739	252.621	0.2490
748.694	245.185	0.2467
759.642	249.447	0.2472
753.463	252.919	0.2513
762.654	252.382	0.2486
740.288	249.057	0.2517
763.064	254.169	0.2499
747.308	253.936	0.2536
736.737	248.529	0.2522
759.395	245.099	0.2440
739.167	247.028	0.2505
740.962	251.038	0.2531
743.166	246.988	0.2494


86.7% of the voltage dividers have a gain that is within 1.5% of 0.25.

```
>>
```
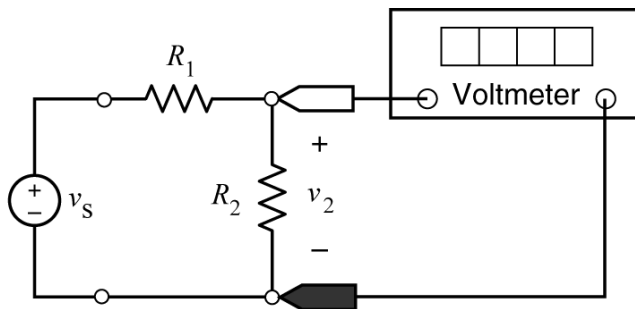
## “Worst-case” Analysis

Voltage Divider:

$$v_2 = \left( \frac{R_2}{R_1 + R_2} \right) v_s \triangleq G v_s$$



It can be shown that:

$$\frac{R_{2 \text{ nom}} \left( 1 - \frac{t_2}{100} \right)}{R_{1 \text{ nom}} \left( 1 + \frac{t_1}{100} \right) + R_{2 \text{ nom}} \left( 1 - \frac{t_2}{100} \right)} < G \leq \frac{R_{2 \text{ nom}} \left( 1 + \frac{t_2}{100} \right)}{R_{1 \text{ nom}} \left( 1 - \frac{t_1}{100} \right) + R_{2 \text{ nom}} \left( 1 + \frac{t_2}{100} \right)}$$

**Example:** Consider a voltage divider with nominal resistances  $R_{1 \text{ nom}} = 100 \Omega$ ,  $R_{2 \text{ nom}} = 400 \Omega$  and tolerances  $t_1 = t_2 = 5\%$ .

Determine the range values of gain of the voltage divider:

$$G_{\min} = \underline{\hspace{2cm}} < G \leq G_{\max} = \underline{\hspace{2cm}}$$

Determine appropriate tolerance for the gain of the voltage divider:  $t_G = \underline{\hspace{2cm}}\%$

**Example:** Consider a voltage divider with nominal resistances  $R_{1 \text{ nom}} = 80 \Omega$ ,  $R_{2 \text{ nom}} = 20 \Omega$  and tolerances  $t_1 = t_2 = 2\%$ .

Suppose we measure  $v_2 = 4.8696 \text{ V}$  when  $v_s = 24 \text{ V}$ . Is this measurement explained by the resistor tolerances?

$$0.1937 = \frac{20(0.98)}{80(1.02) + 20(0.98)} < G \leq \frac{20(1.02)}{80(0.98) + 20(1.02)} = 0.2065$$

Since 
$$0.1937 < \frac{4.8696}{24} = 0.2029 < 0.2065$$

The error could be entirely due to the resistor tolerances.