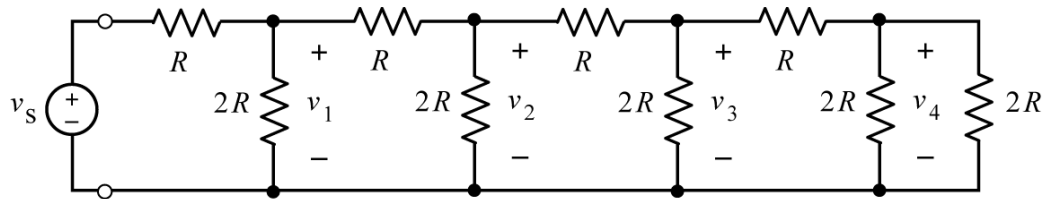


R-2R Ladder Networks

Example

Consider the R-2R ladder network:










Show that

$$v_1 = \frac{1}{2^1} v_s = \frac{1}{2} v_s, \quad v_2 = \frac{1}{2^2} v_s = \frac{1}{4} v_s, \quad v_3 = \frac{1}{2^3} v_s = \frac{1}{8} v_s \quad \text{and} \quad v_4 = \frac{1}{2^4} v_s = \frac{1}{16} v_s$$

Solution

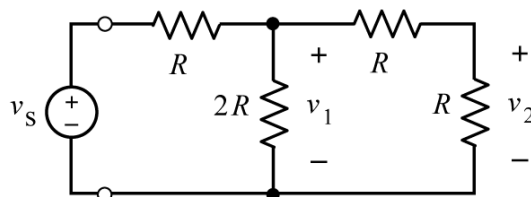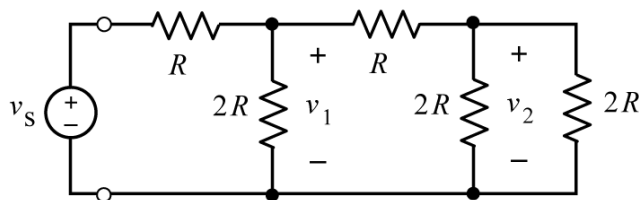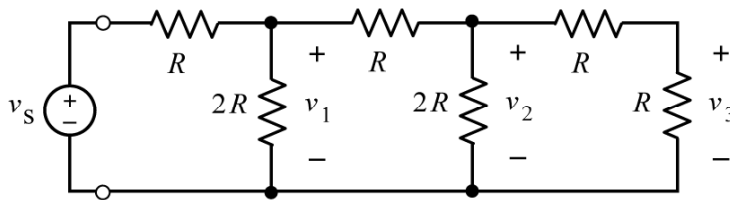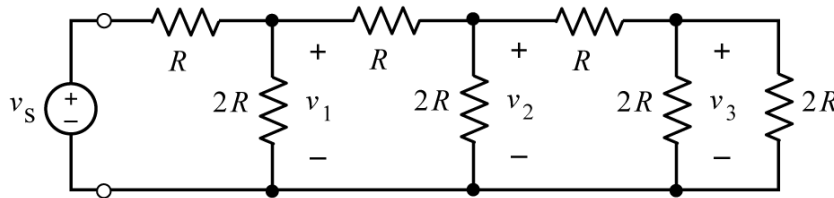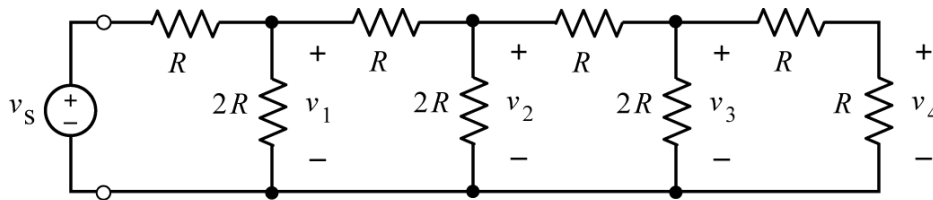Reduce the circuit using equivalent resistances as follows:



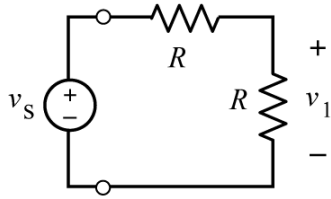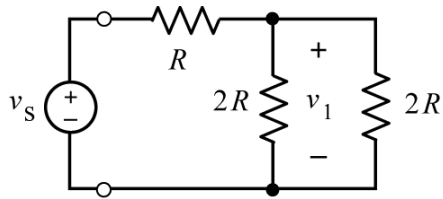

Using voltage division, we see that

$$v_4 = \frac{1}{2}v_3, v_3 = \frac{1}{2}v_2, v_2 = \frac{1}{2}v_1, \text{ and } v_1 = \frac{1}{2}v_s$$

Consequently

$$v_1 = \frac{1}{2^1}v_s = \frac{1}{2}v_s, v_2 = \frac{1}{2^2}v_s = \frac{1}{4}v_s, v_3 = \frac{1}{2^3}v_s = \frac{1}{8}v_s \text{ and } v_4 = \frac{1}{2^4}v_s = \frac{1}{16}v_s$$