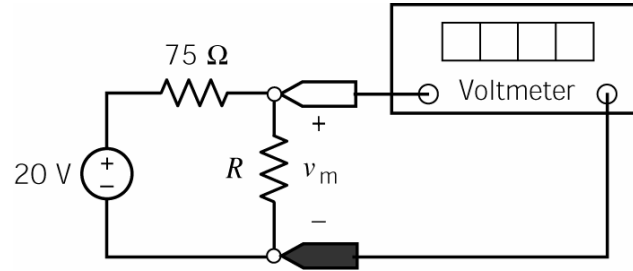


Example

Consider the voltage divider circuit



The resistor represents a temperature sensor. Suppose the resistance R , in Ω , is related to the temperature T , in $^{\circ}\text{C}$, by the equation

$$R = 50 + \frac{1}{2}T$$

Suppose the temperature is expected to be in the range $0^{\circ}\text{C} \leq T \leq 100^{\circ}\text{C}$.

- Determine the meter voltage, v_m , corresponding to temperatures 0°C , 75°C and 100°C .
- Determine the temperature, T , corresponding to the meter voltages 8 V , 10 V and 15 V .

Solution

Using voltage division

$$v_m = \left(\frac{R}{75 + R} \right) 20$$

Solving for R yields

$$R = \frac{75v_m}{20 - v_m}$$

The temperature can be calculated from the resistance using

$$T = 2(R - 50) = 2 \left(\frac{75v_m}{20 - v_m} - 50 \right) = \frac{150v_m}{20 - v_m} - 100$$

a) At 0°C the resistance is $R = 50\ \Omega$ so $v_m = \left(\frac{50}{75 + 50} \right) 20 = 8\text{ V}$. At 75°C the resistance is

$R = 87.5\ \Omega$ so $v_m = \left(\frac{87.5}{75 + 87.5} \right) 20 = 10.77\text{ V}$. At 100°C the resistance is $R = 100\ \Omega$ so

$v_m = \left(\frac{100}{75 + 100} \right) 20 = 11.43\text{ V}$.

b) When $v_m = 8\text{ V}$, the temperature is $T = \frac{150(8)}{20 - 8} - 100 = 0^{\circ}\text{C}$. When $v_m = 10\text{ V}$, the temperature is

$T = \frac{150(10)}{20 - 10} - 100 = 50^{\circ}\text{C}$. When $v_m = 15\text{ V}$, the temperature is $T = \frac{150(15)}{20 - 15} - 100 = 350^{\circ}\text{C}$.